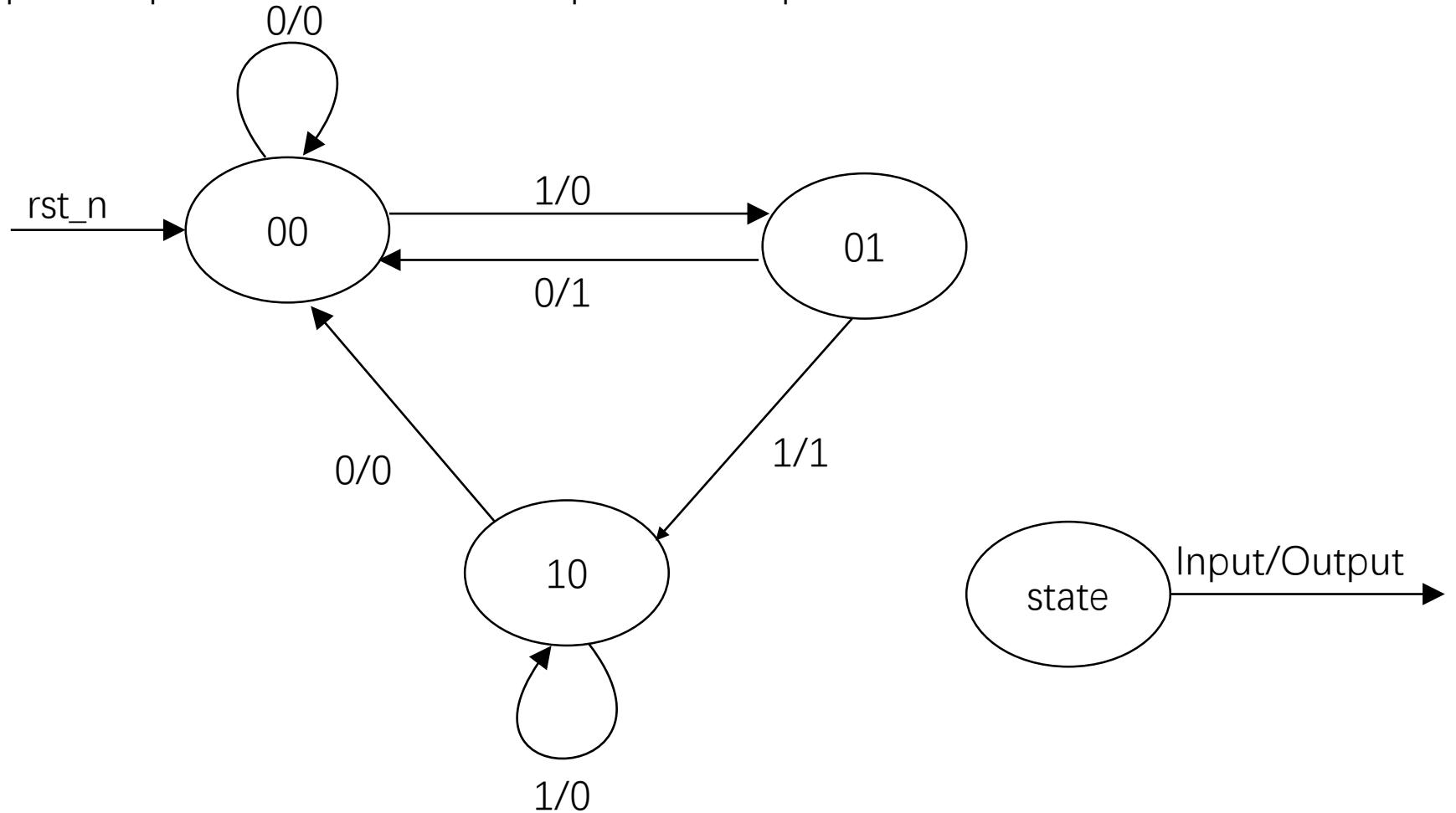


From a FSM to a Digital Circuit
&
Designing an Adder/Subtractor

Zhu Chen

The FSM Diagram


Function: Generate a positive pulse after the button is pushed. Keep 0 until the button is released and pushed again.



From FSM to Truth Table


- List the input, current state, next state and output
 - Empty states represented by X, will be useful later

Current State		Input	Next State		Output
S_1	S_0	I	S'_1	S'_0	Y
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	1
0	1	1	1	0	1
1	0	0	0	0	0
1	0	1	1	0	0
1	1	0	X	X	X
1	1	1	X	X	X

 


Represent the states

 - Represent a state by the output of several flip-flops
 - Store the state value
 - Can be changed at the rising edge of the clock



 - A D-Flip Flop
 - **Output = Input** at rising edge
 - \bar{Q} is the complement of Q
 - Set $S=R=0$ to use it as expected
 - If $S=R=1$, output will always be 0



Simplifying the logical representations

- Simplify the circuit with a Karnaugh Map
 - Useful for 3 to 4 input variables (e.g., your next experiment)
 - Hamming Distance of neighbor columns/rows = 1 (e.g., 01 and 11)
 - Group 1's and X's together (1x2, 2x1, 2x2, 1x4, 4x1, etc.) and simplify
- S_0S_1 are inputs of the 2 D-Flip flops, $S'_0S'_1$ are the outputs

$S_0 \backslash S_1 I$	00	01	11	10
0	0	0	1	0
1	0	1	X	X

Cancel S_1

Cancel S_0


$S_0 \backslash S_1 I$	00	01	11	10
0	0	1	0	0
1	0	0	X	X

Ignore redundant X

- $S'_0 = S_0I + S_1I = (S_0 + S_1)I, S'_1 = \overline{S_0} \overline{S_1}I, Y = \overline{S_0}S_1$




Connect the circuit

 - $S'_0 = S_0I + S_1I = (S_0 + S_1)I$, $S'_1 = \overline{S_0} \overline{S_1}I$, $Y = \overline{S_0}S_1$



Designing an Adder/Subtractor

   - An adder/subtractor is a circuit that is:
 - An adder when $S_0 = 0$
 - An subtractor when $S_0 = 1$
 - Required in ALU (top figure)
- Can be a cascade of 1-bit adders
- 1-bit adders(bottom figure):
 - Input: a, b, c_0 (carry of last adder)
 - Output: s, c_1 (sum and carry)
 - Design by truth table. $s = a \text{ xor } b \text{ xor } c$




Cascade of 1-bit adders into an adder

- Rather intuitive
- C_n to represent overflow


$$\begin{array}{r} a_3 a_0 \\ + b_3 b_0 \\ \hline s_3 s_0 \end{array}$$

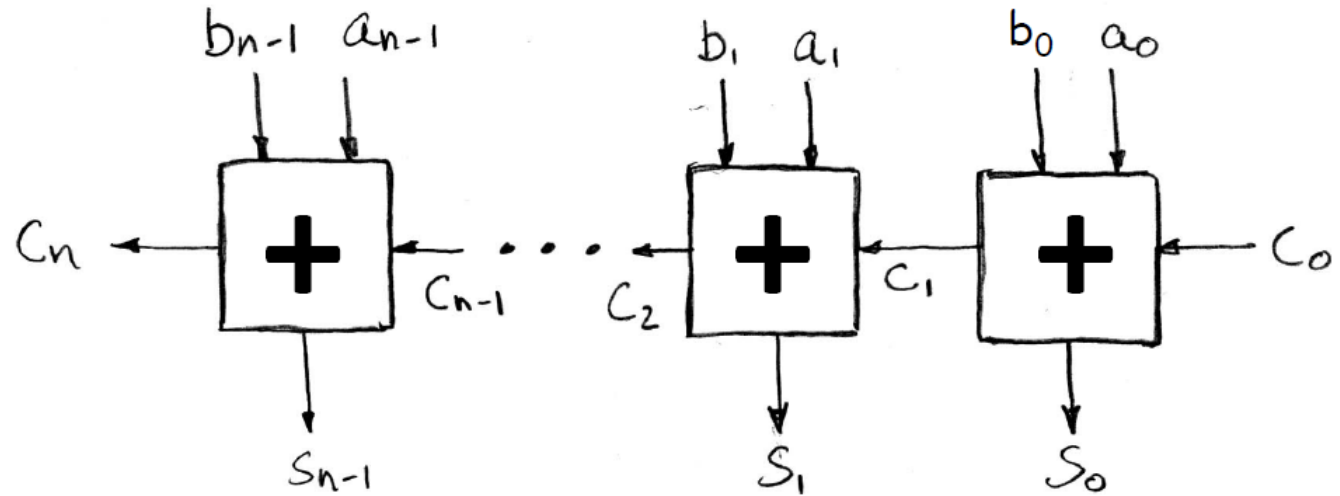(Note: In the original image, the a_1 , b_1 , and s_1 columns are enclosed in a box.)



Cascade of 1-bit adders into a subtractor

- How come?

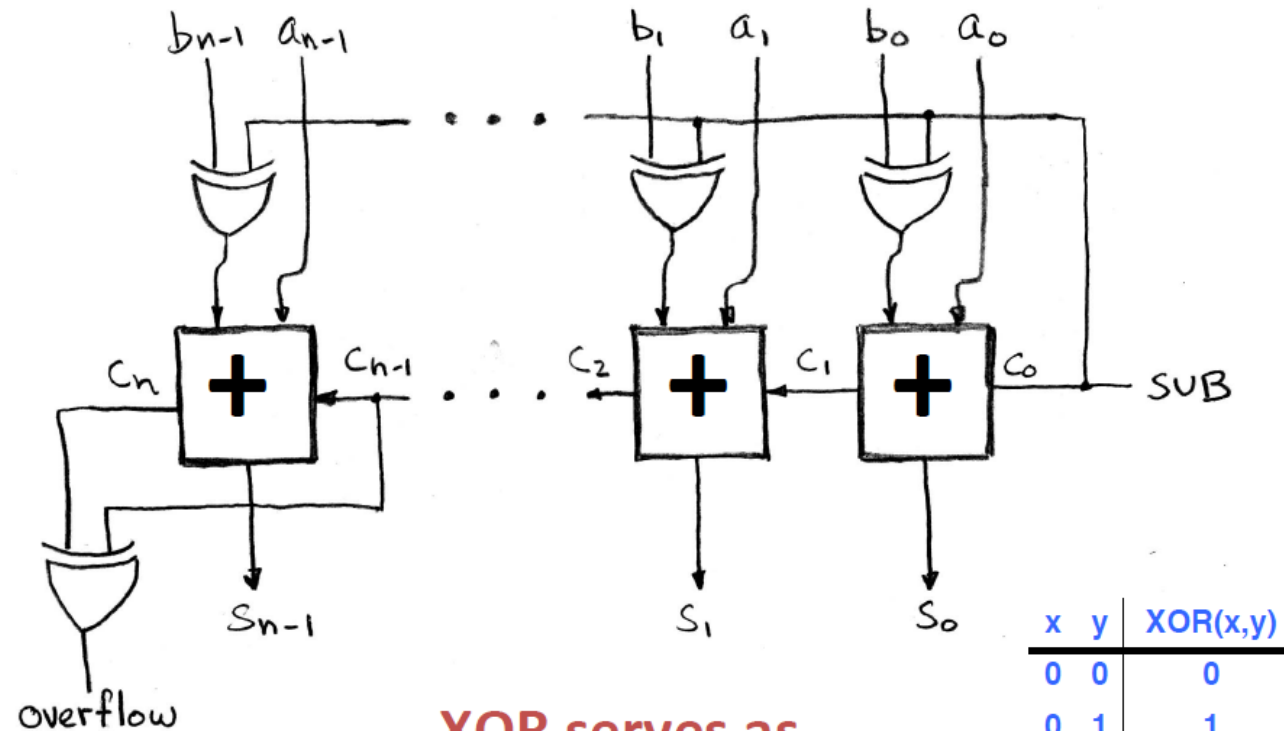


**XOR serves as
conditional inverter!**


x	y	XOR(x,y)
0	0	0
0	1	1
1	0	1
1	1	0

Cascade of 1-bit adders into a subtractor

- A, B are n -bit numbers with signs
- \tilde{A} is the 2's complement, \bar{A} is 1's complement
- Setting $SUB = 1$ to get \bar{B}
 - $b_i \text{ xor } SUB = b_i$ when $SUB = 0$
 - $b_i \text{ xor } SUB = \bar{b}_i$ when $SUB = 1$
- Subtract to addition: $A - B = A + \tilde{B}$
 - $-B = \tilde{B}$ considering only the lowest $(n-1)$ bits:
 $(-B)_{n-1} = (2^{n-1} + (-B))_{n-1} = (2^{n-1} - 1 - B) + 1$
 Where $(\cdot)_{n-1}$ represents taking the lowest $(n-1)$ bits

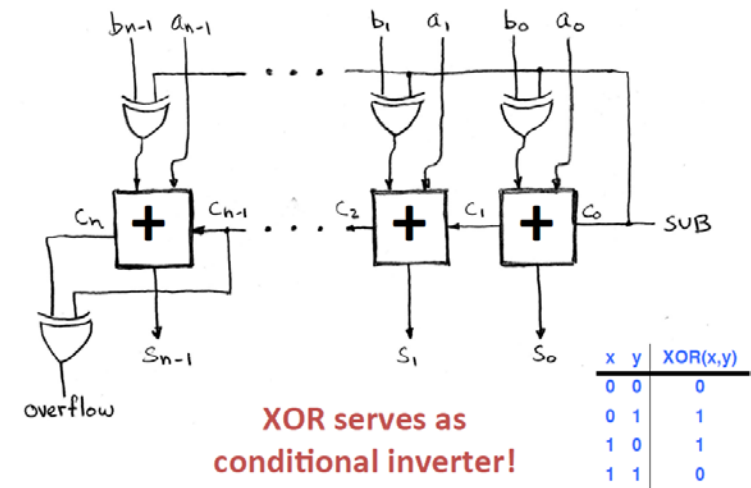

Overflow of n-bit adder

 

- Let A, B be the equivalent inputs to an n-bit adder
- If $A > 0, B > 0$
 - $a_{n-1} = b_{n-1} = 0 \Rightarrow c_n = 0$
 - If overflow, $c_{n-1} = 1$
- If $AB < 0$
 - Overflow won't happen since $|A + B| \leq |A|$

Overflow of n-bit adder

- If $A < 0, B < 0$, we actually add their complements \bar{A}, \bar{B}
 - $a_{n-1} = b_{n-1} = 1 \Rightarrow c_n = 1$
 - If overflow, $c_{n-1} = 0$ (a bit tricky here)
 - If $(A + B)_{n-1} = 2^{n-1}$, then $A + B = -2^n$, represented by $0b100 \dots 0$, not overflow
 - Overflows when $(A + B)_{n-1} > 2^{n-1}$
 $\Rightarrow 2^{n-1} - \tilde{A}_{n-1} + 2^{n-1} - \tilde{B}_{n-1} > 2^{n-1} \Rightarrow \tilde{A}_{n-1} + \tilde{B}_{n-1} < 2^{n-1} \Rightarrow c_{n-1} = 0$
- To sum up, the addition overflows if and only if $c_n \text{ xor } c_{n-1} = \text{true}$

The End