

CS 110
Computer Architecture
Lecture 8:
Synchronous Digital Systems

Instructor:
Sören Schwertfeger


<http://shtech.org/courses/ca/>

School of Information Science and Technology SIST

ShanghaiTech University

Slides based on UC Berkley's CS61C

Levels of Representation/Interpretation

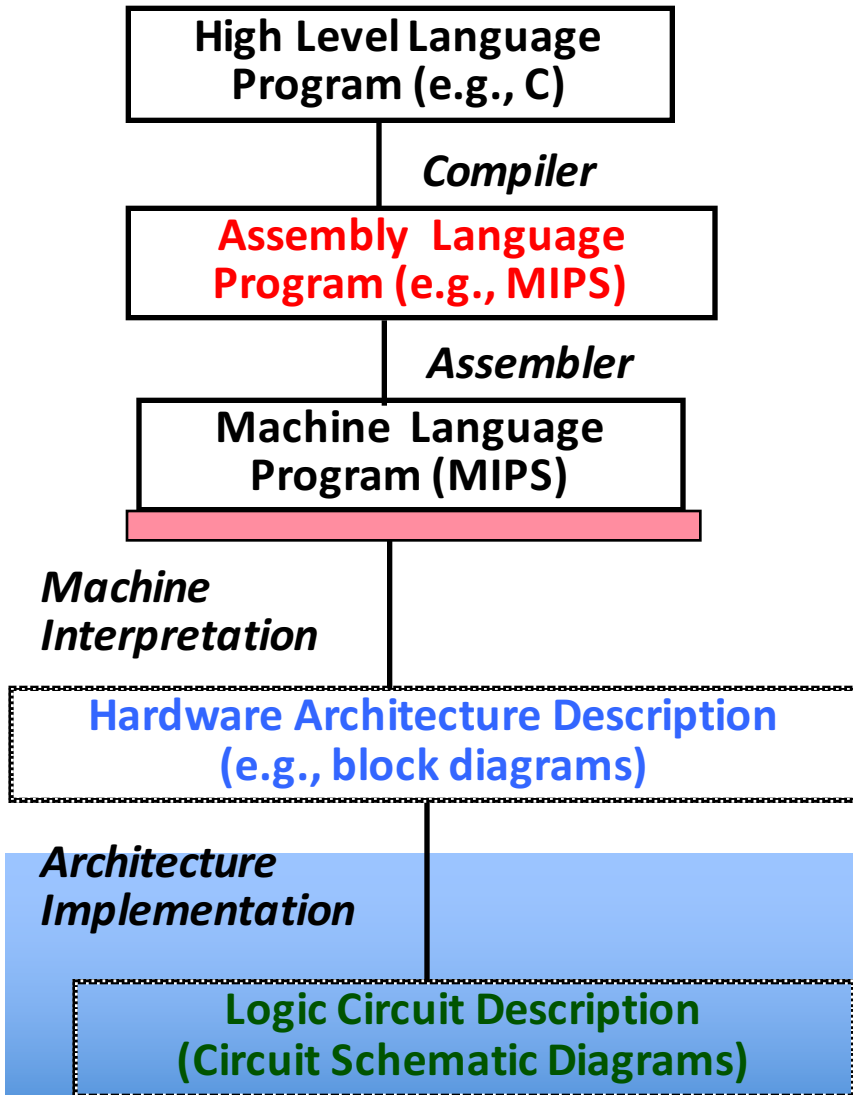


```
temp = v[k];
v[k] = v[k+1];
v[k+1] = temp;
```

```
lw $t0, 0($2)
lw $t1, 4($2)
sw $t1, 0($2)
sw $t0, 4($2)
```

Anything can be represented as a *number*, i.e., data or instructions
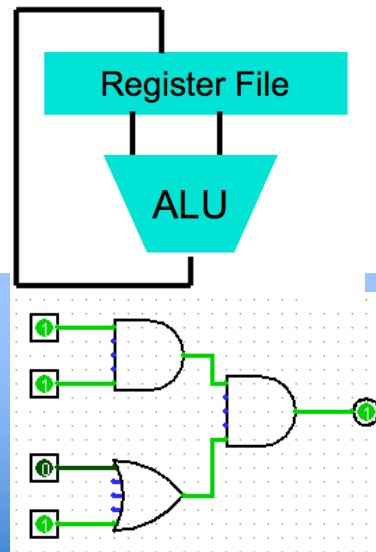
```
0000 1001 1100 0110 1010 1111 0101 1000
1010 1111 0101 1000 0000 1001 1100 0110
1100 0110 1010 1111 0101 1000 0000 1001
0101 1000 0000 1001 1100 0110 1010 1111
```



You are Here!

Software

Hardware




Warehouse Scale Computer

Smart Phone



Harness Parallelism & Achieve High Performance

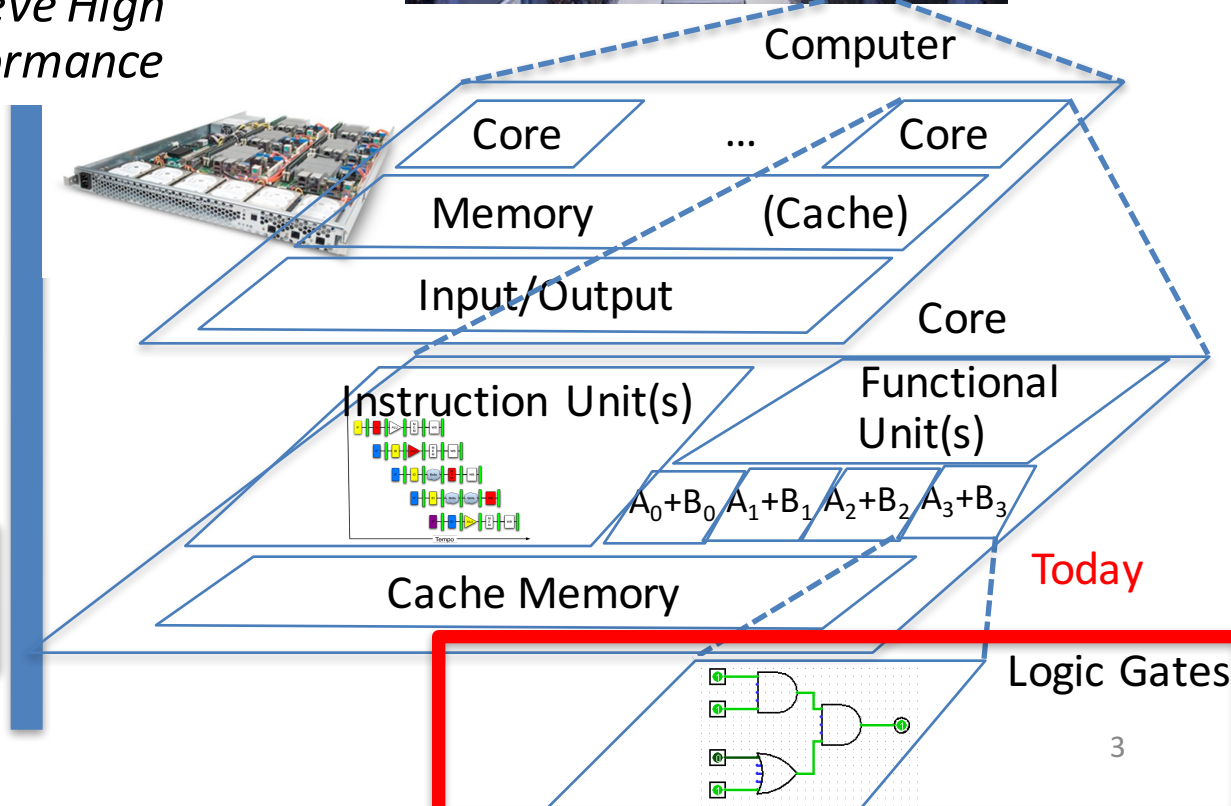- Parallel Requests
Assigned to computer
e.g., Search “Katz”
- Parallel Threads
Assigned to core
e.g., Lookup, Ads
- Parallel Instructions
>1 instruction @ one time
e.g., 5 pipelined instructions
- Parallel Data
>1 data item @ one time
e.g., Add of 4 pairs of words
- Hardware descriptions
All gates @ one time
- Programming Languages



Hardware Design

- Next several weeks: how a modern processor is built, starting with basic elements as building blocks
- Why study hardware design?
 - Understand capabilities and limitations of HW in general and processors in particular
 - What processors can do fast and what they can't do fast (avoid slow things if you want your code to run fast!)
 - Background for more in-depth HW courses
 - Hard to know what you'll need for next 30 years
 - There is only so much you can do with standard processors: you may need to design own custom HW for extra performance
 - Even some commercial processors today have customizable hardware!

Synchronous Digital Systems

Hardware of a processor, such as the MIPS, is an example of a Synchronous Digital System

Synchronous:


- All operations coordinated by a central clock
 - “Heartbeat” of the system!

Digital:


- Represent all values by discrete values
- Two binary digits: 1 and 0
- Electrical signals are treated as 1's and 0's
 - 1 and 0 are complements of each other
- High /low voltage for true / false, 1 / 0

Switches: Basic Element of Physical Implementations

 - Implementing a simple circuit (arrow shows action if wire changes to “1” or is *asserted*):



 On-switch (if A is “1” or asserted) turns-on light bulb (Z)




Off-switch (if A is “0” or unasserted) turns-off light bulb (Z)


$$Z \equiv A$$

Switches (cont'd)

 - Compose switches into more complex ones (Boolean functions):




$$Z \equiv A \text{ and } B$$

 

$$Z \equiv A \text{ or } B$$

Historical Note

 - Early computer designers built ad hoc circuits from switches
- Began to notice common patterns in their work: ANDs, ORs, ...
- Master's thesis (by Claude Shannon, 1940) made link between work and 19th Century Mathematician George Boole
 - Called it “Boolean” in his honor
- Could apply math to give theory to hardware design, minimization, ...




Transistors

- High voltage (V_{dd}) represents 1, or true
 - In modern microprocessors, $V_{dd} \sim 1.0$ Volt
- Low voltage (0 Volt or Ground) represents 0, or false
- Pick a midpoint voltage to decide if a 0 or a 1
 - Voltage greater than midpoint = 1
 - Voltage less than midpoint = 0
 - This removes noise as signals propagate – a big advantage of digital systems over analog systems
- If one switch can control another switch, we can build a computer!
- Our switches: CMOS transistors


CMOS Transistor Networks

- Modern digital systems designed in CMOS
 - MOS: Metal-Oxide on Semiconductor
 - C for complementary: use *pairs* of normally-*on* and normally-*off* switches
- CMOS transistors act as voltage-controlled switches
 - Similar, though easier to work with, than electro-mechanical relay switches from earlier era
 - Use energy primarily when switching

CMOS Transistors

 

 - Three terminals: source, gate, and drain
 - Switch action:
if voltage on gate terminal is (some amount) higher/lower than source terminal then conducting path established between drain and source terminals (switch is closed)




n-channel transistor

off when voltage at Gate is low

on when:

voltage(Gate) > voltage (Threshold)

 

p-channel transistor

on when voltage at Gate is low

off when:


voltage(Gate) > voltage (Threshold)

field-effect transistor (FET) => CMOS circuits use a combination of p-type and n-type metal-oxide-semiconductor field-effect transistors =>

MOSFET


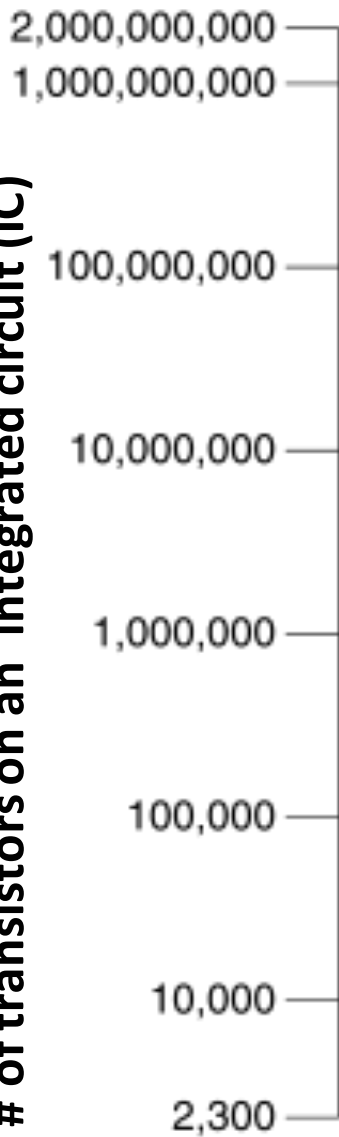
#2: Moore's Law

of transistors on an integrated circuit (IC)




Predicts:
2X Transistors / chip
every 2 years

 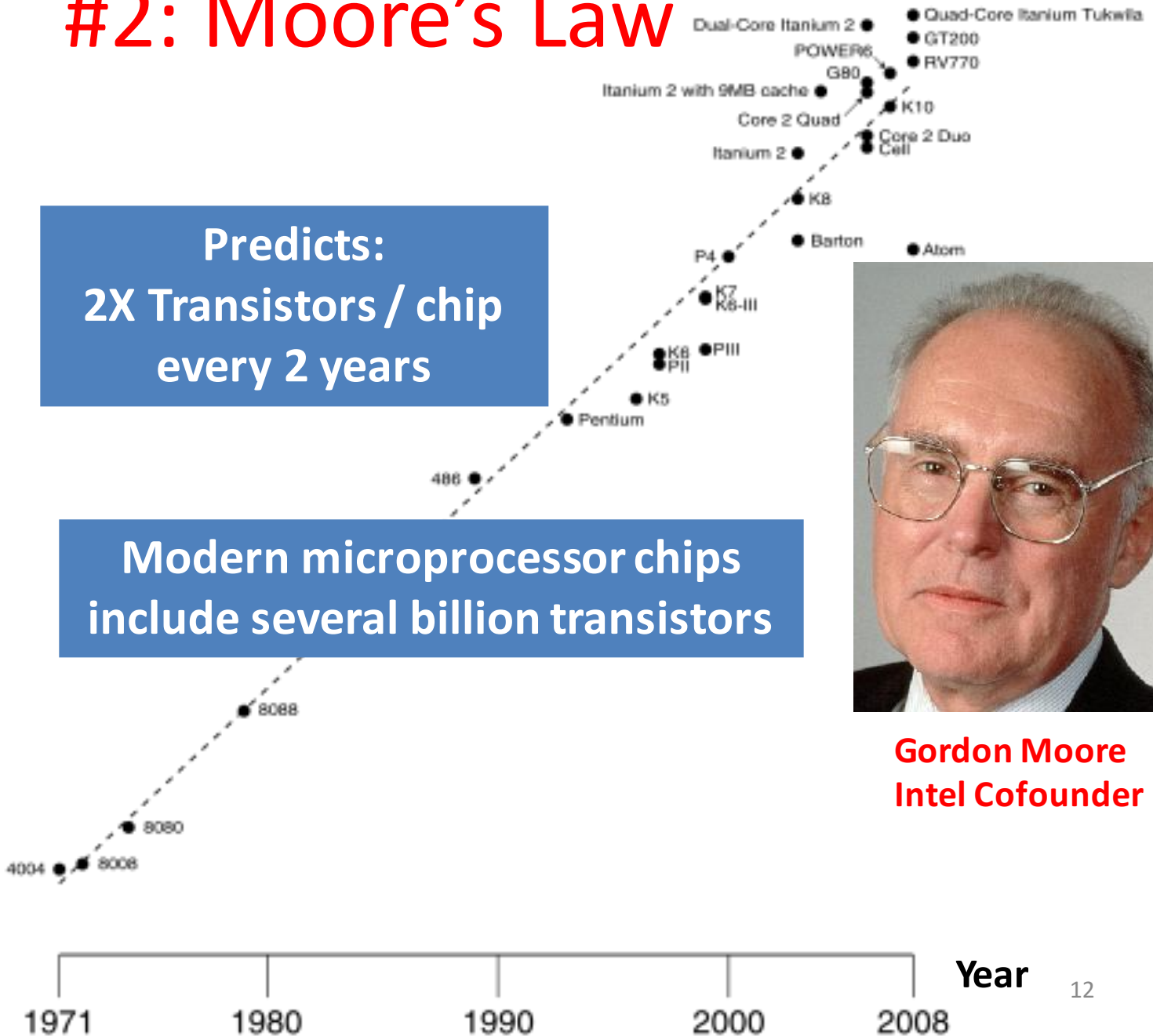Modern microprocessor chips
include several billion transistors




Gordon Moore
Intel Cofounder

Intel 14nm Technology

 

Plan view of transistors

 

Side view of wiring layers


Sense of Scale



Mark
1.66 m



Fly
7 mm

 


Mite
300 μm




Blood Cell
7 μm



Virus
100 nm

 

Silicon Atom
0.24 nm

 

meter	millimeter	micrometer	nanometer
-------	------------	------------	-----------

Source: Mark Bohr, IDF14

CMOS Circuit Rules

- Don't pass weak values => Use Complementary Pairs
 - N-type transistors pass weak 1's ($V_{dd} - V_{th}$)
 - N-type transistors pass strong 0's (ground)
 - Use N-type transistors only to pass 0's (N for negative)
 - Converse for P-type transistors: Pass weak 0s, strong 1s
 - Pass weak 0's (V_{th}), strong 1's (V_{dd})
 - Use P-type transistors only to pass 1's (P for positive)
 - Use pairs of N-type and P-type to get strong values
- Never leave a wire undriven
 - Make sure there's always a path to V_{dd} or GND
- Never create a path from V_{dd} to GND (ground)
 - This would short-circuit the power supply!


CMOS Networks

p-channel transistor

on when voltage at Gate is low

off when:

voltage(Gate) > voltage (Threshold)

 

n-channel transistor

off when voltage at Gate is low

on when:


voltage(Gate) > voltage (Threshold)

what is the relationship between x and y?

x	y
0 Volt (GND)	1 Volt (Vdd)
1 Volt (Vdd)	0 Volt (GND)

Called an *inverter* or *not gate*

Two-Input Networks

 


what is the relationship between x, y and z?

x	y	z
0 Volt	0 Volt	1 Volt
0 Volt	1 Volt	1 Volt
1 Volt	0 Volt	1 Volt
1 Volt	1 Volt	0 Volt

Called a *NAND gate*
(*NOT AND*)

Clickers/Peer Instruction

 

x	y	z				
		A	B	C	D	
0 Volt	0 Volt	0	0	1	1	Volts
0 Volt	1 Volt	0	1	0	1	Volts
1 Volt	0 Volt	0	1	0	1	Volts
1 Volt	1 Volt	1	1	0	0	Volts

Administrivia

- Final HW1 scores will be published next week:
 - We will by hand take a quick look and deduct points for bugs, e.g.
 - Memory leaks
 - reverse_list changing the provided list
 - Empty or meaningless comments
- Project 1.1 test cases will be updated latest Monday – grading similar to above
 - 11 groups did not register their group e-mail yet!
 - 8 groups have registrations pending in gradebot!

Administrivia

- Bug in HW3 grading script ...
- In Lab 8:
 - Your project team explains the TA and Prof your projects 1.1 and 1.2
 - Both of you should know your software well
 - If we find one of you clearly did contribute much less, we will reduce that students points a little
- Check out the additional material provided by UC Berkeley:
 - <http://inst.eecs.berkeley.edu/~cs61c/resources/sds.pdf>
 - <http://inst.eecs.berkeley.edu/~cs61c/resources/boolean.pdf>


Policy on Assignments and Independent Work

- **ALL PROJECTS WILL BE DONE WITH A PARTNER**
- With the exception of laboratories and assignments that explicitly permit you to work in groups, all homework and projects are to be YOUR work and your work ALONE.
- PARTNER TEAMS MAY NOT WORK WITH OTHER PARTNER TEAMS
- You are encouraged to discuss your assignments with other students, and credit will be assigned to students who help others, particularly by answering questions on Piazza, but we expect that what you hand in is yours.
- It is NOT acceptable to copy solutions from other students.
- It is NOT acceptable to copy (or start your) solutions from the Web.
- **It is NOT acceptable to use PUBLIC github archives (giving your answers away)**
- We have tools and methods, developed over many years, for detecting this. You WILL be caught, and the penalties WILL be severe.
- **At the minimum F in the course**, and a letter to your university record documenting the incidence of cheating.
- **Both Giver and Receiver are equally culpable and suffer equal penalties**

Combinational Logic Symbols

- Common combinational logic systems have standard symbols called logic gates


– Buffer, NOT

 

– AND, NAND



– OR, NOR

 

Inverting versions (NOT, NAND, NOR) easiest to implement with CMOS transistors (the switches we have available and use most)

Remember...

- AND

- OR

Boolean Algebra

- Use plus “+” for OR
 - “logical sum” $1+0 = 0+1 = 1$ (True); $1+1=2$ (True); $0+0 = 0$ (False)
- Use product for AND ($a \bullet b$ or implied via ab)
 - “logical product” $0*0 = 0*1 = 1*0 = 0$ (False); $1*1 = 1$ (True)
- “Hat” to mean complement (NOT)

• Thus


$$ab + a + \bar{c}$$

$$= a \bullet b + a + \bar{c}$$

$$= (a \text{ AND } b) \text{ OR } a \text{ OR } (\text{NOT } c)$$



Truth Tables for Combinational Logic

 

Exhaustive list of the output value
generated for each combination of inputs

How many logic functions can be defined
with N inputs?

a	b	c	d	y
0	0	0	0	F(0,0,0,0)
0	0	0	1	F(0,0,0,1)
0	0	1	0	F(0,0,1,0)
0	0	1	1	F(0,0,1,1)
0	1	0	0	F(0,1,0,0)
0	1	0	1	F(0,1,0,1)
0	1	1	0	F(0,1,1,0)
0	1	1	1	F(0,1,1,1)
1	0	0	0	F(1,0,0,0)
1	0	0	1	F(1,0,0,1)
1	0	1	0	F(1,0,1,0)
1	0	1	1	F(1,0,1,1)
1	1	0	0	F(1,1,0,0)
1	1	0	1	F(1,1,0,1)
1	1	1	0	F(1,1,1,0)
1	1	1	1	F(1,1,1,1)

Truth Table Example #1:

$y = F(a,b): 1 \text{ iff } a \neq b$

a	b	y
0	0	0
0	1	1
1	0	1
1	1	0

Truth Table Example #3: 32-bit Unsigned Adder

A	B	C
000 ... 0	000 ... 0	000 ... 00
000 ... 0	000 ... 1	000 ... 01
.	.	.
.	.	.
.	.	.
111 ... 1	111 ... 1	111 ... 10

How
Many
Rows?

Truth Table Example #4: 3-input Majority Circuit


$Y =$

This is called *Sum of Products* form;
Just another way to represent the TT
as a logical expression

More simplified forms
(fewer gates and wires)

a	b	c	y
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

 Boolean Algebra: Circuit & Algebraic Simplification




original circuit

$$y = ((ab) + a) + c$$

equation derived from original circuit


$$\begin{aligned} &\downarrow \\ &= ab + a + c \\ &\downarrow \\ &= a(b + 1) + c \\ &= a(1) + c \\ &= a + c \end{aligned}$$

algebraic simplification

 

simplified circuit

 Representations of Combinational Logic (groups of logic gates)



Laws of Boolean Algebra

$$X \bar{X} = 0$$

$$X 0 = 0$$

$$X 1 = X$$

$$X X = X$$

$$X Y = Y X$$

$$(X Y) Z = Z (Y Z)$$

$$X (Y + Z) = X Y + X Z$$

$$X Y + X = X$$

$$\bar{X} Y + X = X + Y$$

$$\overline{X Y} = \bar{X} + \bar{Y}$$

$$X + \bar{X} = 1$$

$$X + 1 = 1$$

$$X + 0 = X$$

$$X + X = X$$

$$X + Y = Y + X$$

$$(X + Y) + Z = Z + (Y + Z)$$

$$X + Y Z = (X + Y) (X + Z)$$

$$(X + Y) X = X$$

$$(\bar{X} + Y) X = X Y$$

$$\overline{X + Y} = \bar{X} \bar{Y}$$

Complementarity

Laws of 0's and 1's

Identities

Idempotent Laws

Commutativity

Associativity

Distribution

Uniting Theorem

Uniting Theorem v. 2

DeMorgan's Law

Boolean Algebraic Simplification Example

$$y = ab + a + c$$

Boolean Algebraic Simplification

Example

$$y = ab + a + c$$

$$a \ b \ c \ y = a(b + 1) + c \quad \textit{distribution, identity}$$

$$0 \ 0 \ 0 \ 0 = a(1) + c \quad \textit{law of 1's}$$

$$0 \ 0 \ 1 \ 1 = a + c \quad \textit{identity}$$

$$0 \ 1 \ 0 \ 0$$

$$0 \ 1 \ 1 \ 1$$

$$1 \ 0 \ 0 \ 1$$

$$1 \ 0 \ 1 \ 1$$

$$1 \ 1 \ 0 \ 1$$


$$1 \ 1 \ 1 \ 1$$

Question



- Simplify $Z = A + BC + \overline{A}(\overline{BC})$
- A: $Z = 0$
- B: $Z = \overline{A(1 + BC)}$
- C: $Z = (A + BC)$
- D: $Z = BC$
- E: $Z = 1$

In the News: Googles AlphaGo beats world champion Lee Sedol

 
- Google wins 4:1
- Go: maybe 200 possible moves per turn
 - 250 or more turns
 - even 200^{150} is about infinite (chess: about 35^{80})
- Monte Carlo Tree Search (MCTS) and Machine Learning (Neural Networks)
- 1202 CPUs und 176 GPU (or more)
- One million USD prize




Signals and Waveforms

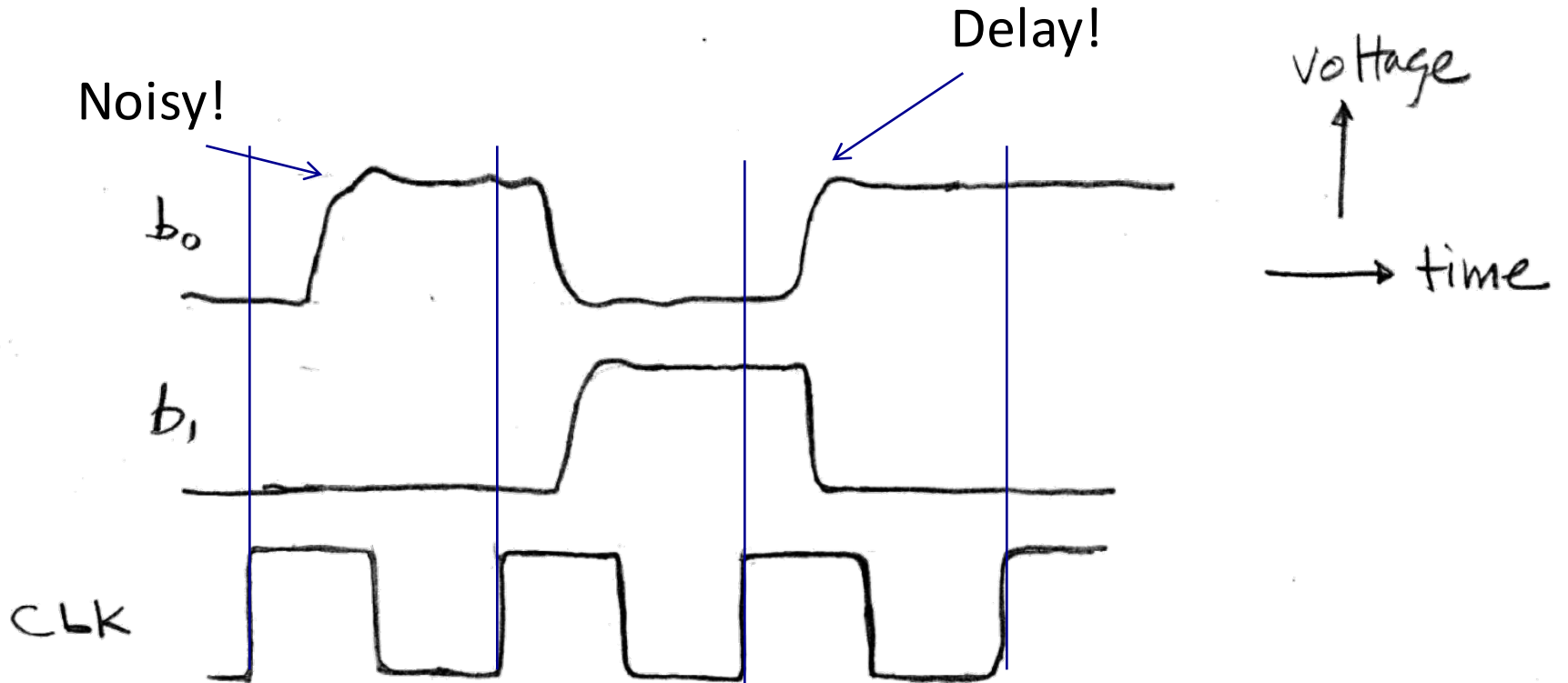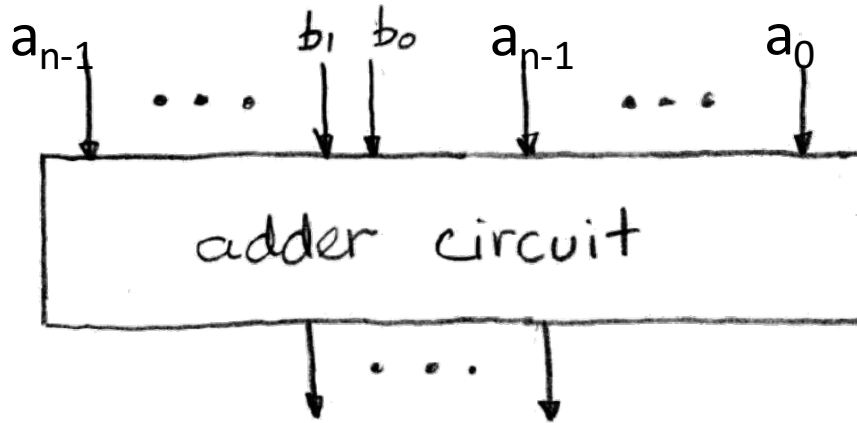

Signals and Waveforms: Grouping


 


Signals and Waveforms: Circuit Delay

 


$$A = [a_3, a_2, a_1, a_0]$$

$$B = [b_3, b_2, b_1, b_0]$$

  

Sample Debugging Waveform

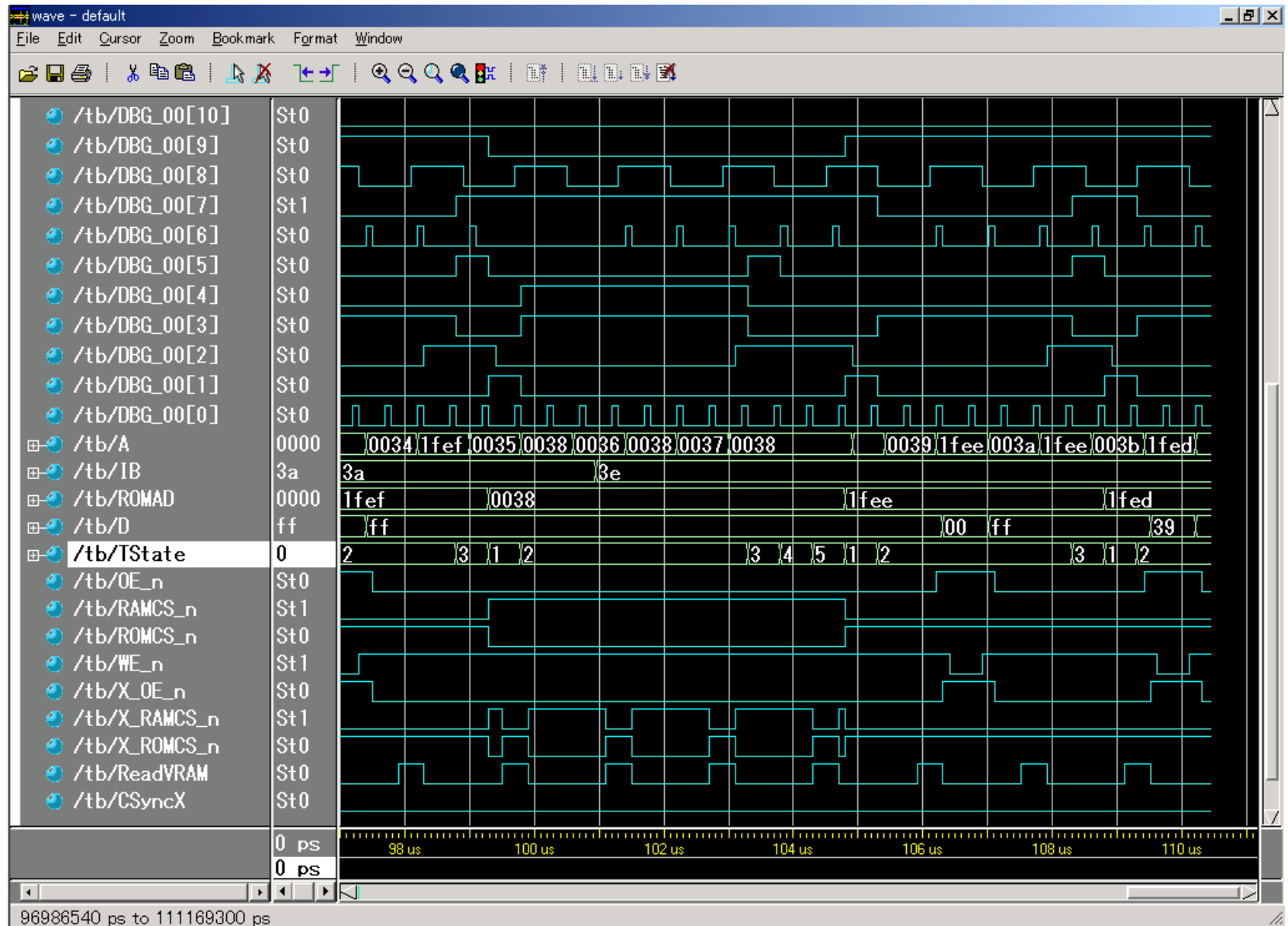

Type of Circuits


- *Synchronous Digital Systems* consist of two basic types of circuits:
 - Combinational Logic (CL) circuits
 - Output is a function of the inputs only, not the history of its execution
 - E.g., circuits to add A, B (ALUs)
 - Sequential Logic (SL)
 - Circuits that “remember” or store information
 - aka “State Elements”
 - E.g., memories and registers (Registers)

Uses for State Elements

- Place to store values for later re-use:
 - Register files (like \$1-\$31 in MIPS)
 - Memory (caches and main memory)
- *Help control flow of information between combinational logic blocks*
 - State elements hold up the movement of information at input to combinational logic blocks to allow for orderly passage

Accumulator Example

 Why do we need to control the flow of information?



Want:

```
S=0;
```


```
for (i=0; i<n; i++)
```

```
    S = S + Xi
```

Assume:

- Each X value is applied in succession, one per cycle
- After n cycles the sum is present on S

First Try: Does this work?

 


No!

Reason #1: How to control the next iteration of the 'for' loop?

Reason #2: How do we say: 'S=0'?


Second Try: How About This?

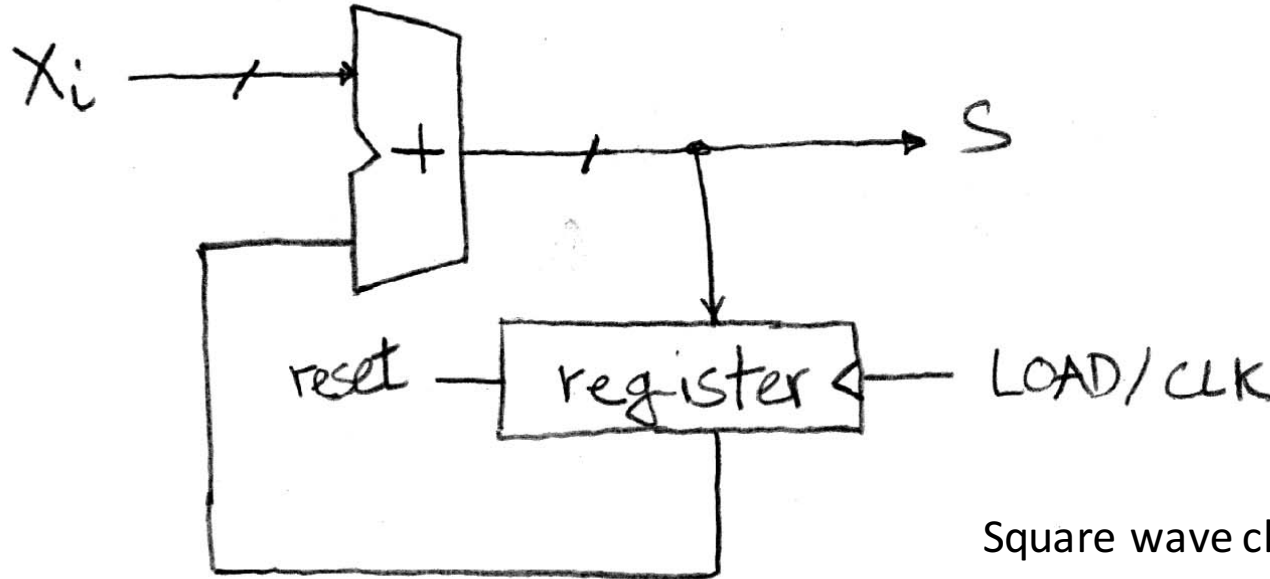


Register is used to hold up the transfer of data to adder

Square wave clock sets when things change

Rough timing ...

 


Second Try: How About This?

 


Register is used to hold up the transfer of data to adder

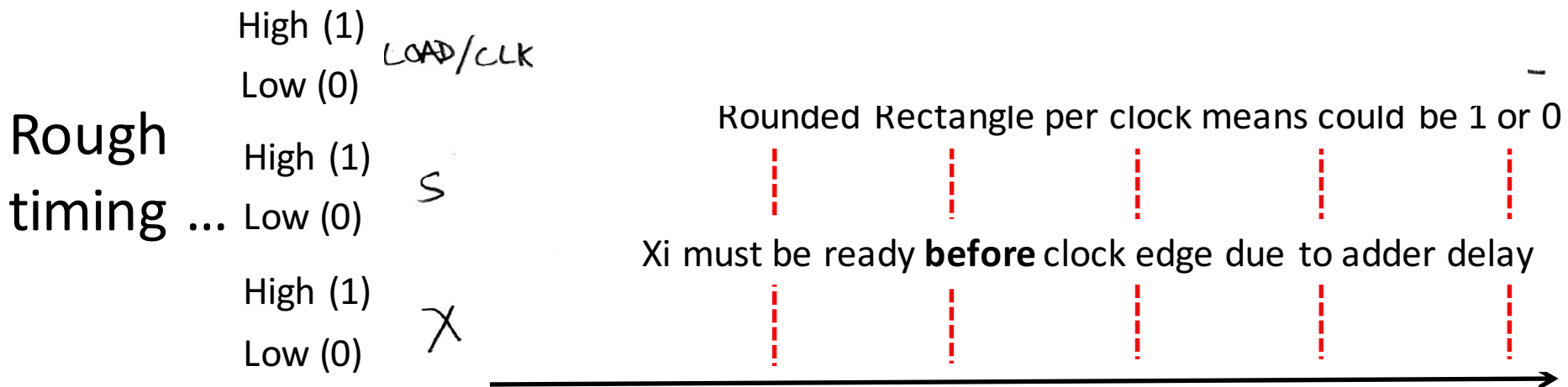Square wave clock sets when things change



Model for Synchronous Systems

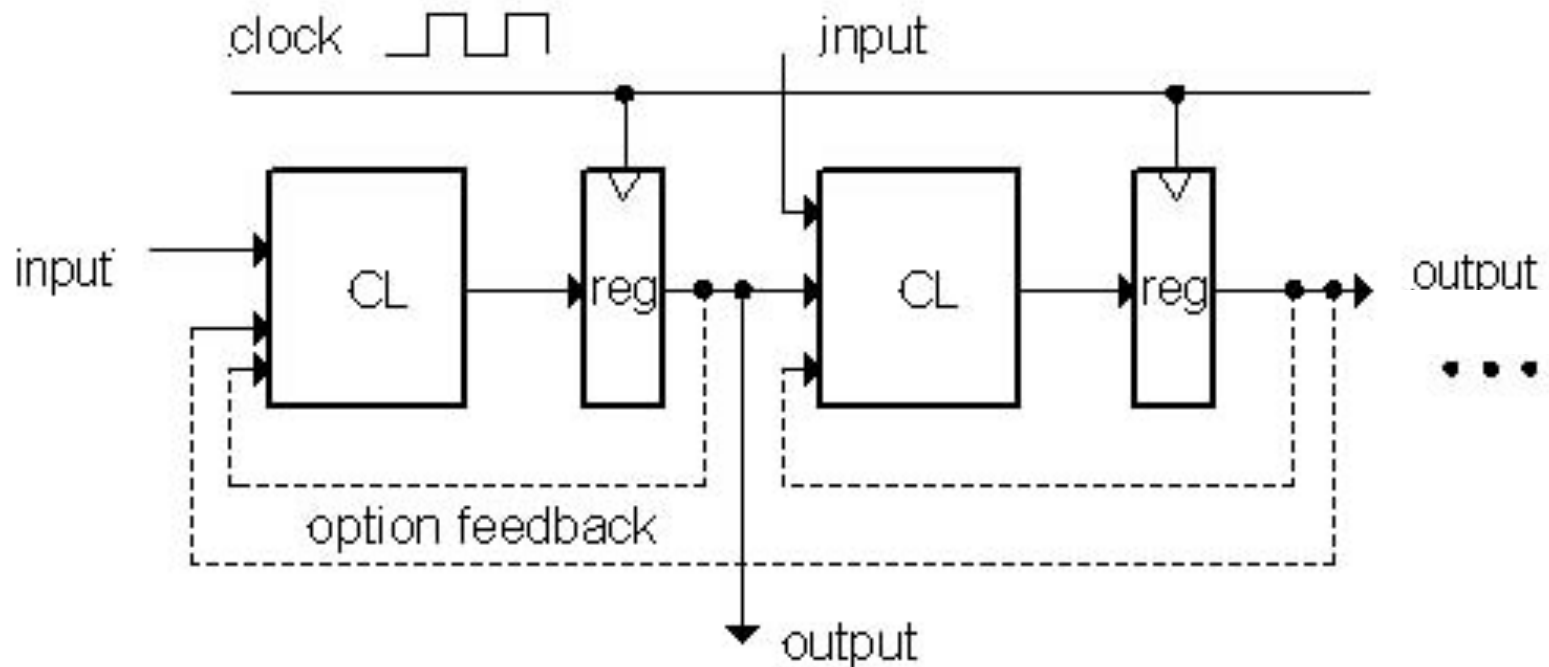

- Collection of Combinational Logic blocks separated by registers
- Feedback is optional
- Clock signal(s) connects only to clock input of registers
- Clock (CLK): steady square wave that synchronizes the system
- Register: several bits of state that samples on rising edge of CLK (positive edge-triggered) or falling edge (negative edge-triggered)