

Name (Pinyin):

Email:

# ShanghaiTech University, Computer Architecture I 2017, HW 5

---

<http://shitech.org/course/ca/17s/>

**Submission Information** Create a pdf (with whichever program you prefer) called *hw5.pdf* and commit and push it to gradebot.

## Question 1 FSM and Truth Tables

---


You have been enlisted to design a gacha machine. The machine accepts three kinds of tokens, bronze token for 1 point, silver token for 2 points and gold token for 4 points. When 4 points have been inserted, it dispenses the gacha, and the dispenser will keep the remaining points. Design an FSM controller for the gacha machine.

### 1. Implement the FSM diagram.

**Requirements:**

1. The FSM states and inputs are 2-bits each, while the outputs are 1-bit.
2. On each cycle, exactly one token is inserted.
3. For inputs,
  - "01" -> bronze token.
  - "10" -> silver token.
  - "11" -> gold token.
  - "00" is not existed in the input.

Example of the FSM diagram:

 

**ANS:**

**2. Represent the truth table of the FSM and use the MOST simplified SOP (Sum of Product) Expression to represent the output with state and input.**

You should represent the two bit of the states individually. So as the inputs.  
The result should be

Hint: Use Karnaugh map.

**ANS:**

1. Truth table

2. Expression

## Question 2 Boolean Algebra

---

Simplify the following expressions.

1.  $A \cdot \overline{B} + \overline{B} \cdot A + C \cdot D \cdot E + \overline{C} \cdot D \cdot E + E \cdot \overline{C} \cdot D$

2.  $(A \cdot B)(L \cdot N \cdot M)(C \cdot D \cdot E)(M \cdot N \cdot L)$

3.  $A \cdot (B + C) + D \cdot E + W \cdot \overline{X} + E \cdot D + \overline{X} \cdot W + (C + B) \cdot A$

4.  $T \cdot (P \cdot Q + R + S \cdot T) \cdot S$

5.  $\overline{\overline{DDE}}$

ANS:

1.

2.

3.

4.

5.

## Question 3 Timing Diagram

---

Consider the circuit shown below. The input is x and output is y. A clock signal is connected to each flip-flop and has a period of 6 ns. The xor gate and the inverter each have a propagation delay of 1ns. Flip-flops are positive edge-triggered and have a set-up time and clock-to-q delay of 1ns each.

