

CS 110
Computer Architecture
Lecture 10:
Datapath

Instructor:
Sören Schwertfeger

<http://shtech.org/courses/ca/>

School of Information Science and Technology SIST


ShanghaiTech University

Slides based on UC Berkley's CS61C

Review

- Timing constraints for Finite State Machines
 - Setup time, Hold Time, Clock to Q time
- Use muxes to select among inputs
 - S control bits selects from 2^S inputs
 - Each input can be n-bits wide, indep of S
 - Can implement muxes hierarchically
- ALU can be implemented using a mux
 - Coupled with basic block elements
 - Adder/ Subtractor & AND & OR & shift

Components of a Computer

 


The CPU

- Processor (CPU): the active part of the computer that does all the work (data manipulation and decision-making)
- Datapath: portion of the processor that contains hardware necessary to perform operations required by the processor (the brawn)
- Control: portion of the processor (also in hardware) that tells the datapath what needs to be done (the brain)

Datapath and Control

 
- Datapath designed to support data transfers required by instructions
- Controller causes correct transfers to happen



Five Stages of Instruction Execution

- Stage 1: Instruction Fetch
- Stage 2: Instruction Decode
- Stage 3: ALU (Arithmetic-Logic Unit)
- Stage 4: Memory Access
- Stage 5: Register Write

Stages of Execution on Datapath

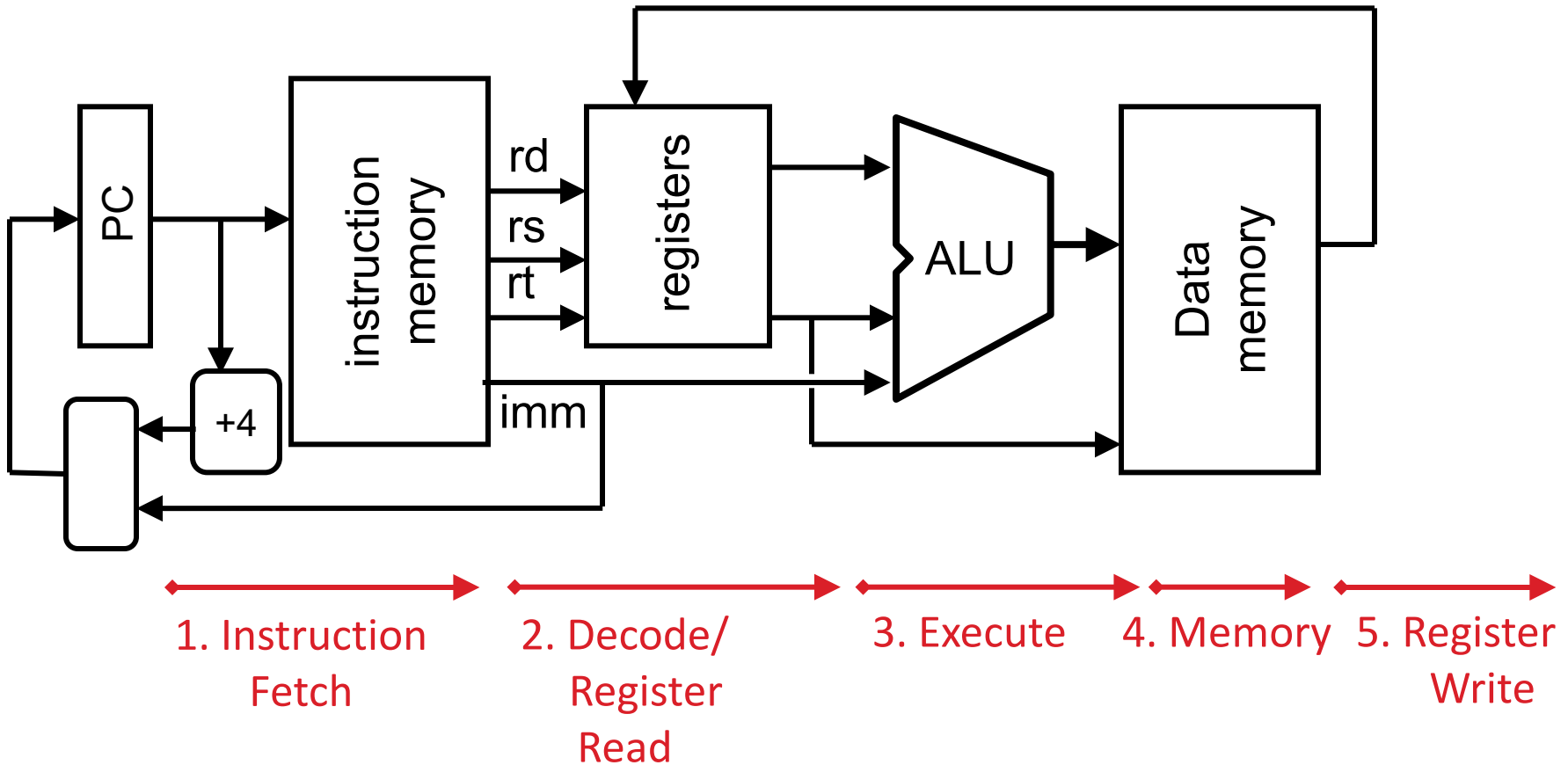

Stages of Execution (1/5)

- There is a wide variety of MIPS instructions: so what general steps do they have in common?
- Stage 1: Instruction Fetch
 - no matter what the instruction, the 32-bit instruction word must first be fetched from memory (the cache-memory hierarchy)
 - also, this is where we Increment PC (that is, $PC = PC + 4$, to point to the next instruction: byte addressing so + 4)

Stages of Execution (2/5)

- Stage 2: Instruction Decode
 - upon fetching the instruction, we next gather data from the fields (decode all necessary instruction data)
 - first, read the opcode to determine instruction type and field lengths
 - second, read in data from all necessary registers
 - for add, read two registers
 - for addi, read one register
 - for jal, no reads necessary

Stages of Execution (3/5)

- Stage 3: ALU (Arithmetic-Logic Unit)
 - the real work of most instructions is done here: arithmetic (+, -, *, /), shifting, logic (&, |), comparisons (slt)
 - what about loads and stores?
 - lw \$t0, 40(\$t1)
 - the address we are accessing in memory = the value in \$t1 PLUS the value 40
 - so we do this addition in this stage


Stages of Execution (4/5)

- Stage 4: Memory Access
 - actually only the load and store instructions do anything during this stage; the others remain idle during this stage or skip it all together
 - since these instructions have a unique step, we need this extra stage to account for them
 - as a result of the cache system, this stage is expected to be fast

Stages of Execution (5/5)

- Stage 5: Register Write
 - most instructions write the result of some computation into a register
 - examples: arithmetic, logical, shifts, loads, slt
 - what about stores, branches, jumps?
 - don't write anything into a register at the end
 - these remain idle during this fifth stage or skip it all together


Stages of Execution on Datapath

 

Datapath Walkthroughs (1/3)

- add \$r3,\$r1,\$r2 # r3 = r1+r2
 - Stage 1: fetch this instruction, increment PC
 - Stage 2: decode to determine it is an add, then read registers \$r1 and \$r2
 - Stage 3: add the two values retrieved in Stage 2
 - Stage 4: idle (nothing to write to memory)
 - Stage 5: write result of Stage 3 into register \$r3


Example: add Instruction

 

Datapath Walkthroughs (2/3)

- `slti $r3,$r1,17`
if (r1 <17) r3 = 1 else r3 = 0
 - Stage 1: fetch this instruction, increment PC
 - Stage 2: decode to determine it is an `slti`, then read register `$r1`
 - Stage 3: compare value retrieved in Stage 2 with the integer 17
 - Stage 4: idle
 - Stage 5: write the result of Stage 3 (1 if reg source was less than signed immediate, 0 otherwise) into register `$r3`


Example: slti Instruction

 

Datapath Walkthroughs (3/3)

- `sw $r3,17($r1) # Mem[r1+17]=r3`
 - Stage 1: fetch this instruction, increment PC
 - Stage 2: decode to determine it is a sw, then read registers \$r1 and \$r3
 - Stage 3: add 17 to value in register \$r1 (retrieved in Stage 2) to compute address
 - Stage 4: write value in register \$r3 (retrieved in Stage 2) into memory address computed in Stage 3
 - Stage 5: idle (nothing to write into a register)

Example: sw Instruction

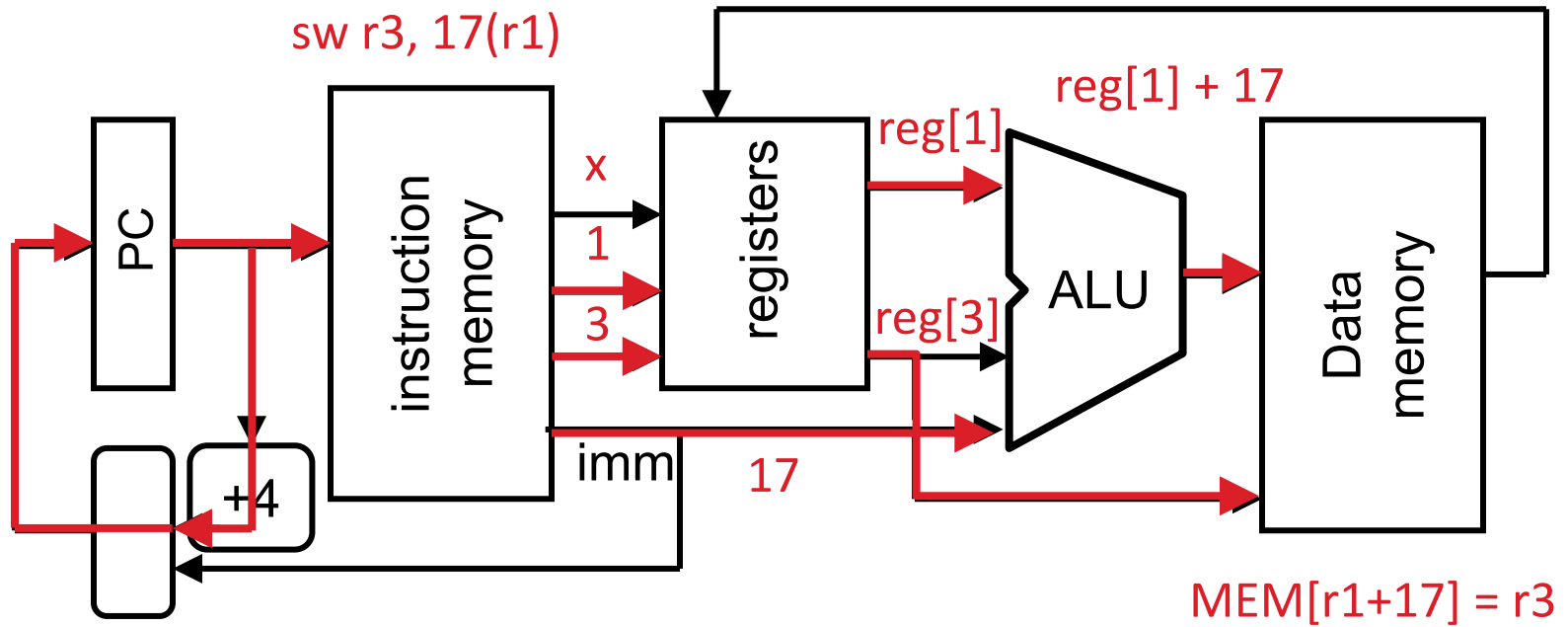


Why Five Stages? (1/2)

- Could we have a different number of stages?
 - Yes, other ISAs have different natural number of stages
- Why does MIPS have five if instructions tend to idle for at least one stage?
 - Five stages are the union of all the operations needed by all the instructions.
 - One instruction uses all five stages: the load

Why Five Stages? (2/2)

- `lw $r3,17($r1) # r3=Mem[r1+17]`
 - Stage 1: fetch this instruction, increment PC
 - Stage 2: decode to determine it is a `lw`, then read register `$r1`
 - Stage 3: add 17 to value in register `$r1` (retrieved in Stage 2)
 - Stage 4: read value from memory address computed in Stage 3
 - Stage 5: write value read in Stage 4 into register `$r3`

Example: lw Instruction

 

Question

- Which type of MIPS instruction is active in the fewest stages?

A: LW

B: BEQ


C: J

D: JAL

E: ADDU

Datapath and Control

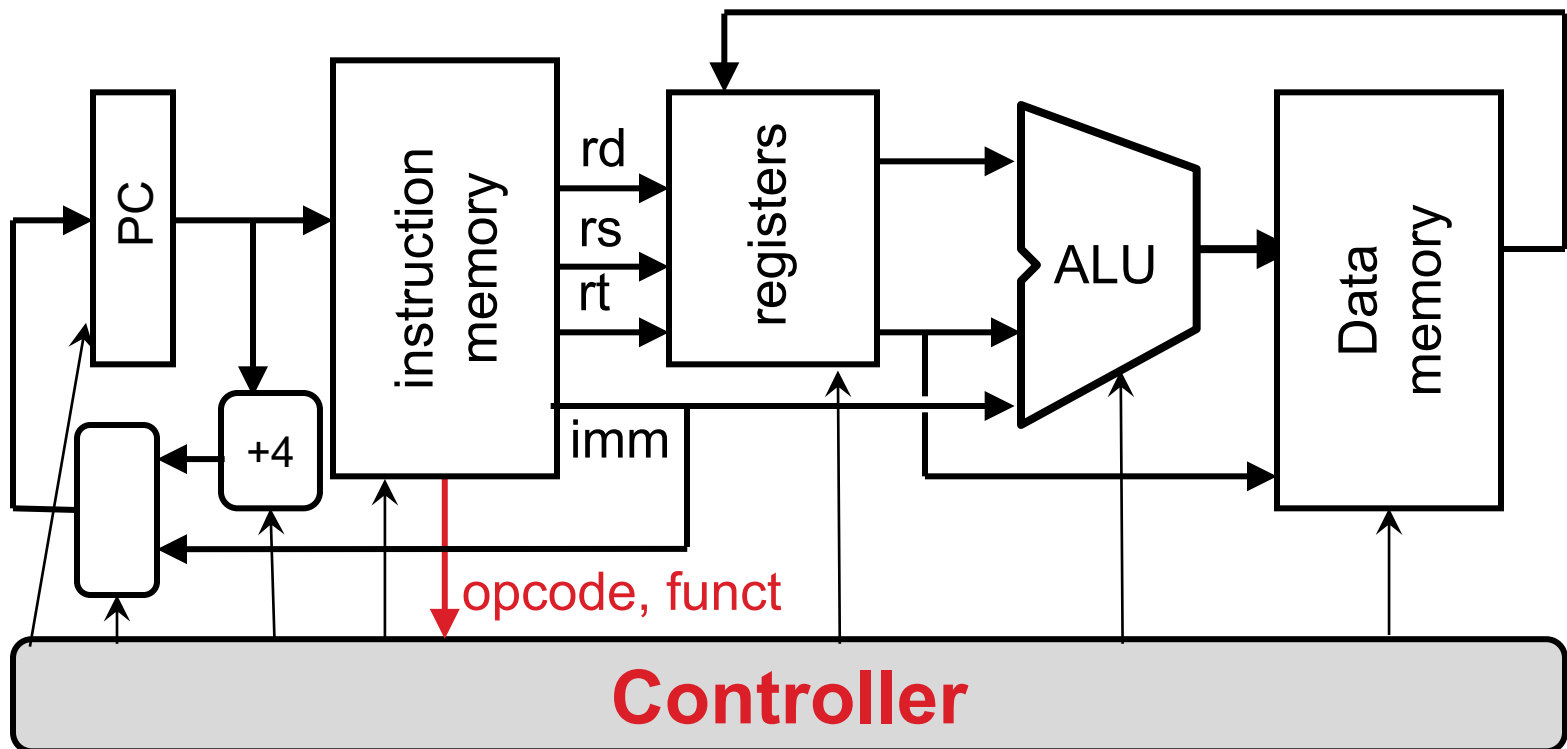- Datapath designed to support data transfers required by instructions
- Controller causes correct transfers to happen



Processor Design: 5 steps

Step 1: Analyze instruction set to determine datapath requirements

- Meaning of each instruction is given by register transfers
- Datapath must include storage element for ISA registers
- Datapath must support each register transfer

Step 2: Select set of datapath components & establish clock methodology


Step 3: Assemble datapath components that meet the requirements

Step 4: Analyze implementation of each instruction to determine setting of control points that realizes the register transfer

Step 5: Assemble the control logic

The MIPS Instruction Formats

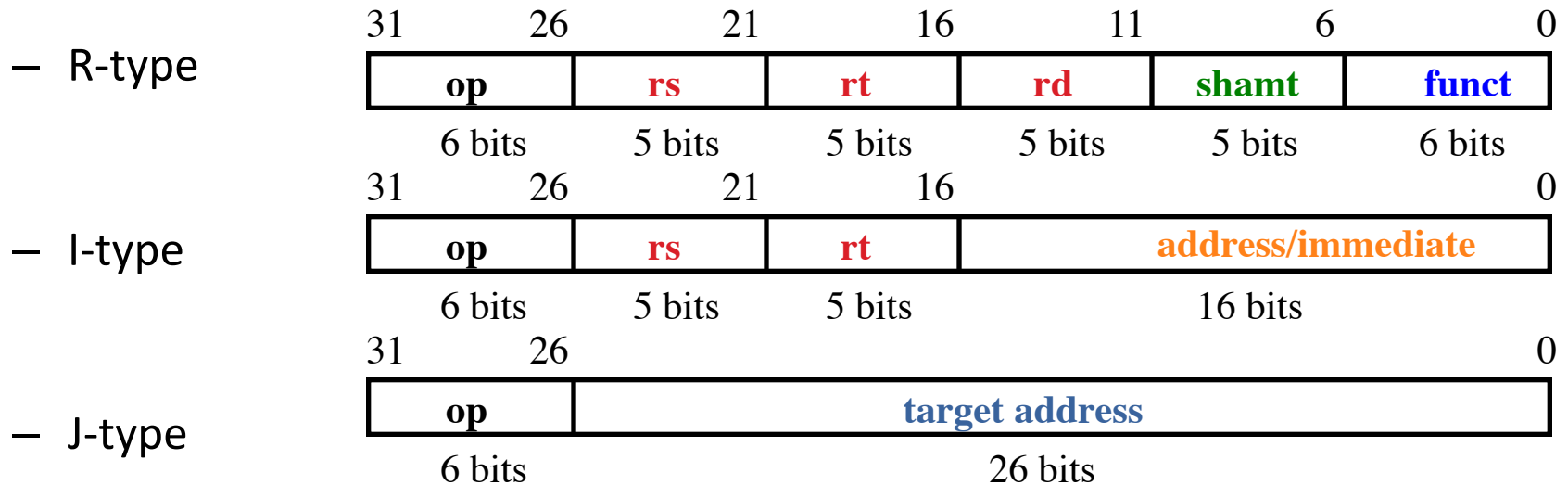- All MIPS instructions are 32 bits long. 3 formats:




- The different fields are:
 - **op**: operation (“opcode”) of the instruction
 - **rs, rt, rd**: the source and destination register specifiers
 - **shamt**: shift amount
 - **funct**: selects the variant of the operation in the “op” field
 - **address / immediate**: address offset or immediate value
 - **target address**: target address of jump instruction

The MIPS-lite Subset

- ADDU and SUBU


- addu rd,rs,rt

- subu rd,rs,rt

 

- OR Immediate:

- ori rt,rs,imm16

 


- LOAD and

- STORE Word


- lw rt,rs,imm16

- sw rt,rs,imm16

 

- BRANCH:

- beq rs,rt,imm16

 

Register Transfer Level (RTL)

- Colloquially called “Register Transfer Language”
- RTL gives the meaning of the instructions
- All start by fetching the instruction itself

```
{op , rs , rt , rd , shamt , funct} ← MEM[ PC ]
```

```
{op , rs , rt , Imm16} ← MEM[ PC ]
```

Inst Register Transfers

```
ADDU    R[rd] ← R[rs] + R[rt]; PC ← PC + 4
```

```
SUBU    R[rd] ← R[rs] - R[rt]; PC ← PC + 4
```

```
ORI     R[rt] ← R[rs] | zero_ext(Imm16); PC ← PC + 4
```

```
LOAD    R[rt] ← MEM[ R[rs] + sign_ext(Imm16) ]; PC ← PC + 4
```

```
STORE   MEM[ R[rs] + sign_ext(Imm16) ] ← R[rt]; PC ← PC + 4
```




```
BEQ     if ( R[rs] == R[rt] )  
          PC ← PC + 4 + {sign_ext(Imm16), 2'b00}  
          else PC ← PC + 4
```

Step 1: Requirements of the Instruction Set

- Memory (MEM)
 - Instructions & data (will use one for each)
- Registers (R: 32, 32-bit wide registers)
 - Read RS
 - Read RT
 - Write RT or RD
- Program Counter (PC)
- Extender (sign/zero extend)
- Add/Sub/OR/etc unit for operation on register(s) or extended immediate (ALU)
- Add 4 (+ maybe extended immediate) to PC
- Compare registers?

Step 2: Components of the Datapath

  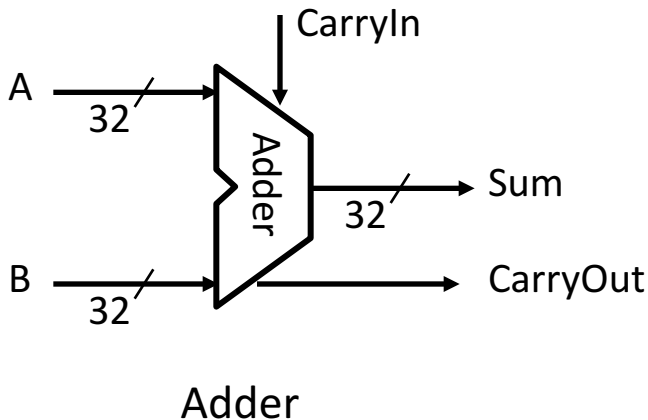- Combinational Elements
- Storage Elements + Clocking Methodology
- Building Blocks



ALU Needs for MIPS-lite + Rest of MIPS

- Addition, subtraction, logical OR, ==:

ADDU $R[rd] = R[rs] + R[rt]; \dots$

SUBU $R[rd] = R[rs] - R[rt]; \dots$


ORI $R[rt] = R[rs] \mid \text{zero_ext}(\text{Imm16}) \dots$

BEQ $\text{if} (R[rs] == R[rt]) \dots$

- Test to see if output == 0 for any ALU operation gives == test. How?
- P&H also adds AND, Set Less Than (1 if $A < B$, 0 otherwise)
- ALU follows Chapter 5


Storage Element: Idealized Memory

- “Magic” Memory
 - One input bus: Data In
 - One output bus: Data Out
- Memory word is found by:
 - For Read: Address selects the word to put on Data Out
 - For Write: Set Write Enable = 1: address selects the memory word to be written via the Data In bus
- Clock input (CLK)
 - CLK input is a factor ONLY during write operation
 - During read operation, behaves as a combinational logic block: Address valid => Data Out valid after “access time”

 

Storage Element: Register (Building Block)

 - Similar to D Flip Flop except
 - N-bit input and output
 - Write Enable input
- Write Enable:
 - Negated (or deasserted) (0): Data Out will not change
 - Asserted (1): Data Out will become Data In on positive edge of clock



Storage Element: Register File

- Register File consists of 32 registers:


- Two 32-bit output busses:
busA and busB
- One 32-bit input bus: busW

- Register is selected by:

- RA (number) selects the register to put on busA (data)
- RB (number) selects the register to put on busB (data)
- RW (number) selects the register to be written via busW (data) when Write Enable is 1


- Clock input (clk)

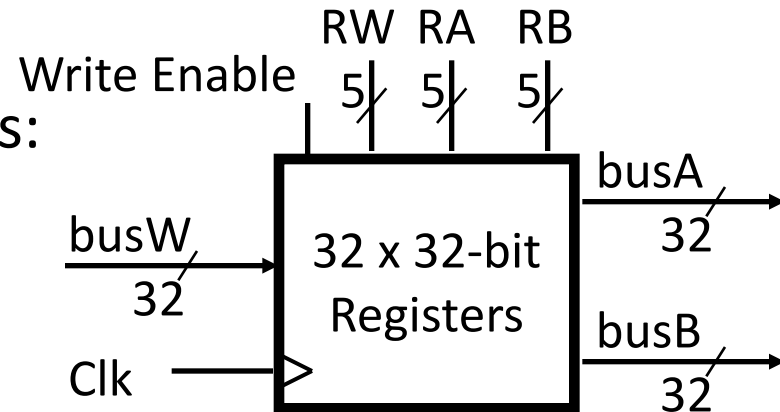- Clk input is a factor ONLY during write operation
- During read operation, behaves as a combinational logic block:
 - RA or RB valid \Rightarrow busA or busB valid after “access time.”




Step 3a: Instruction Fetch Unit

 - Register Transfer Requirements => Datapath Assembly
- Instruction Fetch
- Read Operands and Execute Operation
- Common RTL operations
 - Fetch the Instruction:
 $\text{mem}[\text{PC}]$
 - Update the program counter:
 - Sequential Code:
 $\text{PC} \leftarrow \text{PC} + 4$
 - Branch and Jump:
 $\text{PC} \leftarrow \text{“something else”}$




Step 3b: Add & Subtract

 - $R[rd] = R[rs] \text{ op } R[rt]$ (`addu rd,rs,rt`)
 - Ra, Rb, and Rw come from instruction's Rs, Rt, and Rd fields




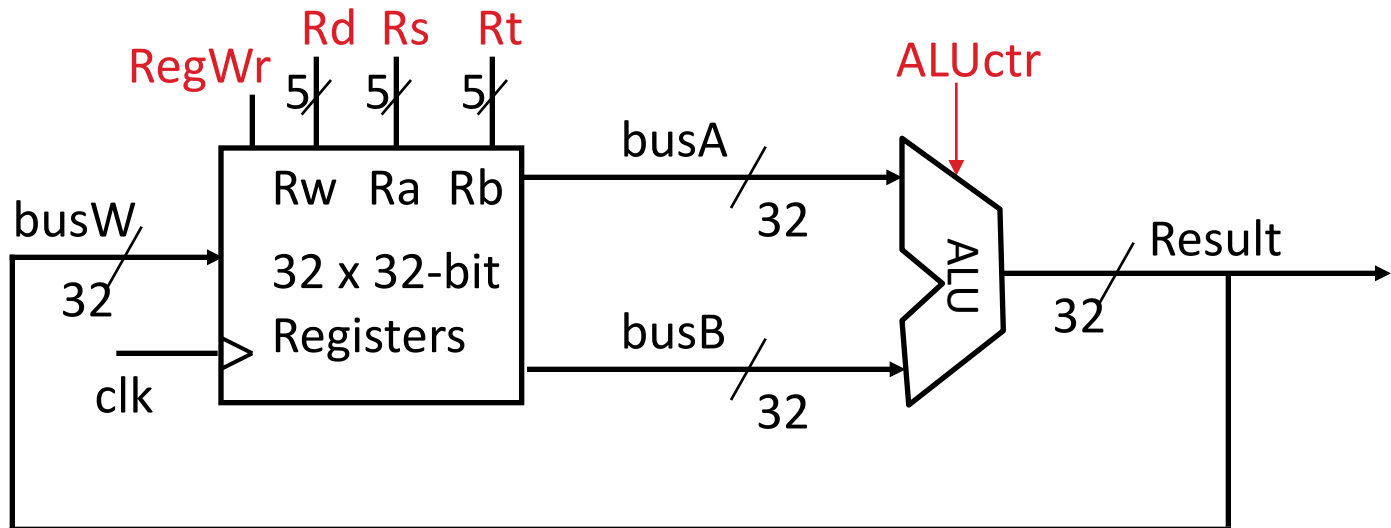- **ALUctr** and **RegWr**: control logic after decoding the instruction





- ... Already defined the register file & ALU

Clocking Methodology

 


- Storage elements clocked by same edge
- Flip-flops (FFs) and combinational logic have some delays
 - Gates: delay from input change to output change
 - Signals at FF D input must be stable before active clock edge to allow signal to travel within the FF (set-up time), and we have the usual clock-to-Q delay
- “Critical path” (longest path through logic) determines length of clock period

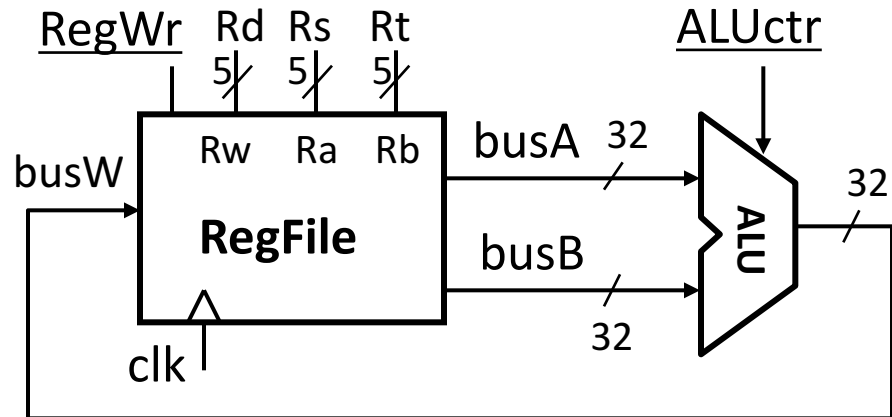 Register-Register Timing: One Complete Cycle (Add/Sub)



Register Write
Occurs Here

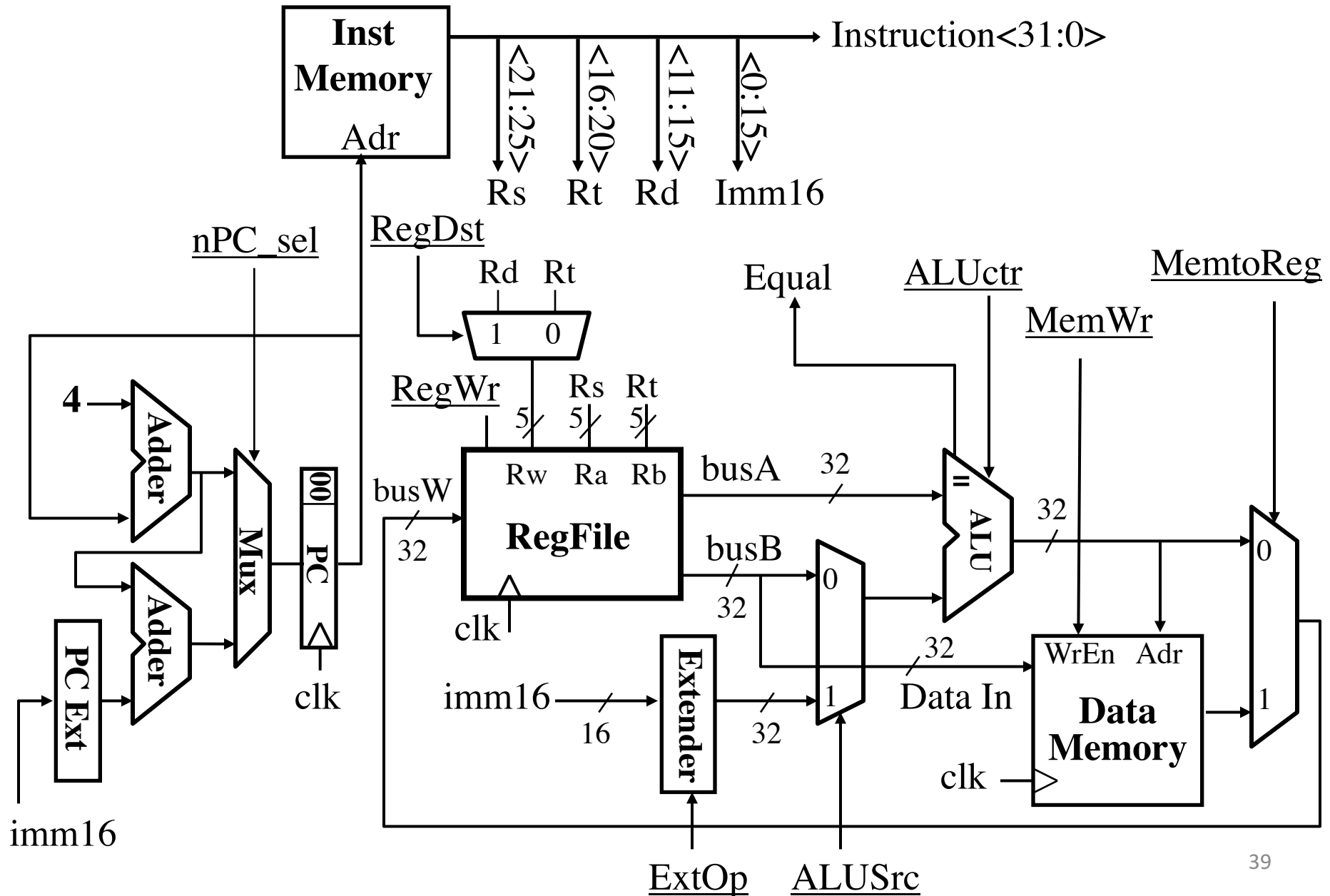Putting it All Together: A Single Cycle Datapath



In Conclusion

- “Divide and Conquer” to build complex logic blocks from smaller simpler pieces (adder)
- Five stages of MIPS instruction execution
- Mapping instructions to datapath components
- Single long clock cycle per instruction