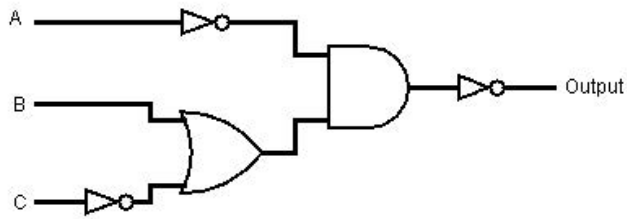


Computer Architecture Homework 4

Spring 2019, March

1 Synchronous Finite State Digital Machine Systems

a. The circuit shown below can be simplified. Write a Boolean expression that represents the function of the simplified circuit using the minimum number of AND, OR, and NOT gate.




$$\text{Sol: } \overline{A} \cdot (B + \overline{C})$$


$$= A + \overline{B + \overline{C}}$$

$$= A + \overline{B} \cdot C$$

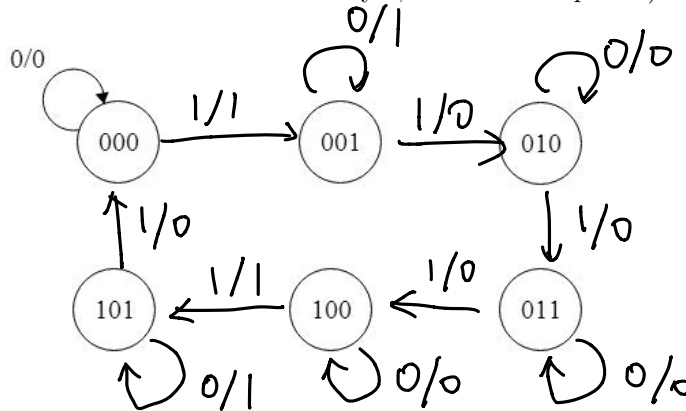b. Consider the finite state machine below which has 6 states and a single input that can take on the value of 0 and 1. The finite state machine should output 1 IF AND ONLY IF 6 + sum of all the input values is not divisible by 2 or 3. One transition has been provided; complete the remainder of the diagram. (Hint: If the sum of the inputs is a multiple of 6, then we have $6 + \text{sum of the inputs} = 6n$ for some n . As $6n$ is divisible by 2, $6n$ cannot be prime.)



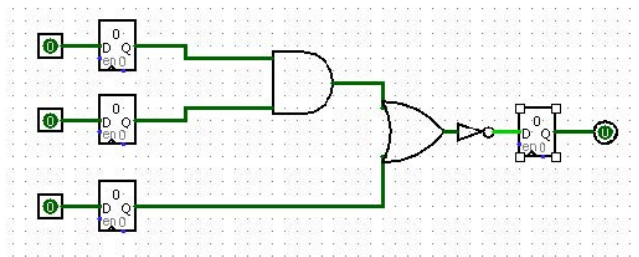c. Consider the following circuit. Assume registers have a CLK to Q time of 60ps, a setup time of 40ps, and a hold time of 30ps. Assuming that all gates have the same propagation delay, what is the maximum propagation delay each individual gate could have to achieve a clock rate of 1 GHz.



Sol: 300 ps.

clock rate = 1 GHz \Rightarrow maximum clock period = 1000 ps.

The critical path includes: 3 combinational logic,
1 CLK-to-Q, 1 setup time.

$$\Rightarrow 3 * CL + 60 \text{ ps} + 40 \text{ ps} = 1000 \text{ ps},$$

$$\Rightarrow CL = 300 \text{ ps}.$$

2 Boolean Logic

1. Simplify each Boolean expression to one of the following ten expressions:

0, 1, A, B, AB, A + B, $\bar{A}\bar{B}$, $\bar{A} + \bar{B}$, $A\bar{B}$, $\bar{A}B$

Each answer may be used as many times as necessary.

a. $A(A + \bar{A}) + B$

$$= A + B$$

b. $(A + B)(\bar{A} + B)\bar{B}$

$$= (AB + B\bar{A} + B)\bar{B}$$

$$= B \cdot \bar{B} = 0$$

c. $\overline{\bar{A} + \bar{B}}$

$$= \bar{\bar{A}} \bar{\bar{B}} = AB$$

2. Simplify the following expression step by step (as simple as possible):

a. Standard: $(A + B)(A + \bar{B})C$

$$= (A + B\bar{B})C$$

$$= AC$$

b. Grouping & Extra Terms: $\bar{A}\bar{B}\bar{C} + \bar{A}B\bar{C} + A\bar{B}\bar{C} + A\bar{B}C + ABC + A\bar{B}C$

$$= \bar{A}\bar{C}(\bar{B} + B) + A\bar{C}(B + \bar{B}) + AC(B + \bar{B})$$

$$= \bar{A}\bar{C} + A\bar{C} + AC$$

$$= \bar{A}\bar{C} + A\bar{C} + A\bar{C} + AC$$

c. DeMorgan's: $\overline{A(\bar{B}\bar{C} + BC)}$

$$= (\bar{A} + A)\bar{C} + A(\bar{C} + C)$$

$$= \bar{A} + \overline{\bar{B}\bar{C} + BC}$$

$$= \bar{C} + A$$

$$= \bar{A} + \overline{\bar{B}\bar{C}} \overline{BC}$$

3

$$= \bar{A} + (B + C)(\bar{B} + \bar{C})$$

$$= \bar{A} + B\bar{C} + \bar{B}C$$

3 Logic Gates


a. Create a NOT gate using only NAND gates.



b. Create an AND gate using only NAND gates. (Hint: use a)



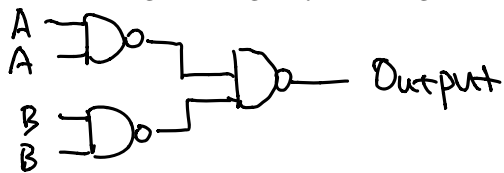c. Create an OR gate using only NAND gates.



d. Create a NOR gate using only NAND gates. (Hint: use a & c)

