

Discussion 10: Project 2

MENGYING WU

DON'T CHANGE THE LOCATIONS OF THE INPUTS AND OUTPUTS!!!!!!


Project 2.1: ALU and RegFile

Files you obtain:


- tests
- alu.circ
- alu_harness.circ
- autolab.txt
- logisim-evolution.jar
- README.md
- regfile.circ
- regfile_harness.circ
- test.sh

Run tests

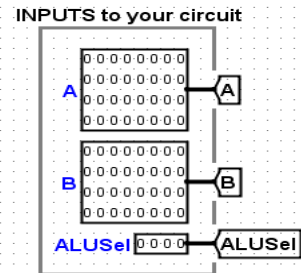You can create your own tests in these two circuit.






 DON'T CHANGE THE LOCATIONS OF THE INPUTS AND OUTPUTS!






DON'T CHANGE THE LOCATIONS OF THE INPUTS AND OUTPUTS!

These are DEBUG/TEST outputs from your circuit.

 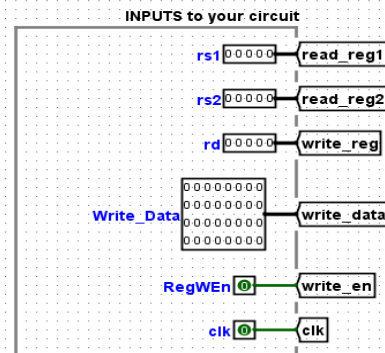 




Project 2.1: ALU

- Input: two 32-bit numbers (A,B) and 4-bit ALUSel
- Output: one 32-bit number
- ALUSel decides what to output (A+B, A-B, or other operations)
- Just like a **multiplexer**
 - You should be familiar with it in Lab5

   

Project 2.1: ALU

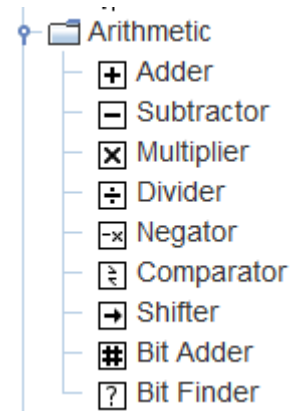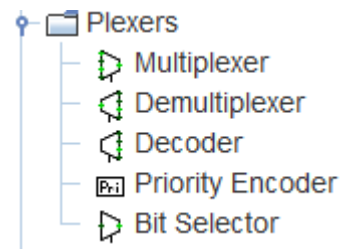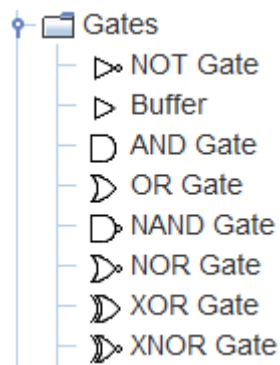
- Your ALU should be able to execute 16 operations as required
 - Some operations may not be used in CPU
 - Some operations may not be included but used in CPU
 - Some operations may not be required but exist in real CPU
 - So you can modify your ALU in later implementation
- You can make good use of Gates, Plexers and Arithmetic to implement.



Of course you can build them by hand if you don't know what to use :)



Project 2.1: ALU

- Tunnel can transfer pins from one place to another without lines
 - Use it to tidy your circuit
 - Recommend if you are OCD

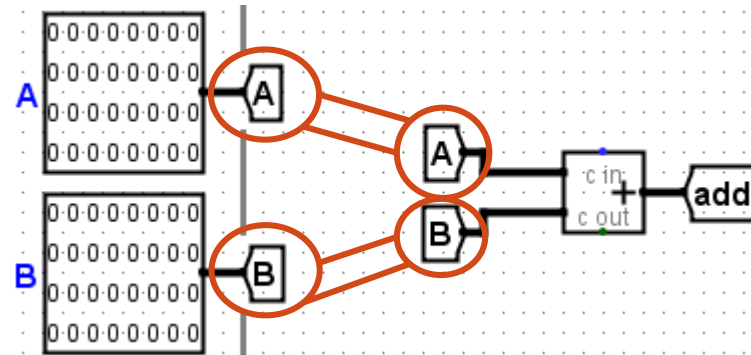

Project 2.1: RegFile


- Our RegFile only has 8 registers.
 - Both in Project 2.1 and Project 2.2
 - But a real CPU has 32 registers, don't make mistakes in exam.
- Input
 - rs1(5-bit), rs2(5-bit), rd(5-bit)
 - WriteData(32-bit)
 - RegWEn(1-bit)
 - Determines whether data is written to the register file on the next rising edge of the clock
 - Clock(1-bit)
 - It is a given clock, which means you shouldn't connect a clock here.
 - Please take a look at `regfile_harness.circ` to see how the clock is used.
- Output
 - Two registers' values, chosen by rs1 and rs2

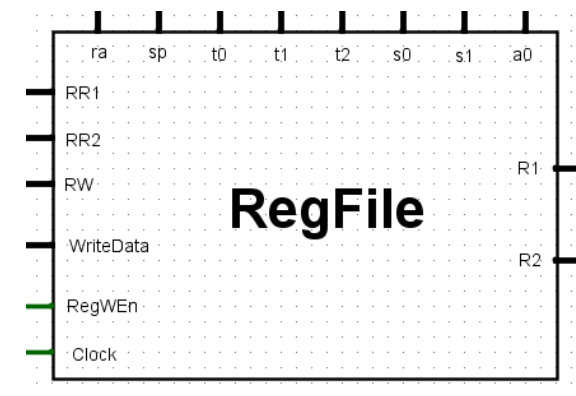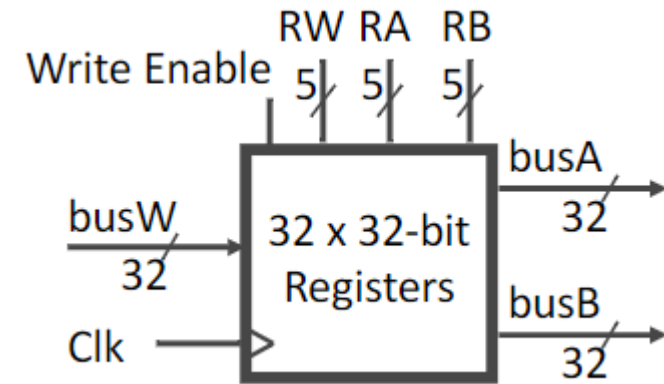

Project 2.1: RegFile



- Only to choose a register and simply output its value then pass RegFile tests?
- No!
- ALU is a Combination Logic, just calculate the current numbers then output.
- RegFile is a Sequential Logic, the most important thing is to maintain the data in your registers.
 - Otherwise you will have all registers equals 0 all the time!

- You can find regi

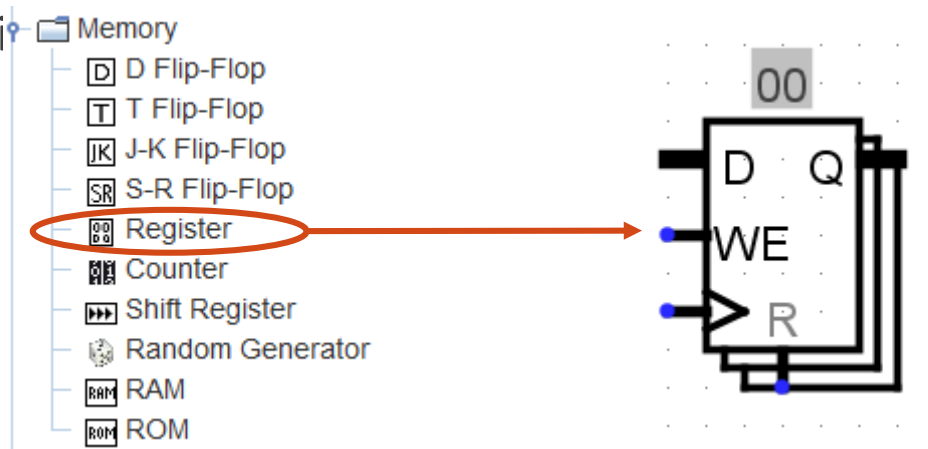


Project 2.1: RegFile

- Demultiplexer
 - A inverse multiplexer
 - Choose one way to output the given number
- You may find it useful when you choose a register to write data according to rd, WriteData and RegWE
- Think of the 5 interfaces of this register, what should them be connected to?

  


Project 2.2: CPU

- Files: `cpu.circ`, `mem.circ`, `run.circ`
- Target: given an address and an instruction, output the updated registers' status.
- `Cpu.circ`
 - You are given PC, DMEM, RegFile and ALU circuits.
 - Remember to move your `regfile.circ` and
 - Main task:
 - Implement a Control Logic, analysis the instruction
 - Connect the lines in this graph
 - And other small logics you need
- `Mem.circ`: DMEM
- `Run.circ`: tests in IMEM

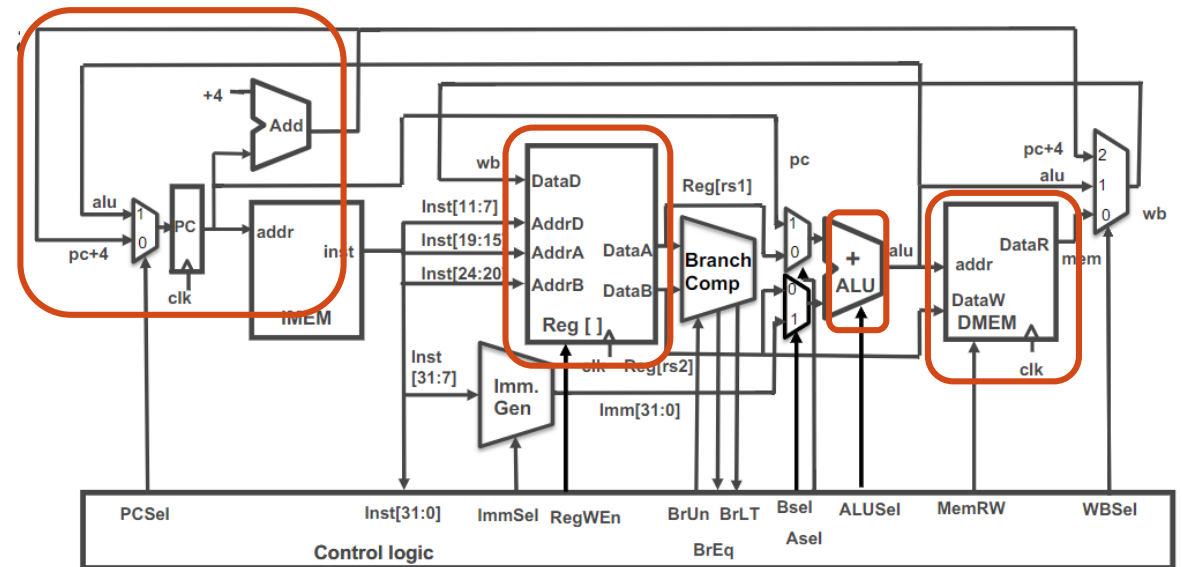


Tip on Logisim

● Zoom

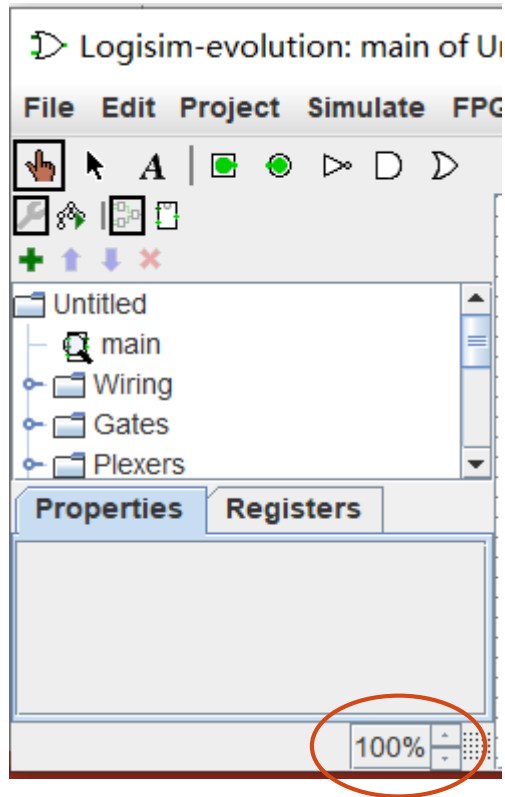

But if you use Logisim on laptop...

 

Project 2

- Project 2.1 will be published tomorrow.
- You have two weeks to implement it.
- Project 2.2 will be published after it.