

Discussion 6: SDS


QIYUAN DAI

A solid red horizontal bar at the bottom of the slide.

Synchronous Digital Systems


- Synchronous:

 - All operations coordinated by a central clock



- Digital:

 - Represent all values by 1 and 0
- High voltage (V_{dd}) = True = On switch = 1
- Low voltage (0V) = False = Off switch = 0




- Synchronous Digital Systems consist of two basic types of circuits:

- Combinational Logic (CL) circuits
- Sequential Logic (SL)


CMOS Transistor Networks

Negative

 


Off when voltage at Gate is low
On when voltage(Gate) > voltage (Threshold)
Can pass 0V when Gate is 1V

Positive

 

On when voltage at Gate is low
Off when voltage(Gate) > voltage (Threshold)
Can pass 1V when Gate is 0V

CMOS Networks

 


X	Y	Z
1	1	0
1	0	1
0	1	1
0	0	1

Combinational Logic


AND

$$A \cdot B$$

 


OR

$$A + B$$

 

NOT

$$\bar{A}$$

 

Truth Table

- Same as Discrete Mathematics
- Single bit input

A	B	C
1	1	0
1	0	1
0	1	1
0	0	0

- Multiple bit input

A	B	C
a_1a_0	b_1b_0	$c_2c_1c_0$

From Truth Table to logical expression

- Sum of Products form (AKA Principal Disjunctive Normal Form in Discrete Mathematics)

- $C = A \cdot \bar{B} + \bar{A} \cdot B$

- This will help you simplify an unknown logic.

- Also you can use Product of Sums (AKA PCNF)

- $C = (A + B) \cdot (\bar{A} + \bar{B})$

- Do not forget to use Laws of Boolean Algebra.

$$X\bar{X} = 0$$

$$X0 = 0$$

$$X1 = X$$

$$XX = X$$

$$XY = YX$$

$$(XY)Z = X(YZ)$$

$$X(Y+Z) = XY + XZ$$

$$XY + X = X$$

$$\bar{X}Y + X = X + Y$$

$$\overline{XY} = \bar{X} + \bar{Y}$$

$$X + \bar{X} = 1$$

$$X + 1 = 1$$

$$X + 0 = X$$

$$X + X = X$$

$$X + Y = Y + X$$

$$(X + Y) + Z = X + (Y + Z)$$

$$X + YZ = (X + Y)(X + Z)$$

$$(X + Y)X = X$$


$$(\bar{X} + Y)X = XY$$

$$\overline{X + Y} = \bar{X}\bar{Y}$$

Complementarity
Laws of 0's and 1's
Identities
Idempotent Laws
Commutativity
Associativity
Distribution
Uniting Theorem
Uniting Theorem v. 2
DeMorgan's Law

Representations of Combinational Logic

Gate Diagram

 


Boolean Expression

$$C = A \cdot \bar{B} + \bar{A} \cdot B$$


Truth Table

A	B	C
1	1	0
1	0	1
0	1	1
0	0	0

Example

 


Example

 


$$\begin{aligned} C &= (A + B) \cdot (\bar{A} + B) \cdot B \\ &= (A \cdot \bar{A} + B \cdot \bar{A} + A \cdot B + B \cdot B) \cdot B \\ &= (B \cdot (\bar{A} + A) + B) \cdot B \\ &= (B + B) \cdot B \\ &= B \cdot B \\ &= B \end{aligned}$$

7. SDS

 - (a) Draw the Timing Diagram for the circuit below. The delay for the gates are 10 ns, the clock-to-q delay for a register is 20 ns, each clock cycle is 80 ns, each grid in the following diagram is a unit of 10 ns. The output is initially given in the graph.



 Use any of those graphs to put in your answer (so you can re-do it). Clearly mark your final answer if you use more than one graph!



8. Circuit time calculation

In this circuit below, RegA and RegB have setup, hold and clk-to-q times of 8ns, NOT logic gate has a delay of 1ns, AND logic gate has a delay of 3ns, XNOR logic gate has a delay of 5ns, and RegC has a setup time of 9ns.

