


Discussion 8

Control Logic & FSM

Yida Zhao

zhaoyd1@shanghaitech.edu.cn

Complete RV32I Datapath!

 

Control Logic Truth Table

Inst[31:0]	BrEq	BrLT	PCSel	ImmSel	BrUn	ASel	BSel	ALUSel	MemRW	RegWEn	WBSel
add	*	*	+4	*	*	Reg	Reg	Add	Read	1	ALU
sub	*	*	+4	*	*	Reg	Reg	Sub	Read	1	ALU
(<i>R-R</i> <i>Op</i>)	*	*	+4	*	*	Reg	Reg	(<i>Op</i>)	Read	1	ALU
addi	*	*	+4	I	*	Reg	Imm	Add	Read	1	ALU
lw	*	*	+4	I	*	Reg	Imm	Add	Read	1	Mem
sw	*	*	+4	S	*	Reg	Imm	Add	Write	0	*
beq	0	*	+4	B	*	PC	Imm	Add	Read	0	*
beq	1	*	ALU	B	*	PC	Imm	Add	Read	0	*
bne	0	*	ALU	B	*	PC	Imm	Add	Read	0	*
bne	1	*	+4	B	*	PC	Imm	Add	Read	0	*
blt	*	1	ALU	B	0	PC	Imm	Add	Read	0	*
bltu	*	1	ALU	B	1	PC	Imm	Add	Read	0	*
jalr	*	*	ALU	I	*	Reg	Imm	Add	Read	1	PC+4
jal	*	*	ALU	J	*	PC	Imm	Add	Read	1	PC+4
auipc	*	*	+4	U	*	PC	Imm	Add	Read	1	ALU

Implementation: ROM or Combinational Logic

Combinational Logic: faster

ROM: easy to design and reprogram

RV32I, a nine-bit ISA!


			imm[31:12]			rd		0110111	LUI
			imm[31:12]			rd		0010111	AUIPC
			imm[20:10:11 19:12]			rd		1101111	JAL
		imm[11:0]		rs1	000	rd		1100111	JALR
	imm[12:10:5]		rs2	rs1	000	imm[4:1:11]		1100011	BEQ
	imm[12:10:5]		rs2	rs1	001	imm[4:1:11]		1100011	BNE
	imm[12:10:5]		rs2	rs1	100	imm[4:1:11]		1100011	BLT
	imm[12:10:5]		rs2	rs1	101	imm[4:1:11]		1100011	BGE
	imm[12:10:5]		rs2	rs1	110	imm[4:1:11]		1100011	BLTU
	imm[12:10:5]		rs2	rs1	111	imm[4:1:11]		1100011	BGEU
		imm[11:0]		rs1	000	rd		0000011	LB
		imm[11:0]		rs1	001	rd		0000011	LH
		imm[11:0]		rs1	010	rd		0000011	LW
		imm[11:0]		rs1	100	rd		0000011	LBU
		imm[11:0]		rs1	101	rd		0000011	LHU
	imm[11:5]		rs2	rs1	000	imm[4:0]		0100011	SB
	imm[11:5]		rs2	rs1	001	imm[4:0]		0100011	SH
	imm[11:5]		rs2	rs1	010	imm[4:0]		0100011	SW
		imm[11:0]		rs1	000	rd		0010011	ADDI
		imm[11:0]		rs1	010	rd		0010011	SLTI
		imm[11:0]		rs1	011	rd		0010011	SLTIU
		imm[11:0]		rs1	100	rd		0010011	XORI
		imm[11:0]		rs1	110	rd		0010011	ORI
		imm[11:0]		rs1	111	rd		0010011	ANDI

inst[30]			inst[14:12]		inst[6:2]		
0000000	shamt	rs1	001	rd	0010011	SLLI	
0000000	shamt	rs1	101	rd	0010011	SRLI	
0100000	shamt	rs1	101	rd	0010011	SRAI	
0000000	rs2	rs1	000	rd	0110011	ADD	
0100000	rs2	rs1	000	rd	0110011	SUB	
0000000	rs2	rs1	001	rd	0110011	SLL	
0000000	rs2	rs1	010	rd	0110011	SLT	
0000000	rs2	rs1	011	rd	0110011	SLTU	
0000000	rs2	rs1	100	rd	0110011	XOR	
0000000	rs2	rs1	101	rd	0110011	SRL	
0100000	rs2	rs1	101	rd	0110011	SRA	
0000000	rs2	rs1	110	rd	0110011	OR	
0000000	rs2	rs1	111	rd	0110011	AND	
0000	pred	succ	0000	000	00000	0001111	FENCE
0000	0000	0000	00000	001	00000	0001111	FENCE.I
000000000000			00000	000	00000	1110011	ECALL
0000000000001			00000	000	00000	1110011	EBREAK
csr			rs1	001	rd	1110011	CSRRW
csr			rs1	010	rd	1110011	CSRRS
csr			rs1	011	rd	1110011	CSRRC
csr			zimm	101	rd	1110011	CSRRWI
csr			zimm	110	rd	1110011	CSRRSI
csr			zimm	111	rd	1110011	CSRRCI

Not in CS110

Instruction type encoded using only 9 bits
inst[30],inst[14:12], inst[6:2]


Control Block Design

 


Control Logic Truth Table

Inst[31:0]	BrEq	BrLT	PCSel	ImmSel	BrUn	ASel	BSel	ALUSel	MemRW	RegWEn	WBSel
add	*	*	+4	*	*	Reg	Reg	Add	Read	1	ALU
sub	*	*	+4	*	*	Reg	Reg	Sub	Read	1	ALU
(<i>R-R</i> <i>Op</i>)	*	*	+4	*	*	Reg	Reg	(<i>Op</i>)	Read	1	ALU
addi	*	*	+4	I	*	Reg	Imm	Add	Read	1	ALU
lw	*	*	+4	I	*	Reg	Imm	Add	Read	1	Mem
sw	*	*	+4	S	*	Reg	Imm	Add	Write	0	*
beq	0	*	+4	B	*	PC	Imm	Add	Read	0	*
beq	1	*	ALU	B	*	PC	Imm	Add	Read	0	*
bne	0	*	ALU	B	*	PC	Imm	Add	Read	0	*
bne	1	*	+4	B	*	PC	Imm	Add	Read	0	*
blt	*	1	ALU	B	0	PC	Imm	Add	Read	0	*
bltu	*	1	ALU	B	1	PC	Imm	Add	Read	0	*
jalr	*	*	ALU	I	*	Reg	Imm	Add	Read	1	PC+4
jal	*	*	ALU	J	*	PC	Imm	Add	Read	1	PC+4
auipc	*	*	+4	U	*	PC	Imm	Add	Read	1	ALU

ROM Controller Implementation

 

Controller: AND logic (add, sw)

 

- $\text{add} = \overline{\text{inst}[2]} \cdot \overline{\text{inst}[3]} \cdot \overline{\text{inst}[4]} \cdot \overline{\text{inst}[5]} \cdot \overline{\text{inst}[6]} \cdot \overline{\text{inst}[12]} \cdot \overline{\text{inst}[13]} \cdot \overline{\text{inst}[14]} \cdot \overline{\text{inst}[30]}$
- $\text{sw} = \overline{\text{inst}[2]} \cdot \overline{\text{inst}[3]} \cdot \overline{\text{inst}[4]} \cdot \overline{\text{inst}[5]} \cdot \overline{\text{inst}[6]} \cdot \overline{\text{inst}[12]} \cdot \overline{\text{inst}[13]} \cdot \overline{\text{inst}[14]}$


AND Controller Logic														
	2	3	4	5	6	12	13	14	30	unused				
add	$\text{xor}(i[2], 1) \cdot \text{xor}(i[3], 1) \cdot \text{xor}(i[4], 0) \cdot \text{xor}(i[5], 0) \cdot \text{xor}(i[6], 1) \cdot \text{xor}(i[12], 1) \cdot \text{xor}(i[13], 1) \cdot \text{xor}(i[14], 1) \cdot (\text{xor}(i[30], 1) + 0)$													
sw	$\text{xor}(i[2], 1) \cdot \text{xor}(i[3], 1) \cdot \text{xor}(i[4], 1) \cdot \text{xor}(i[5], 0) \cdot \text{xor}(i[6], 1) \cdot \text{xor}(i[12], 1) \cdot \text{xor}(i[13], 1) \cdot \text{xor}(i[14], 1) \cdot (\text{xor}(i[30], 1) + 1)$													
...														


- $\text{bne_t} = \text{bne} \cdot \overline{\text{BrEQ}}$
- $\text{bne_f} = \text{bne} \cdot \text{BrEQ}$

Controller: OR logic



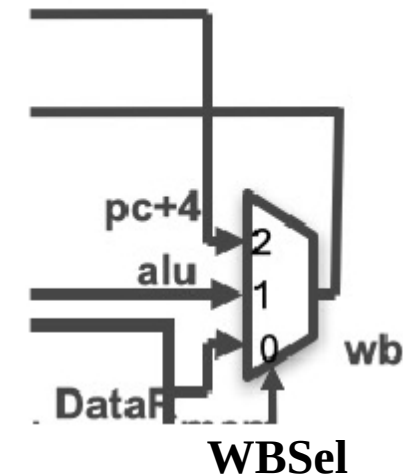- MemRW = sw + sh + sB
- WBSel[0] = add + (all reg. to reg.) + AUIPC + ...
- WBSel[1] = JALR + JAL
- PCSel = Beq_t + Bne_t + Blt_t + Bltu_t + jal + jalr
- ...



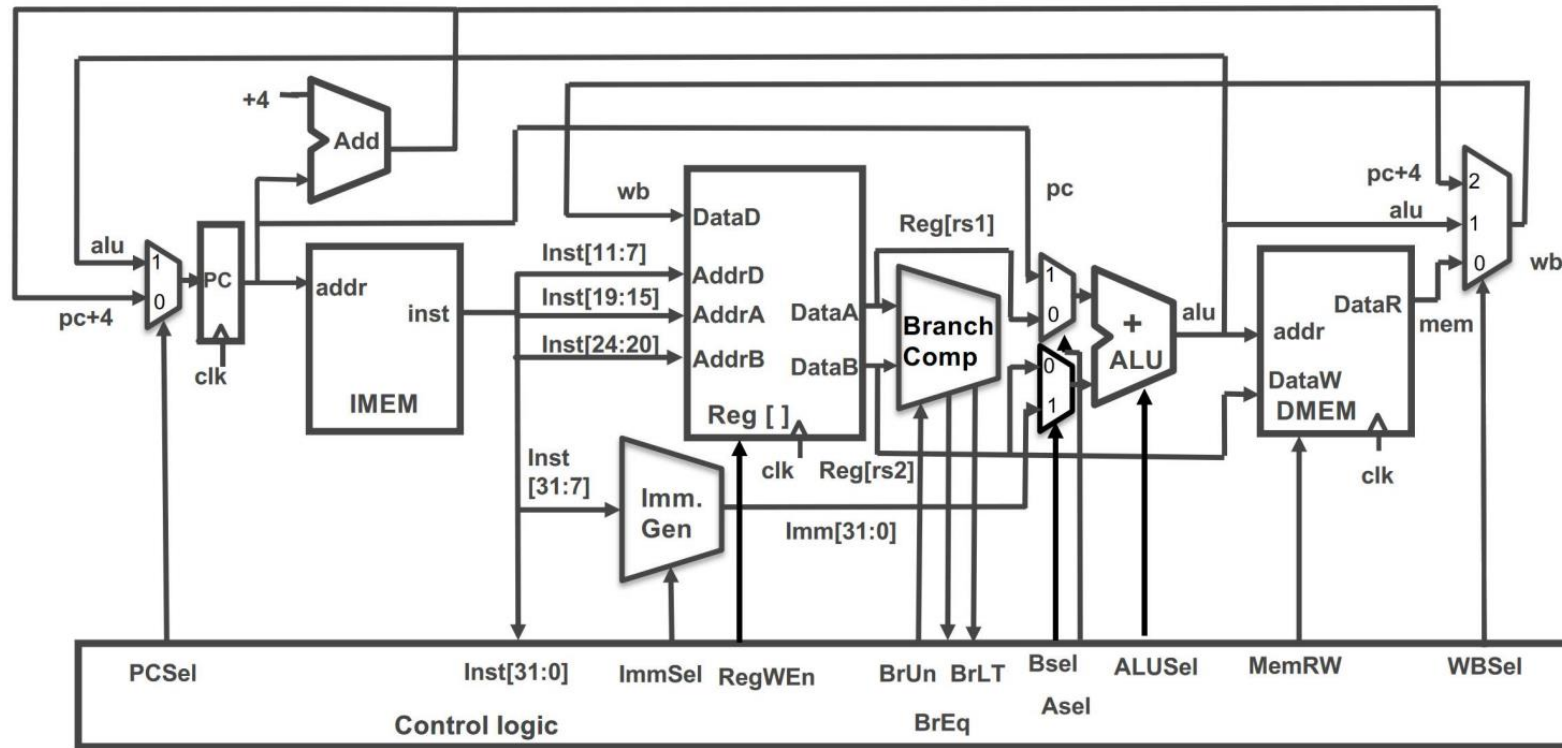


- (c) Assume $t3 = 0x8ffffff$, $t4 = 0x0ffffff$. Write down control signals for **blt t3, t4, label**. Please use * to indicate that what this signal does not matter.

PCSel	ImmSel	RegWEn	BrUn	BrEq	BrLT	ASel	BSel	ALUSel	MemRW	WBSel


Solution: PCSel = 1 ImmSel = B RegWEn = 0 BrUn = 0 BrEq = 0 BrLT = 1 ASel = 1 BSel = 1 ALUSel = Add MemRW = Read WBSel = *

Finite State Machines

 - A convenient way to conceptualize computation over time
- Start at a state, given an input, follow some edge to another
- With combinational logic and registers, any FSM can be implemented in hardware
- edge: input/output




Example

 

state bit1	state bit0	Input	next state bit1	next state bit0	Output
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	1	0	0
0	1	1	0	1	0
1	0	0	0	0	0
1	0	1	0	1	1


Example

 

What does the given FSM output with the input bit string '0100101010'?

Solution: It outputs '0000001010'.

Example

 

What does the given FSM implement (Describe when the FSM will output 1)?

Solution: When the FSM receives '101', it outputs 1.

(d) Draw a FSM that outputs 1 when it receives two or more successive '0'.



Solution:

