## EE100-Electronics Homework 2

Due June 11th, 2015 @ class

Read Harris textbook, Chapter 2.

Problem 1 Write a Boolean equation in sum-of products form for each of the truth tables in Fig. 1

(a)			(b	)				(c)				(d)					(e)				
Α	В	Y		Α	В	С	Y	Α	В	С	Y	Α	В	С	D	Y	A	В	С	D	Y
0	0	0		0	0	0	0	0	0	0	0	0	0	0	0	1	0	0	0	0	0
0	1	1		0	0	1	1	0	0	1	1	0	0	0	1	0	0	0	0	1	0
1	0	1		0	1	0	1	0	1	0	0	0	0	1	0	1	0	0	1	0	0
1	1	1		0	1	1	1	0	1	1	0	0	0	1	1	1	0	0	1	1	1
				1	0	0	1	1	0	0	0	0	1	0	0	0	0	1	0	0	0
				1	0	1	0	1	0	1	0	0	1	0	1	0	0	1	0	1	0
				1	1	0	1	1	1	0	1	0	1	1	0	1	0	1	1	0	1
				1	1	1	0	1	1	1	1	0	1	1	1	1	0	1	1	1	1
												1	0	0	0	1	1	0	0	0	1
												1	0	0	1	0	1	0	0	1	1
												1	0	1	0	1	1	0	1	0	1
												1	0	1	1	0	1	0	1	1	1
												1	1	0	0	0	1	1	0	0	0
												1	1	0	1	0	1	1	0	1	0
												1	1	1	0	0	1	1	1	0	0
												1	1	1	1	0	1	1	1	1	0

Figure 1:

**Problem 2** Simplify each of the following Boolean equations. Sketch a reasonably simple combinational circuit implementing the simplified equation.

- (a)  $Y = \overline{A}BC + \overline{B}\overline{C} + BC$
- (b)  $Y = \overline{A + B + C}D + AD + B$
- (c)  $Y = ABCD + \overline{A}B\overline{C}D + (\overline{\overline{B}} + D)E$

Α	В	С	D	Y
0	0	0	0	Х
0	0	0	1	Х
0	0	1	0	Х
0	0	1	1	0
0	1	0	0	0
0	1	0	1	Х
0	1	1	0	0
0	1	1	1	Х
1	0	0	0	1
1	0	0	1	0
1	0	1	0	Х
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	Х
1	1	1	1	1

**Problem 3** Find a minimal Boolean equation for the function in Fig. 2. Remember to take advantage of the don't care entries.

Figure 2: