

Lecture 3



信息科学与技术学院
School of Information Science and Technology

Combinational Logic Circuits

Haoyu Wang
ShanghaiTech University



Introduction to Information Science and Technology (Electronics)

ShanghaiTech University

Outline



信息科学与技术学院
School of Information Science and Technology

- Logic Circuits Simplification
- Combinational Logic Circuits Design
- Karnaugh Map
- Exclusive-OR & Exclusive-NOR Circuits
- Enable/Disable Circuits

Introduction to Information Science and Technology (Electronics)

ShanghaiTech University



Outline

- Logic Circuits Simplification
- Combinational Logic Circuits Design
- Karnaugh Map
- Exclusive-OR & Exclusive-NOR Circuits
- Enable/Disable Circuits



Sum-of-Products Form

- **Sum-of-products (SOP) :**
 - » Multiple **AND** terms **ORed** together

1. $ABC + \overline{A}\overline{B}\overline{C}$

2. $AB + \overline{A}BC + \overline{C}\overline{D} + D$

3. $\overline{A}B + \overline{C}\overline{D} + EF + GK + H\overline{L}$



Products-of-Sums Form

- **Product-of-sums (POS) expression:**

- » Multiple **OR** terms (sums) **AND**ed together.


1. $(A + \bar{B} + C)(A + C)$

2. $(A + \bar{B})(\bar{C} + D)F$

3. $(A + C)(B + \bar{D})(\bar{B} + C)(A + \bar{D} + \bar{E})$



Simplifying Logic Circuits

 

- (a) and (b) are equivalent!

- » Circuit (b) is clearly less complex.



Algebraic Simplification

- (a) \Rightarrow (b) logic circuit simplification
- Circuit simplification techniques
 - » Boolean algebra (algebraic simplification)
 - » Karnaugh map




Algebraic Simplification

- 1. Place the expression in SOP form by applying DeMorgan's theorems and multiplying terms.
- 2. Check the SOP form for common factors
 - » Factoring where possible should eliminate one or more terms.




Example

Simplify the logic circuit shown.

 

Step 1

 


Determine the expression for the output:

$$z = ABC + A\overline{B} \cdot (\overline{A}C)$$



Step 2

 


$$z = ABC + \overline{A}\overline{B} \cdot (\overline{A}\overline{C})$$

Convert the expression to SOP form by applying DeMorgan's theorems and multiplying terms

$$\begin{aligned} z &= ABC + \overline{A}\overline{B}(\overline{A} + \overline{C}) && \text{[theorem (17)]} \\ &= ABC + \overline{A}\overline{B}(A + C) && \text{[cancel double inversions]} \\ &= ABC + \overline{A}\overline{B}A + \overline{A}\overline{B}C && \text{[multiply out]} \\ &= ABC + \overline{A}\overline{B} + \overline{A}\overline{B}C && \text{[}A \cdot A = A\text{]} \end{aligned}$$



Step 3

 


$$z = ABC + \overline{A}\overline{B} + \overline{A}\overline{B}C$$

Factoring

$$\begin{aligned} z &= AC(B + \overline{B}) + \overline{A}\overline{B} \\ &= AC(1) + \overline{A}\overline{B} \\ &= AC + \overline{A}\overline{B} \end{aligned}$$




Step 4

 

$$z = A(C + \bar{B})$$

Draw the simplified logic circuit

 


Outline

- Logic Circuits Simplification
- **Combinational Logic Circuits Design**
- Karnaugh Map
- Exclusive-OR & Exclusive-NOR Circuits
- Enable/Disable Circuits



 Description: circuit that produces a 1 output only for the $A = 0, B = 1$ condition.



- Question: How to implement a combinational digital circuit from the literal description?



Example

- Design a logic circuit
 - » The circuit has 3 inputs, A, B, and C, and 1 output, X.
 - » X will be HIGH only when a majority of the inputs are HIGH



Step 1

- Set up the truth table

Problem: Design a logic circuit that has 3 inputs, A, B, and C, and whose output will be HIGH only when a majority of the inputs are HIGH.

A	B	C	X
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1



Step 2

- Write the **AND** term for each case where the output is a 1.

A	B	C	X
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1



Step 3

- Write the sum-of-products expression for the output

A	B	C	X
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

$$X = A'BC + AB'C + ABC' + ABC$$

→ A'BC

→ AB'C

→ ABC'

→ ABC



Step 4

- Simplify the output expression
 - Recall Algebraic Simplification

$$\begin{aligned} X &= A'BC + AB'C + ABC' + ABC \\ &= A'BC + ABC + AB'C + ABC + ABC' + ABC \end{aligned}$$


$$X = BC(A' + A) + AC(B' + B) + AB(C' + C)$$

$$X = BC + AC + AB$$



Step 5

 - Implement the circuit for the final expression



Since the expression is in SOP form, the circuit is a group of **AND** gates, working into a single **OR** gate,



Generalized Procedures

- » 1. Interpret the problem and set up its truth table.
- » 2. Write the **AND** (product) term for each case where output = 1.
- » 3. Combine the terms in SOP form.
- » 4. Simplify the output expression if possible.
- » 5. Implement the circuit for the final, simplified expression.



Outline

- Logic Circuits Simplification
- Combinational Logic Circuits Design
- **Karnaugh Map**
- Exclusive-OR & Exclusive-NOR Circuits
- Enable/Disable Circuits



What is Karnaugh Map?

- A graphical method of simplifying logic equations or truth tables
- Also called a K map (卡诺图)



Example: 2-variable K map

A	B	X
0	0	1 → $\bar{A}\bar{B}$
0	1	0
1	0	0
1	1	1 → AB

$$\left\{ x = \bar{A}\bar{B} + AB \right\}$$

	\bar{B}	B
\bar{A}	1	0
A	0	1



Example: 4-variable K map

A	B	C	D	X
0	0	0	0	0
0	0	0	1	1 → $ABCD$
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	1 → $\bar{A}BCD$
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	0
1	1	0	0	0
1	1	0	1	1 → $ABCD$
1	1	1	0	0
1	1	1	1	1 → $ABCD$

$$\left\{ X = \bar{A}BCD + ABCD + AB\bar{C}D + ABCD \right\}$$

	$\bar{C}\bar{D}$	$\bar{C}D$	CD	$C\bar{D}$
$\bar{A}\bar{B}$	0	1	0	0
$\bar{A}B$	0	1	0	0
$A\bar{B}$	0	1	1	0
AB	0	0	0	0

-Adjacent K map square differ in only one variable both horizontally and vertically.

-A SOP expression can be obtained by **OR**ing all squares that contain a 1.



Looping

- Looping 1s in adjacent groups of 2, 4, or 8 will result in further simplification.

	C'	C
A'B'	0	0
A'B	1	1
AB	0	0
AB'	0	0

$$X = A'BC' + A'BC = A'B$$



Pairs

- Pairs: Looping 1s in adjacent groups of 2 elements

	C'	C
AB	0	0
AB	1	1
AB	0	0
AB	0	0

$X = ABC + ABC = AB$

	C'	C
AB	0	0
AB	1	0
AB	1	0
AB	0	0

$X = ABC + ABC = BC$

	C'	C
AB	1	0
AB	0	0
AB	0	0
AB	1	0

$X = ABC + ABC = BC$

	CD	CD	CD	CD
AB	0	0	1	1
AB	0	0	0	0
AB	0	0	0	0
AB	1	0	0	0

$X = ABCD + ABCD + ABCD + ABCD = ABC + ABD$

Note: Looping a pair of adjacent 1s eliminates **1** variable that appears in complemented and uncomplemented form



Quads

- Quads: Looping 1s in adjacent groups of 4 elements

	$\bar{C}\bar{D}$	$\bar{C}D$	CD	$C\bar{D}$
$\bar{A}\bar{B}$	0	0	0	0
$\bar{A}B$	0	0	0	0
AB	1	1	1	1
$A\bar{B}$	0	0	0	0

$X = AB$

Note: Looping a quad of adjacent 1s eliminates **2** variable that appears in complemented and uncomplemented form



Octets

- Octets: Looping 1s in adjacent groups of 8 elements

	$\bar{C}\bar{D}$	$\bar{C}D$	CD	$C\bar{D}$
$\bar{A}\bar{B}$	1	0	0	1
$\bar{A}B$	1	0	0	1
AB	1	0	0	1
$A\bar{B}$	1	0	0	1

$X = \bar{D}$

Note: Looping a octet of adjacent 1s eliminates **3** variable that appears in complemented and uncomplemented form



- Note:
 - » 1. When the largest possible groups have been looped, only the common terms are placed in the final expression.
 - » 2. Looping may also be wrapped between **top**, **bottom**, and **sides**.



Example: Step 1

- Construct the K map from the truth table
- Place 1s as indicated in the truth table.

X	C'D'	C'D	CD	CD'
A'B'	0	0	0	1
A'B	0	1	1	0
AB	0	1	1	0
AB'	0	0	1	0



Step 2

- Loop 1s that are not adjacent to any other 1s.

X	C'D'	C'D	CD	CD'
A'B'	0	0	0	1
A'B	0	1	1	0
AB	0	1	1	0
AB'	0	0	1	0

→ A'B'CD'



Step 3

- Loop 1s that are in pairs.

X	C'D'	C'D	CD	CD'
A'B'	0	0	0	1
A'B	0	1	1	0
AB	0	1	1	0
AB'	0	0	1	0

→ A'B'CD'

→ ACD



Step 4

- Loop 1s in octets even if they have already been looped

X	C'D'	C'D	CD	CD'
A'B'	0	0	0	1
A'B	0	1	1	0
AB	0	1	1	0
AB'	0	0	1	0

→ A'B'CD'

→ ACD

There are no octets



Step 5

- Loop quads that have one or more 1s not already looped.

X	C'D'	C'D	CD	CD'
A'B'	0	0	0	1
A'B	0	1	1	0
AB	0	1	1	0
AB'	0	0	1	0

→ A'B'CD'

→ BD

→ ACD



Step 6

- Loop any pairs necessary to include 1st not already looped.

X	C'D'	C'D	CD	CD'
A'B'	0	0	0	1
A'B	0	1	1	0
AB	0	1	1	0
AB'	0	0	1	0

Diagram illustrating the Karnaugh map for Step 6. The map shows the following 1s: (A'B', CD'), (A'B, C'D), (A'B, CD), (AB, C'D), (AB, CD), (AB', CD). The 1s are grouped into three loops: a vertical loop for A'B'CD', a horizontal loop for BD, and a vertical loop for ACD.

All 1s have already been looped



Step 7

- Form the **OR** sum of terms generated by each loop.

X	C'D'	C'D	CD	CD'
A'B'	0	0	0	1
A'B	0	1	1	0
AB	0	1	1	0
AB'	0	0	1	0

Diagram illustrating the Karnaugh map for Step 7. The map shows the following 1s: (A'B', CD'), (A'B, C'D), (A'B, CD), (AB, C'D), (AB, CD), (AB', CD). The 1s are grouped into three loops: a vertical loop for A'B'CD', a horizontal loop for BD, and a vertical loop for ACD.

$$X = A'B'CD' + ACD + BD$$



Generalized Procedures

- » 1. Construct the K map, place 1s as indicated in the truth table.
- » 2. Loop 1s that are not adjacent to any other 1s.
- » 3. Loop 1s that are in pairs.
- » 4. Loop 1s in octets even if they have already been looped.
- » 5. Loop quads that have one or more 1s not already looped.
- » 6. Loop any pairs necessary to include 1st not already looped.
- » 7. Form the **OR** sum of terms generated by each loop.



X	C'D'	C'D	CD	CD'
A'B'	0	0	0	1
A'B	0	1	1	0
AB	0	1	1	0
AB'	0	0	1	0

● Note:

- » 1. When a variable appears in both complemented and uncomplemented form within a loop, that variable is eliminated from the expression.
- » 2. Variables that are the same for all squares of the loop must appear in the final expression.
- » 3. K map theoretically can be used for any number of input variables—practically limited to 5 or 6 variables.



Don't-Care Conditions

- x represents the don't care condition
 - » Its free to make the output for any don't care condition either a 0 or a 1 to produce the simplest output expression.

A	B	C	Z
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	x
1	0	0	x
1	0	1	1
1	1	0	1
1	1	1	1

	C'	C
A'B'	0	0
A'B	0	x
AB	1	1
AB'	x	1

	C'	C
A'B'	0	0
A'B	0	0
AB	1	1
AB'	1	1

$z = A$



Outline

- Logic Circuits Simplification
- Combinational Logic Circuits Design
- Karnaugh Map
- **Exclusive-OR & Exclusive-NOR Circuits**
- Enable/Disable Circuits




Exclusive OR and Exclusive NOR Circuits

- The exclusive **OR (XOR)** produces a HIGH output whenever the two inputs are at *opposite* levels.



Exclusive OR (XOR)

 Exclusive **OR** circuit and truth table.




A	B	x
0	0	0
0	1	1
1	0	1
1	1	0

Output expression: $x = \bar{A}B + A\bar{B}$

This circuit produces a **HIGH** output whenever the two inputs are at opposite levels.



Traditional **XOR** gate symbol.

 

An **XOR** gate has only *two* inputs, combined so that $x = \overline{A}B + A\overline{B}$.

A shorthand way indicate the **XOR** output expression is: $x = A \oplus B$.

...where the symbol \oplus represents the **XOR** gate operation.

Output is **HIGH** only when the two inputs are **different** levels.




Exclusive NOR (**XNOR**)

- The exclusive **NOR** (**XOR**) produces a HIGH output whenever the two inputs are at the *same* level.
 - » **XOR** and **XNOR** outputs are opposite.



 Exclusive **NOR** circuit and truth table.




Output expression: $x = AB + \bar{A}\bar{B}$

XNOR produces a HIGH output whenever the two inputs are at the **SAME** levels.



Traditional **XNOR** gate symbol.

 

An **XNOR** gate has only two inputs, combined so that $x = AB + \bar{A}\bar{B}$.


A shorthand way indicate the **XOR** output expression is: $x = \overline{A \oplus B}$.

XNOR represents inverse of the **XOR** operation.


Output is HIGH only when the two inputs are at the same level.



 
Truth table and circuit for detecting equality of two-bit binary numbers.



x_1	x_0	y_1	y_0	z (Output)
0	0	0	0	1
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	1
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	1

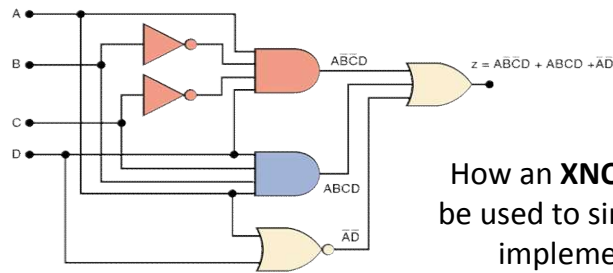

 How an **XNOR** gate may be used to simplify circuit implementation.






Even Parity

- When using **even** parity, the parity bit is set to 1 if the number of ones in a given set of bits (not including the parity bit) is odd, making the entire set of bits (including the parity bit even) even
- Example of even parity is
 - » 0000000
 - » 11010001



Parity Generator and Checker

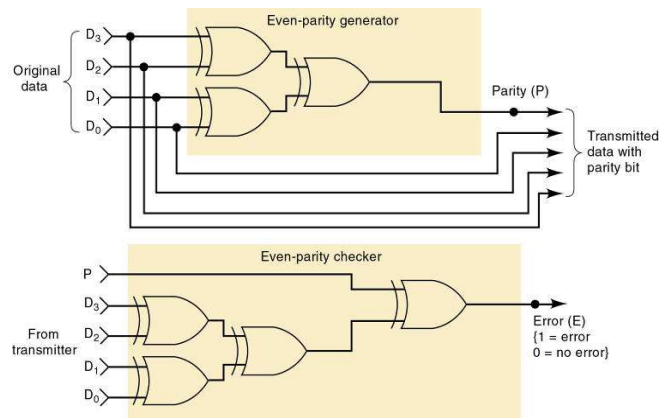XOR and **XNOR** gates are useful in circuits for parity generation and checking.





Outline

- Logic Circuits Simplification
- Combinational Logic Circuits Design
- Karnaugh Map
- Exclusive-OR & Exclusive-NOR Circuits
- **Enable/Disable Circuits**



Enable/Disable Circuits

- A circuit is *enabled* when it *allows* the passage of an input signal to the output.
- A circuit is *disabled* when it *prevents* the passage of an input signal to the output.





Note: Situations requiring enable/disable circuits occur frequently in digital circuit design.



AND

ENABLE





DISABLE

    

OR

ENABLE


DISABLE

    



 Example 1

Input signal: **A** Control inputs: **B & C** Output: **X**



-Question: How can A be transmitted to X?


-Allows A to **pass** to X only when control inputs B and C are both HIGH.

-Otherwise, output will stay LOW.



 Example 2

Input Signal: **A** Control inputs: **B & C** Output: **X**



-Question: How can A be transmitted to X?


-Allow A to **pass** to output only when one, but *not* both control inputs are HIGH.

- Otherwise, output will stay HIGH.



 Example 3

Input signal: **A** Control input: **B** Output: **X&Y**



-Question: How can A be transmitted to X?

- When $B = 1$, output X will follow input A, and output Y will be 0.
- When $B = 0$, output X will be 0, and output Y will follow input A.