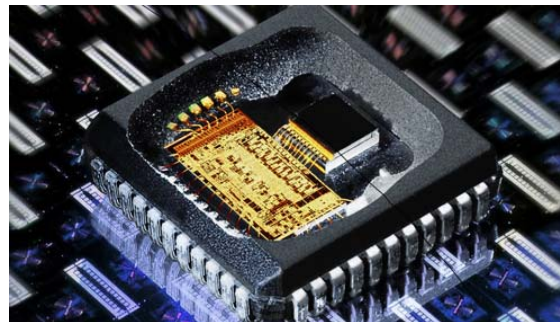




## Lecture 6


# Electronics beyond the Logic Switches

Junrui Liang  
ShanghaiTech University


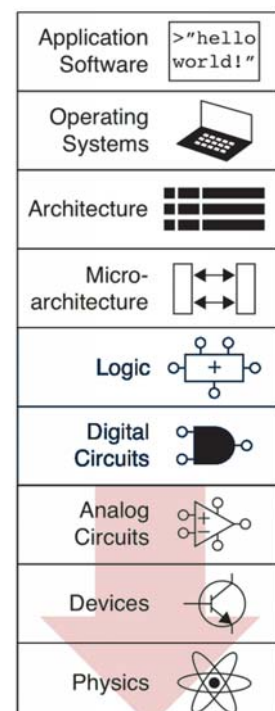
## Outline

- Beneath the digital abstraction
  - » Physical embodiment of digital logics
  - » Noise margins
- Analog electronics
  - » Definition
  - » Diode & MOSFET
  - » Operational amplifier
  - » A/D and D/A conversion
  - » Example: audio systems
- Power electronics
- MEMS





# Outline

- **Beneath the digital abstraction**

- » **Digital abstraction**

- » Noise margins

- Analog electronics

- » Definition

- » Diode & MOSFET


- » Operational amplifier

- » A/D and D/A conversion

- » Example: audio systems

- Power electronics

- MEMS

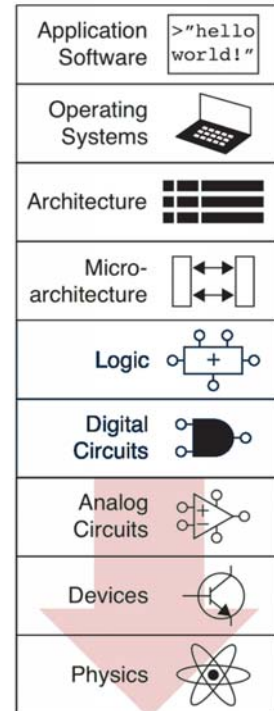

# Digital abstraction

- Digital systems

- » Representing information with discrete-valued variables

- » Binary (two-valued) representation in modern computers


Physical variable	Binary variable		
Positive voltage	"1"	TRUE	HIGH
Zero voltage	"0"	FALSE	LOW

- » Boolean logic: AND, OR, XOR, ....



- » Other operations: addition, subtraction, comparison, ....

# Characteristics of a NOT gate

- Ideal

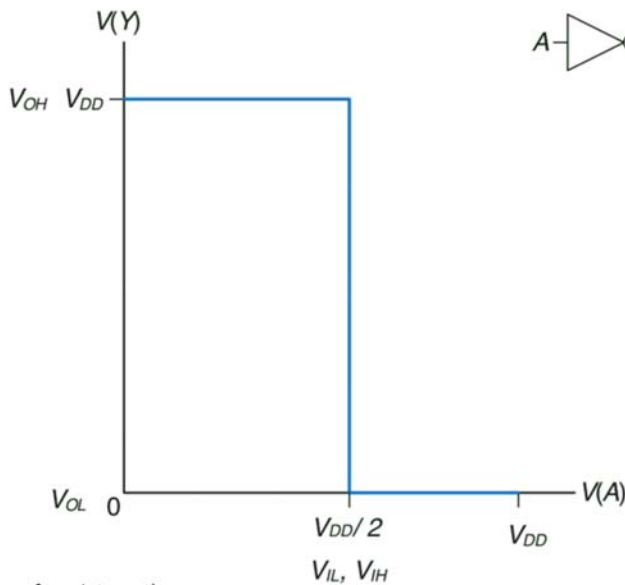

- Practical

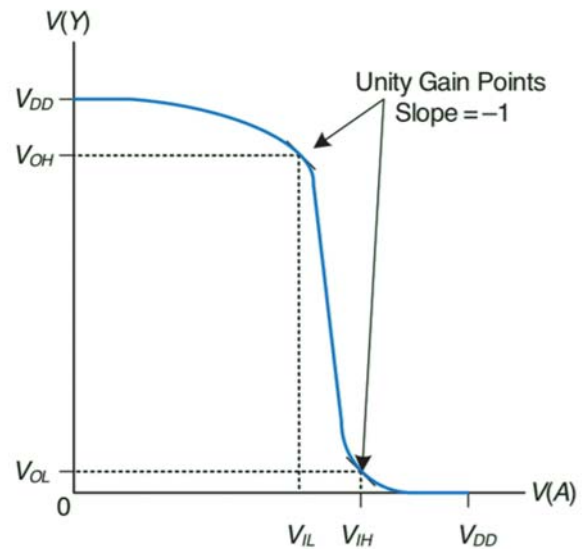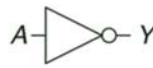

(Figures are from internet)

# Outline

- **Beneath the digital abstraction**


- » Digital abstraction
- » **Noise margins**

- Analog electronics


- » Definition
- » Diode & MOSFET
- » Operational amplifier
- » A/D and D/A conversion
- » Example: audio systems

- Power electronics

- MEMS

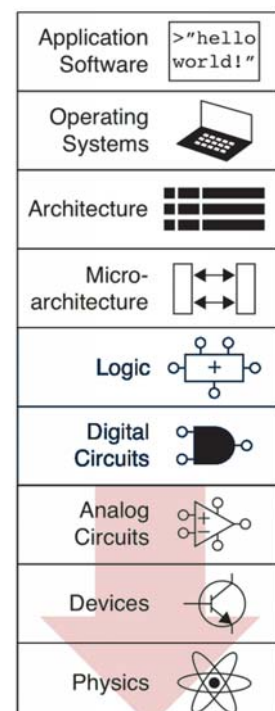


# Noise margins

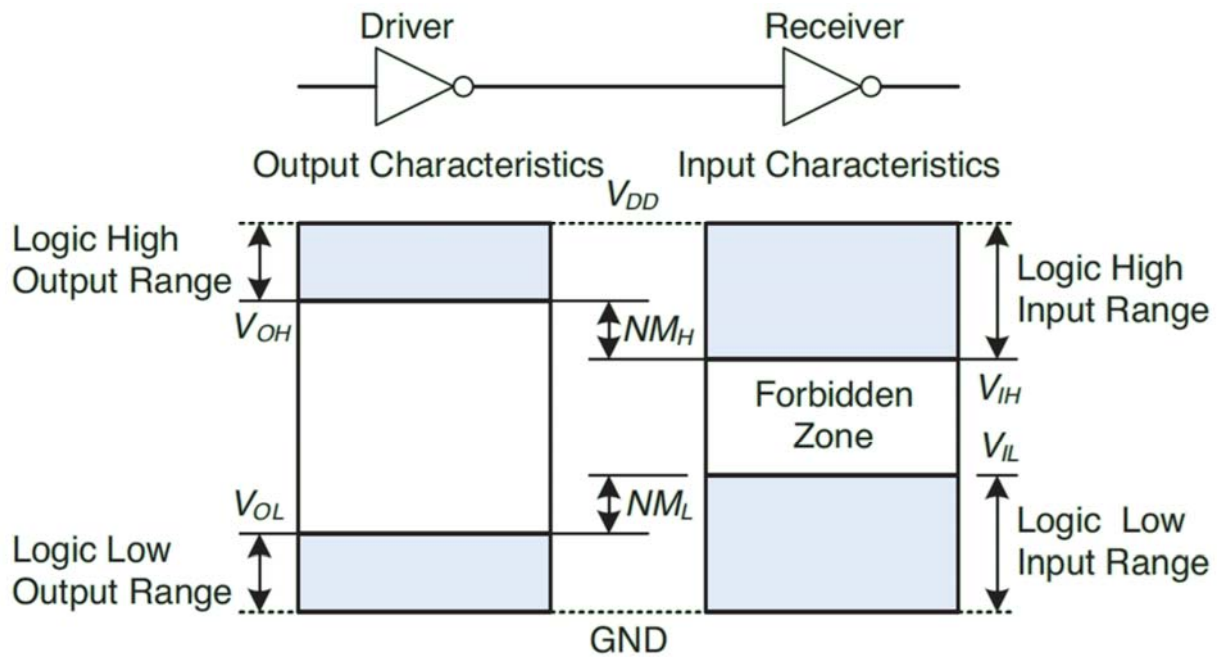

(Figures are from internet)


# Logic family

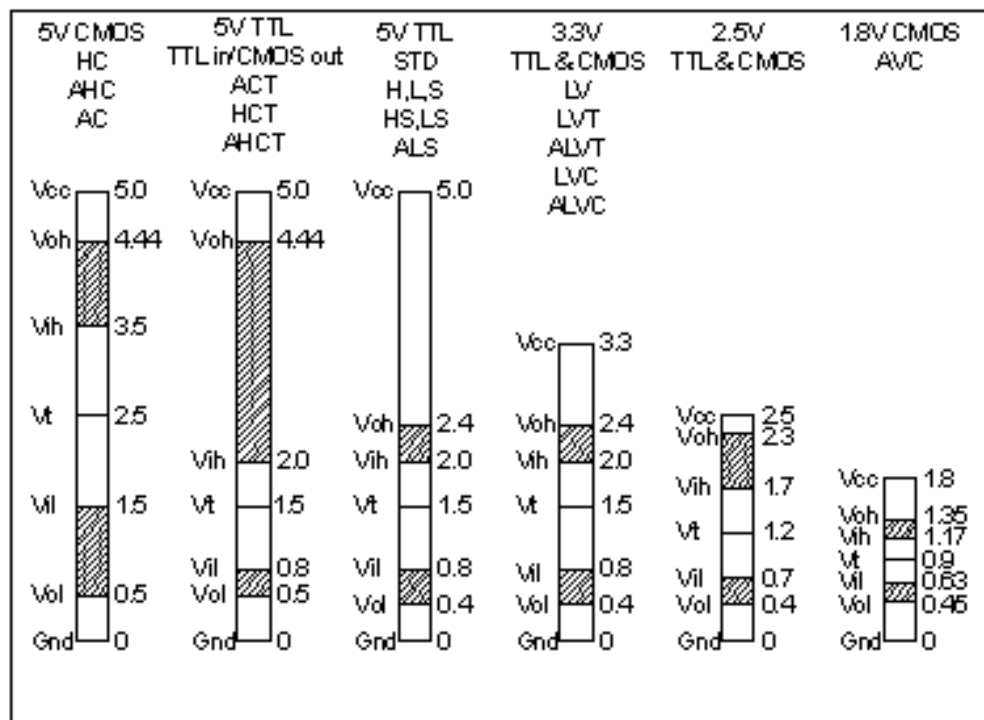

(Figures are from internet)

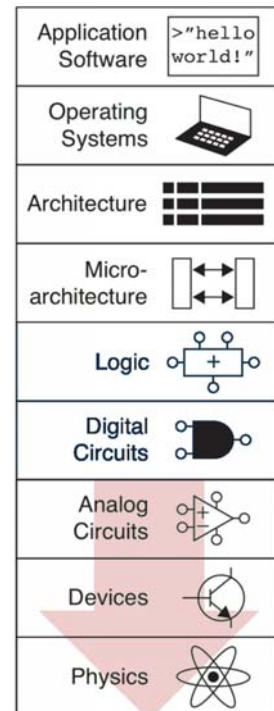
# Outline

- Beneath the digital abstraction
  - » Digital abstraction
  - » Noise margins
- **Analog electronics**
  - » **Definition**
  - » Diode & MOSFET
  - » Operational amplifier
  - » A/D and D/A conversion
  - » Example: audio systems
- Power electronics
- MEMS



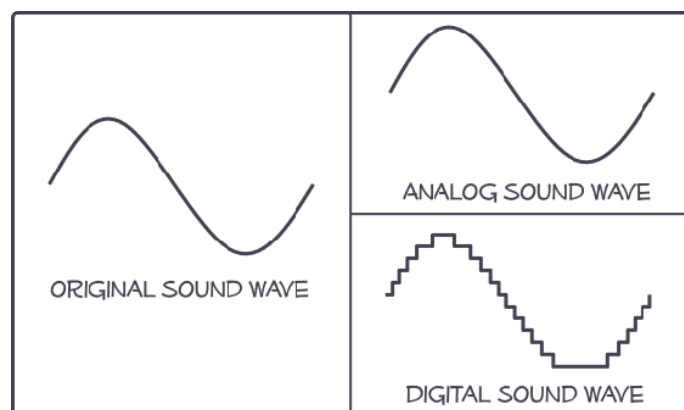
# Definition

- Electronic systems with a **continuously variable signal**
- The term "analog", derived from the Greek word  $\alpha\acute{\nu}\alpha\lambda\omicron\gamma\omicron\varsigma$  (analogos), describes the **proportional relationship** between a signal and a voltage or current that represents the signal




(Figures are from internet)

# Diode vs. one way valve

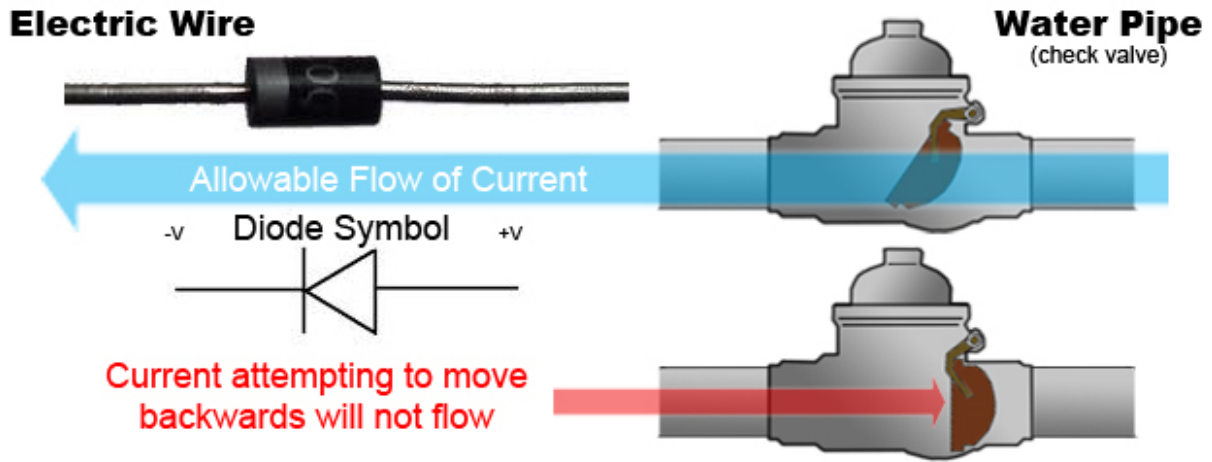

(Figures are from internet)


# Semiconductors

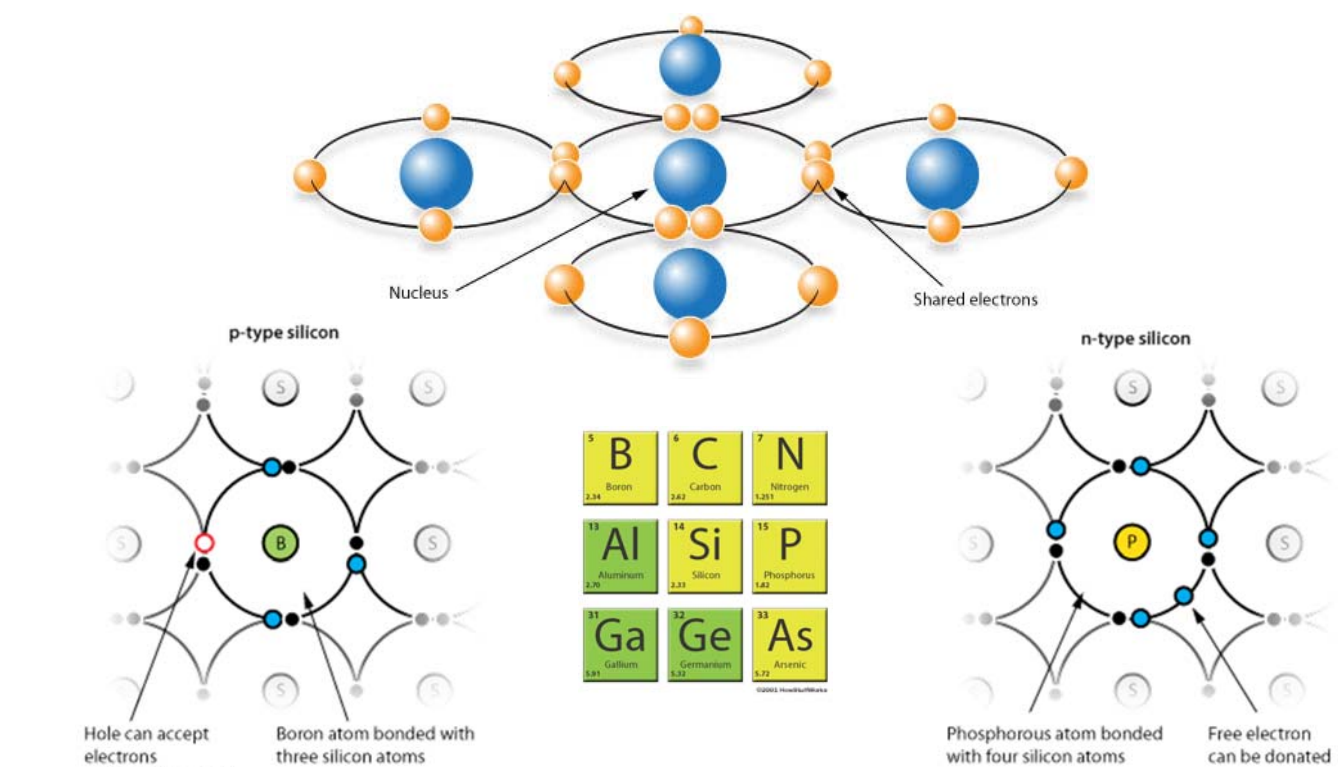

(Figures are from internet)




# PN junction

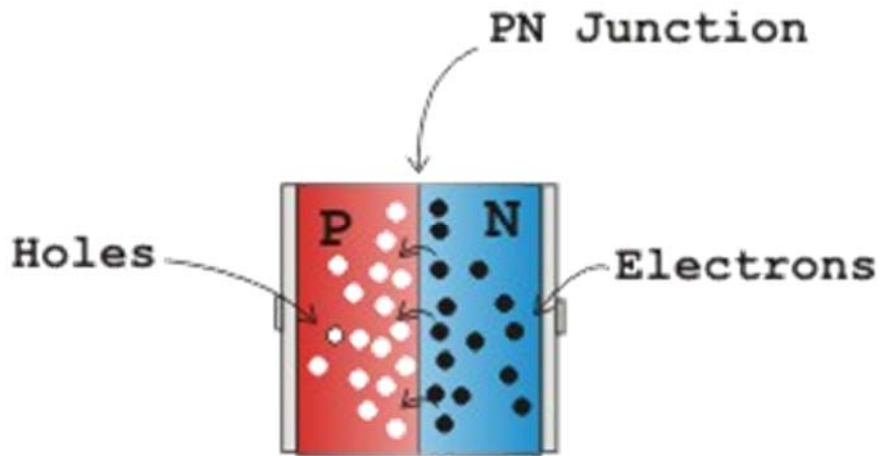


(Figures are from internet)

# PN junction

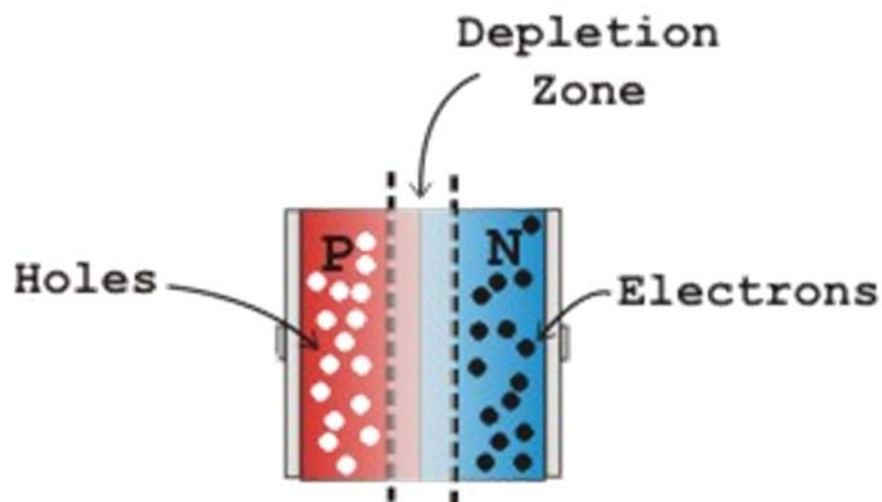


(Figures are from internet)

# Forward Biased

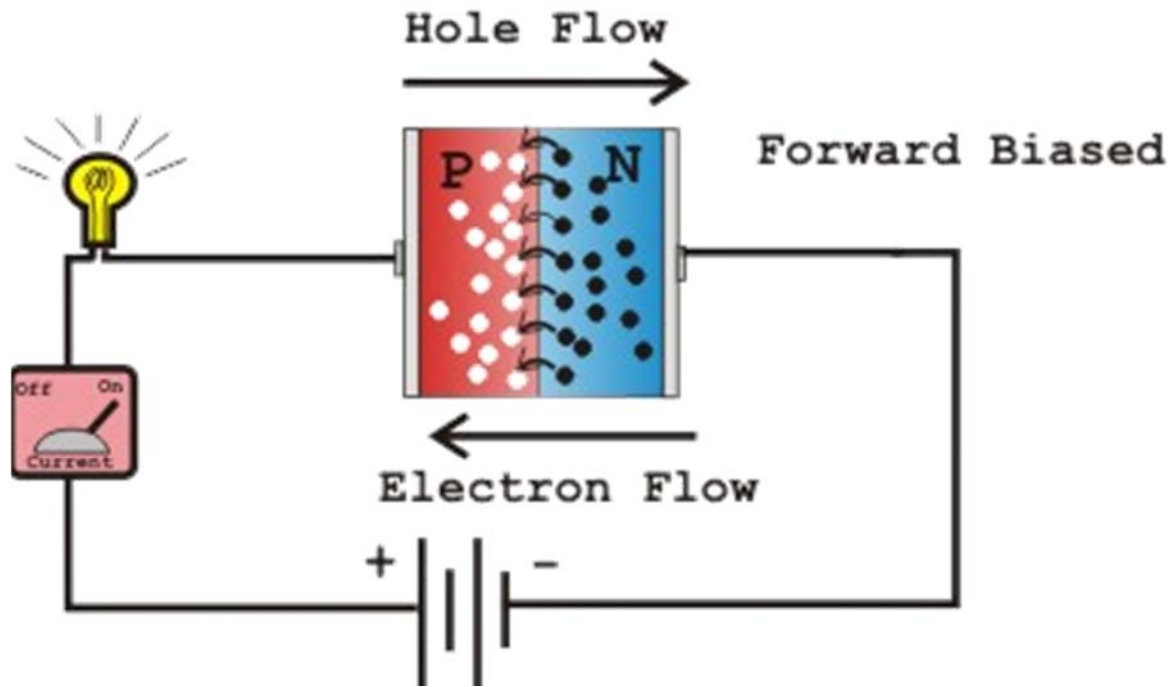

(Figures are from internet)

# Reverse Biased

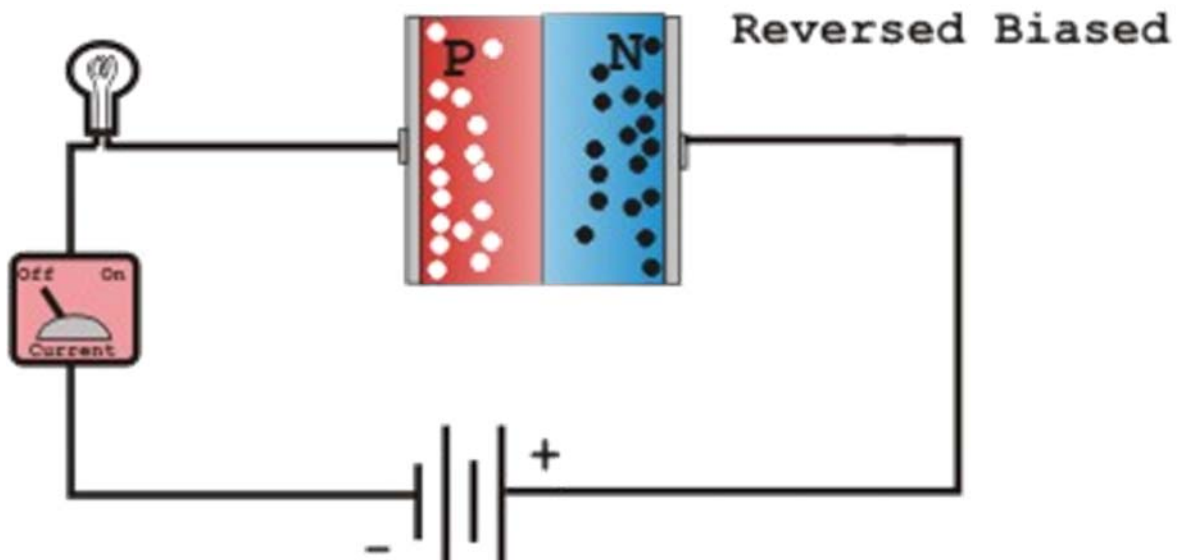


(Figures are from internet)






# Electrical behavior of a switch

● Switch on 

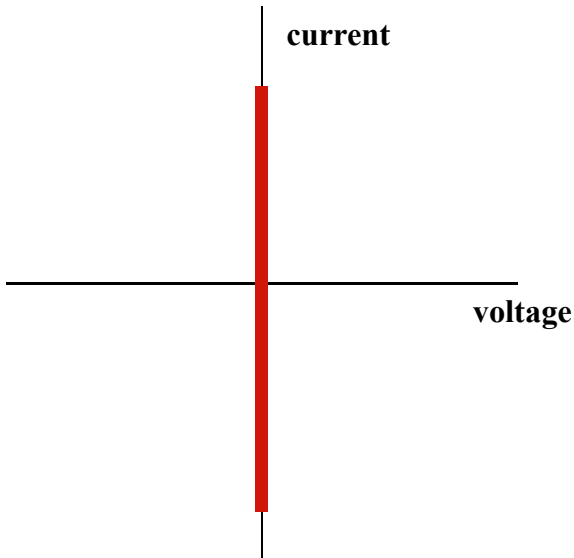

● Switch off 

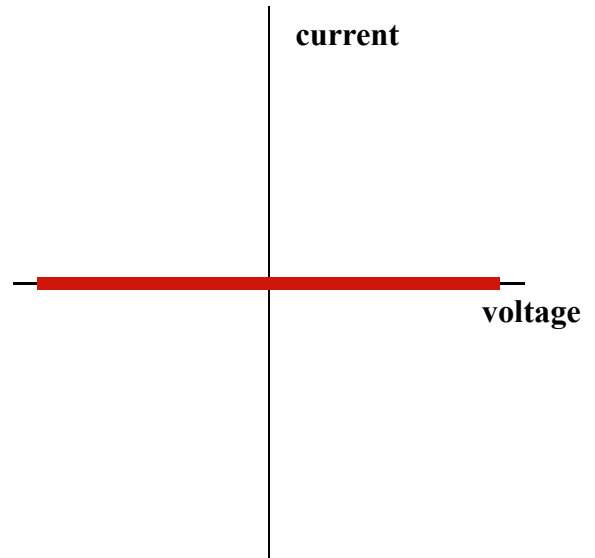


(Figures are from internet)




# Electrical behavior of an diode

● Ideal diode

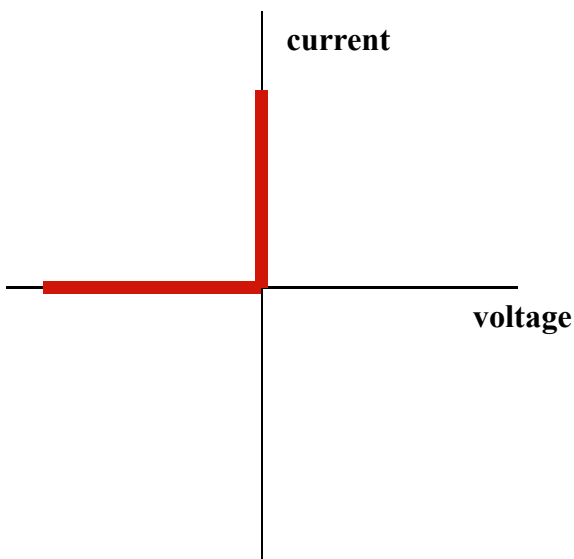


● Practical diode

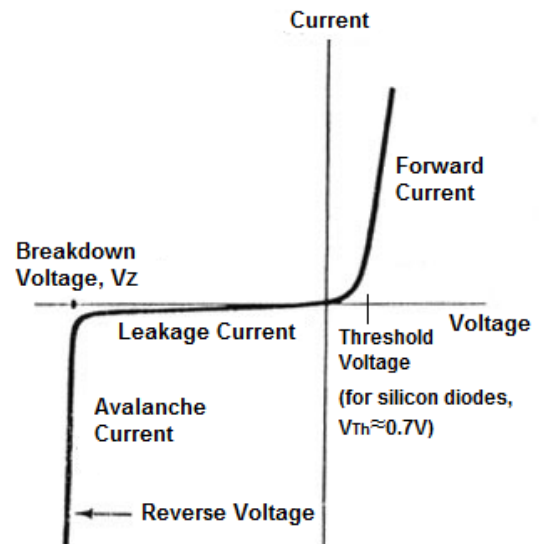

(Figures are from internet)

# Diode modeling

- Piecewise-linear model

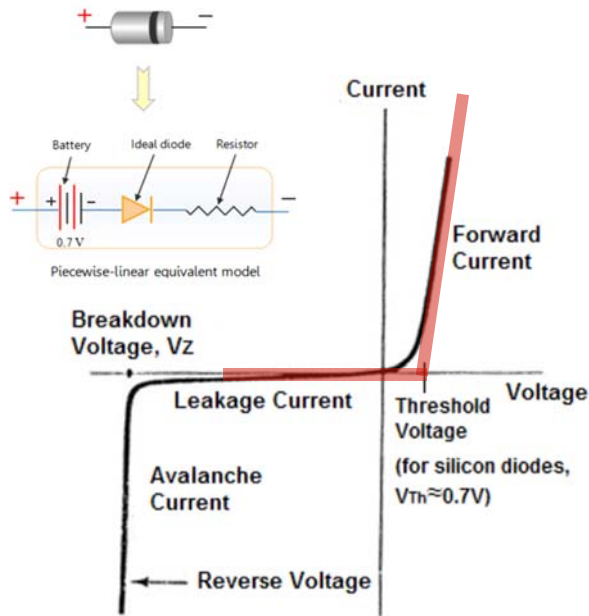

- I/V characteristics

$$I = I_S \left[ e^{\left(\frac{V_D}{nV_T}\right)} - 1 \right]$$


$I_S$ : saturation current

$V_T = kT/q$ : thermal voltage


$n$ : diode ideality factor (1~2 for silicon diodes)

(Figures are from internet)


# MOSFET

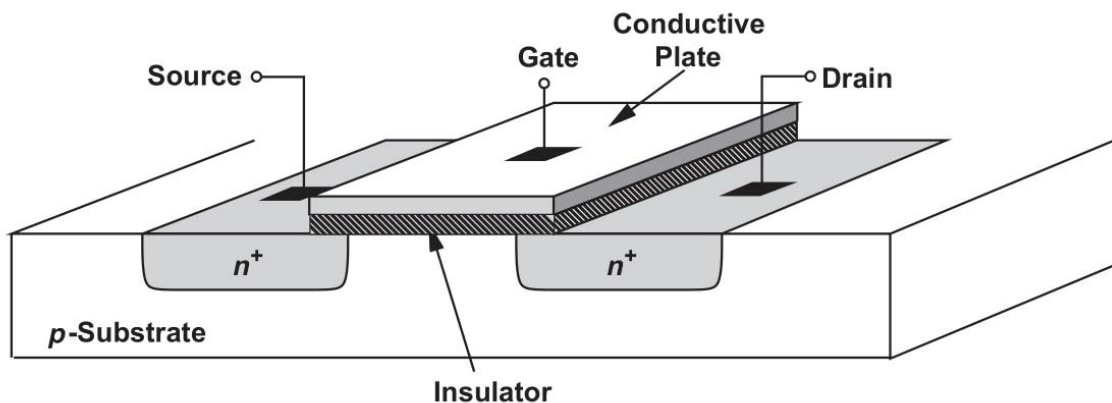

Sideview



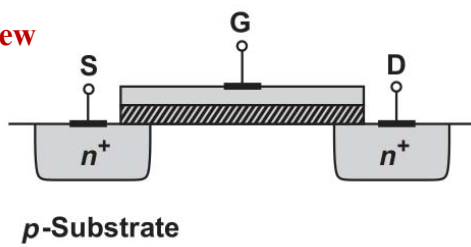


Symbol

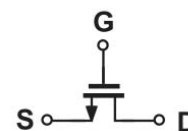


(Razavi, Fundamentals of Microelectronics)

# Applying gate voltage

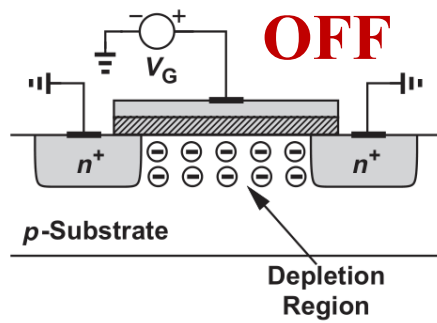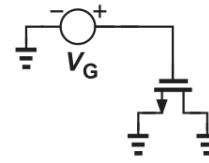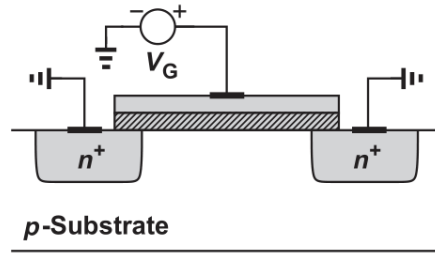

**Formation of depletion region**

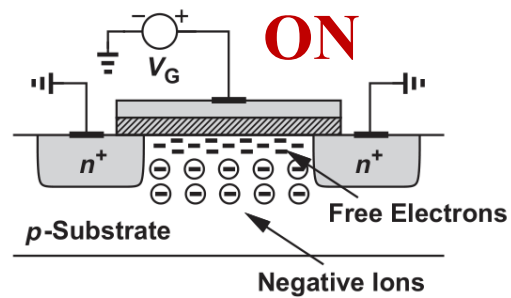


**Formation of channel**


(Razavi, Fundamentals of Microelectronics)

# Physical layout of MOS NAND gate

- CMOS NAND gate

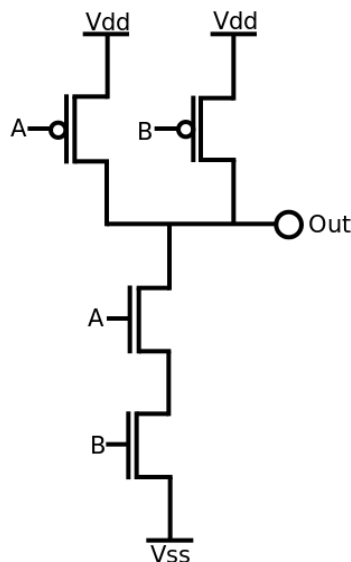


- Physical layout

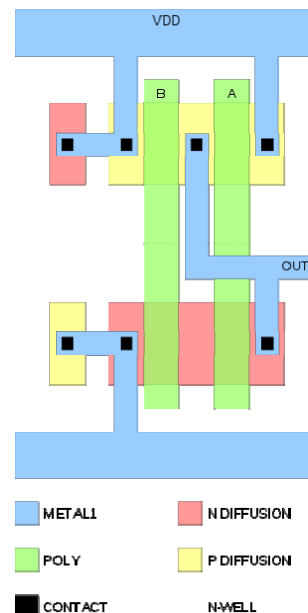


(Razavi, Fundamentals of Microelectronics)

# Beyond the on/off states

- For digital electronics

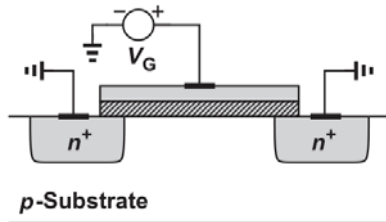


**Cut off**

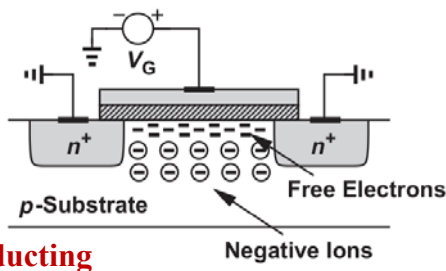


**Conducting**

- For analog electronics

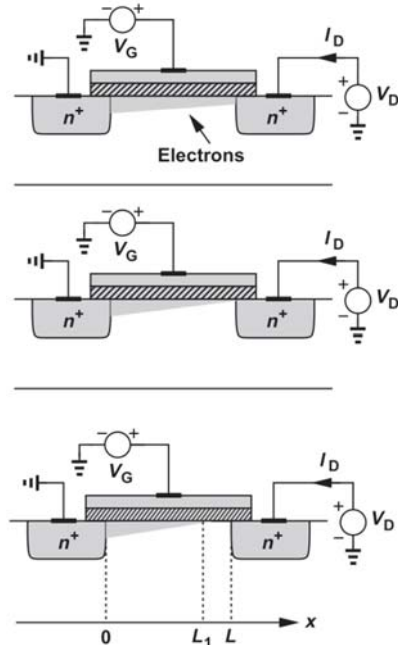

(Razavi, Fundamentals of Microelectronics)

# I/V characteristics

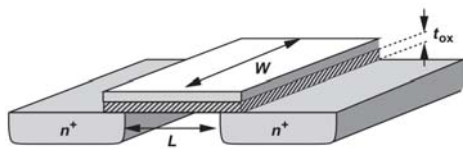

**Linear region:**


$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} [2(V_{GS} - V_{TH})V_{DS} - V_{DS}^2]$$

**A voltage-controlled resistor**

**Saturation region:**


$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2 (1 + \lambda V_{DS})$$

**A voltage controlled current source**

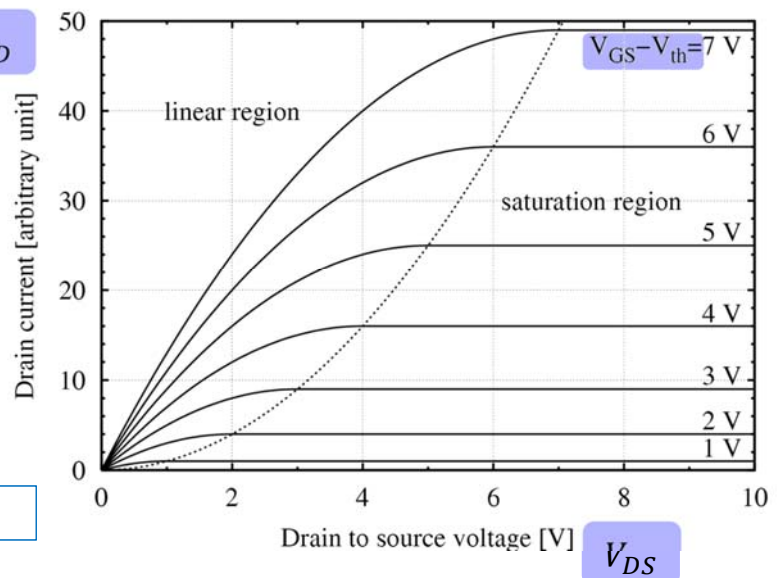

(Razavi, Fundamentals of Microelectronics)


# Basic MOS amplifier

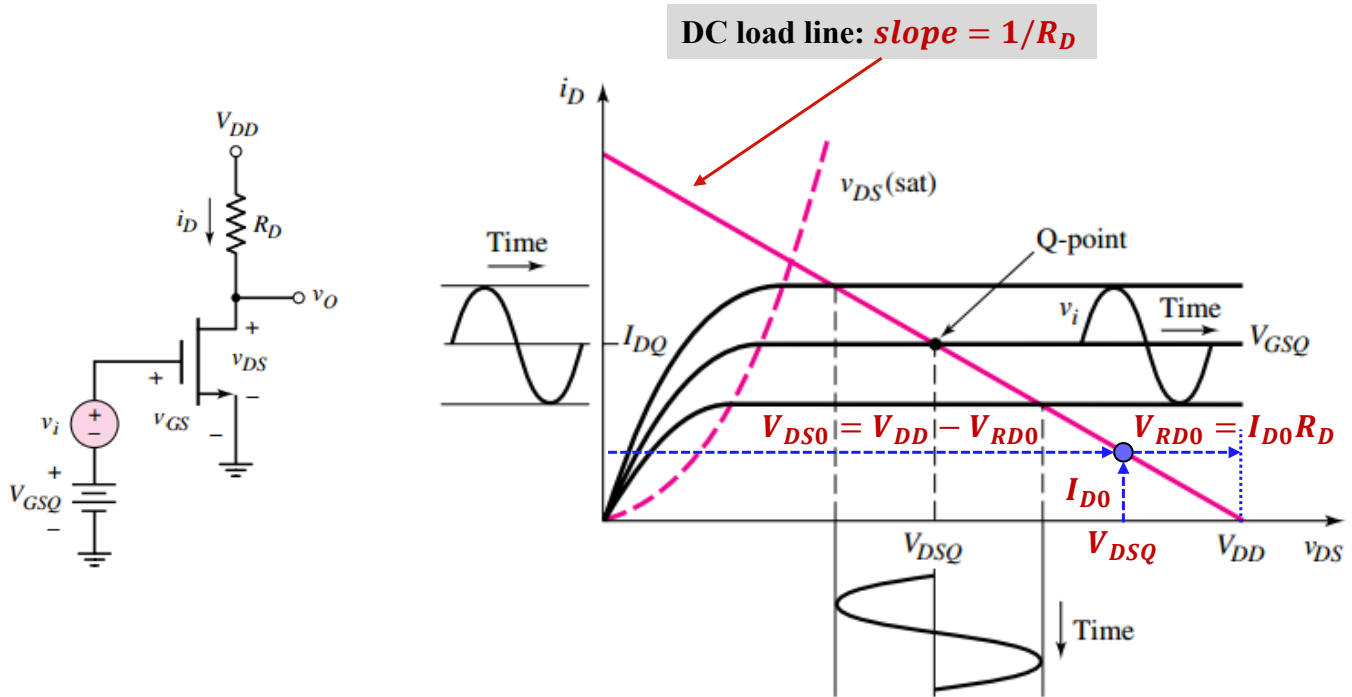

(Neamen, Electronic Circuit Analysis and Design)

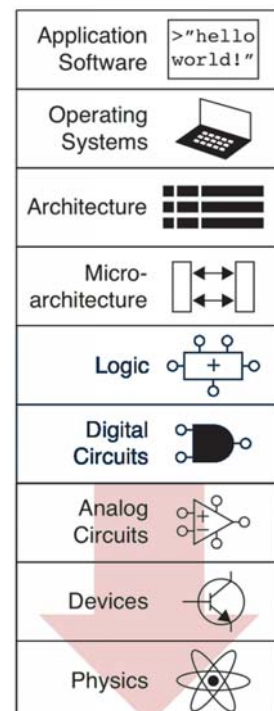
# Outline

- Beneath the digital abstraction
  - » Digital abstraction
  - » Noise margins
- **Analog electronics**
  - » Definition
  - » Diode & MOSFET
  - » **Operational amplifier**
  - » A/D and D/A conversion
  - » Example: audio systems
- Power electronics
- MEMS


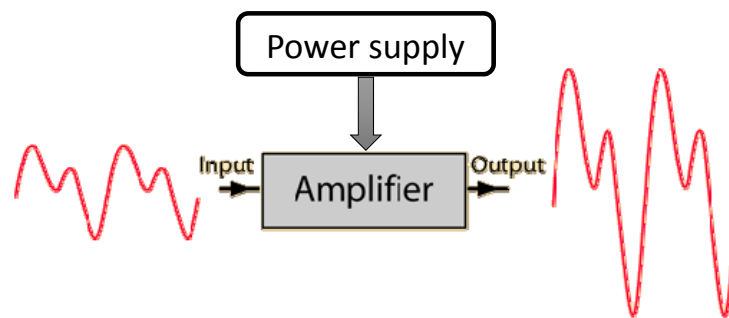
# Amplifier


- An electronic device that increases the power of a signal
  - » Taking energy from a **power supply**
  - » controlling the output to match the input signal shape but with a larger **amplitude**
  - » The opposite of an attenuator
  - » An amplifier provides **gain**, an attenuator provides loss




(Figures are from internet)
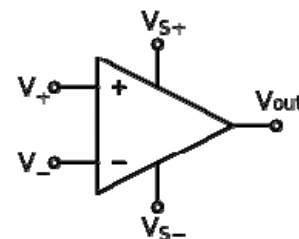
# Operational amplifier (运算放大器)

- Characteristics
  - » DC-coupled
  - » Voltage amplifier
  - » High gain ( $A \rightarrow \infty$ )
  - » A differential input ( $V_+ - V_-$ )
  - » A single-ended output ( $V_{out}$ )
- Originally from analog computers for doing mathematical operations
- One of the most widely used electronic devices



$$V_{out} = A(V_+ - V_-)$$

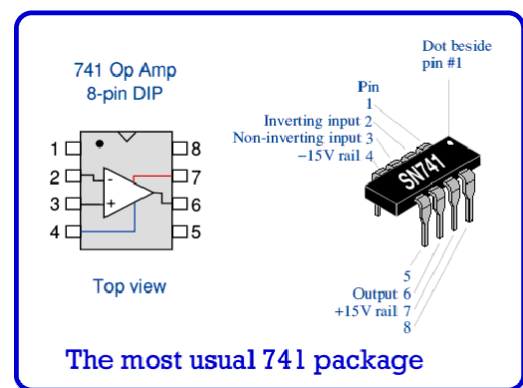


(Figures are from internet)




# Realization

- BJT Technology

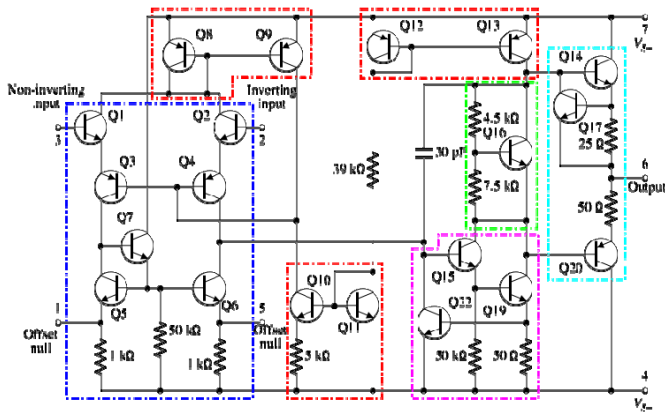

- CMOS Technology

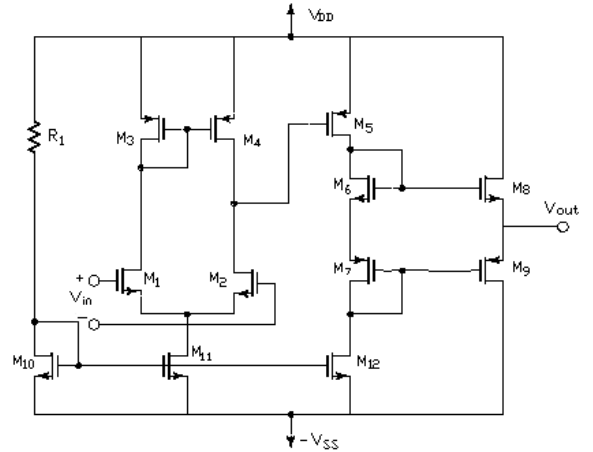


A component-level diagram of the common 741 op-amp. Dotted lines outline: current mirrors (red); differential amplifier (blue); class A gain stage (magenta); voltage level shifter (green); output stage (cyan).

(Figures are from internet)
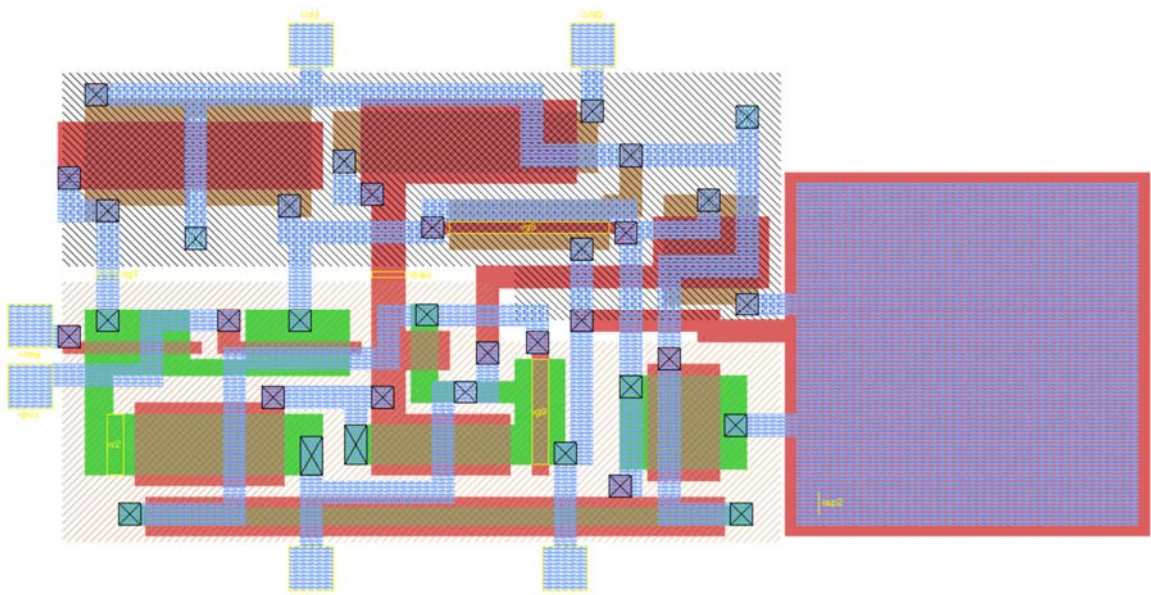
# Realization


- Layout view of a simple CMOS operational amplifier




(Figures are from internet)

# Applications

- Audio system

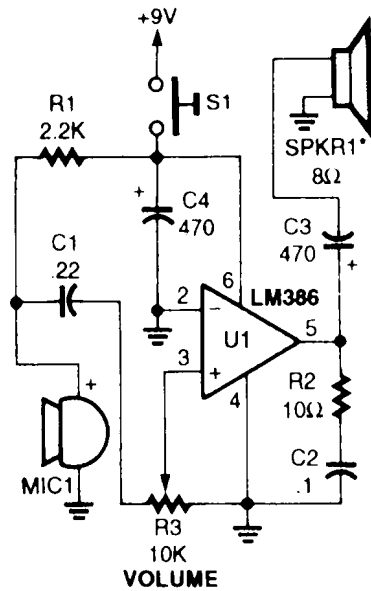


- Bio-electric signal

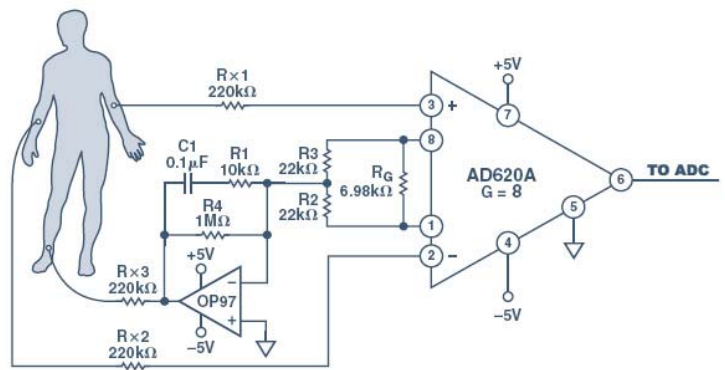

(Figures are from internet)

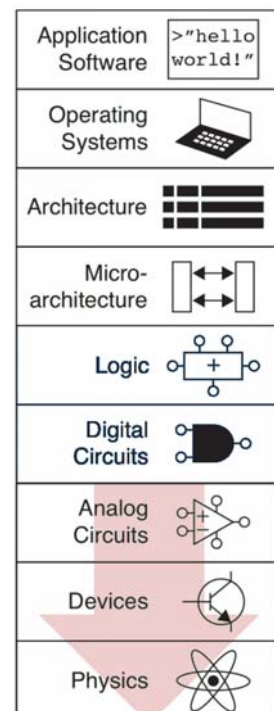
# Outline

- Beneath the digital abstraction
  - » Digital abstraction
  - » Noise margins
- **Analog electronics**
  - » Definition
  - » Diode & MOSFET
  - » Operational amplifier
  - » **A/D and D/A conversion**
  - » Example: audio systems
- Power electronics
- MEMS


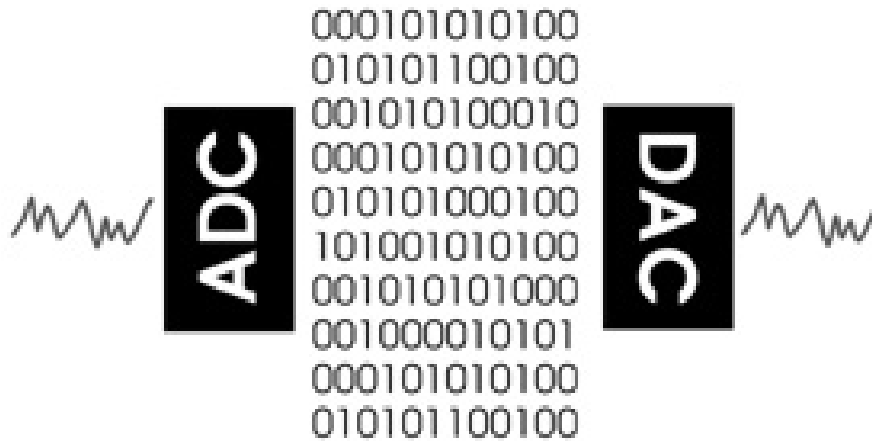
# Applications



- Connecting the digital computers and physical world



(Figures are from internet)

# A/D and D/A conversions



- Symbols

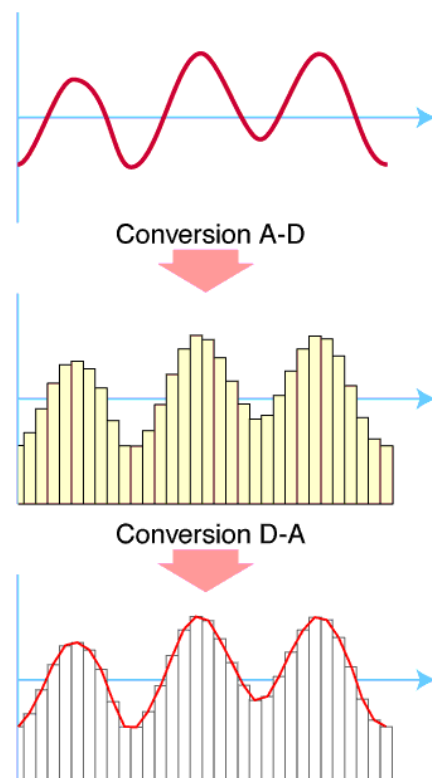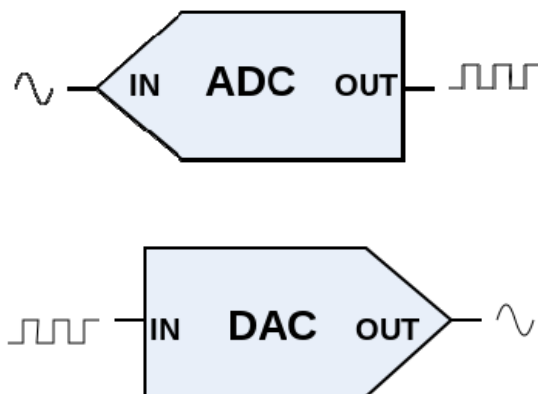

(Figures are from internet)


# Digital-to-analog converters

- Pulse-width modulation

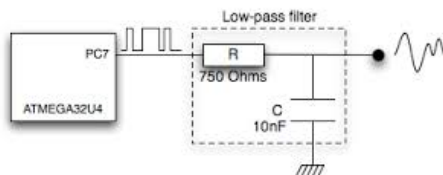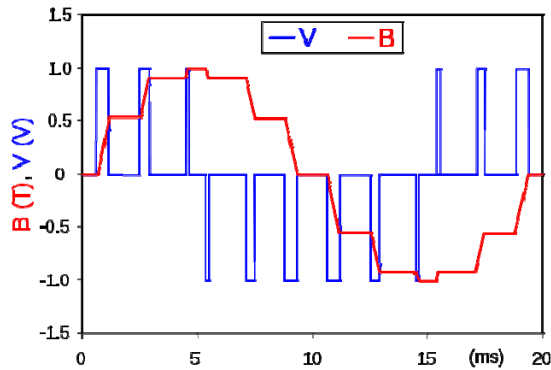

(Figures are from internet)


- The R-2R ladder DAC

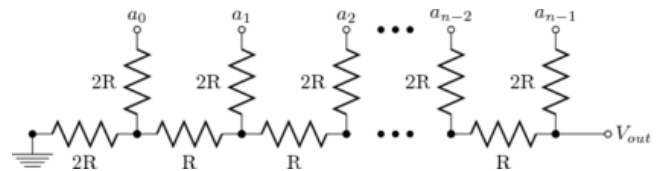


$$V_{out} = \frac{a_{n-1}}{2} + \frac{a_{n-2}}{4} + \dots + \frac{a_2}{2^{n-2}} + \frac{a_1}{2^{n-1}} + \frac{a_0}{2^n}$$
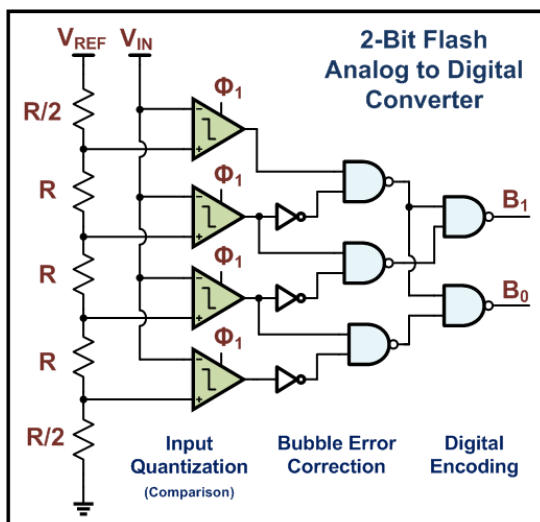
# Analog-to-digital converters

- Flash ADC (also known as a Direct conversion ADC)




- Successive approximation ADC

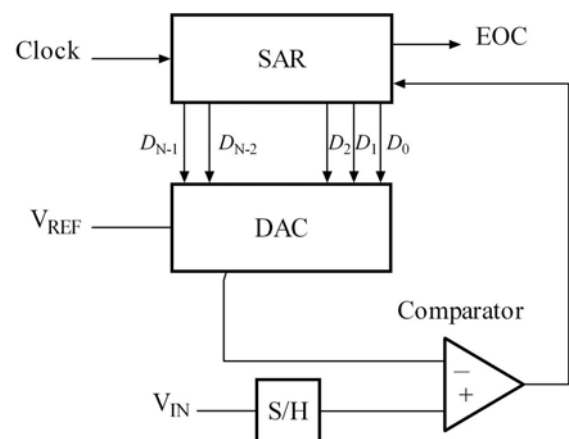
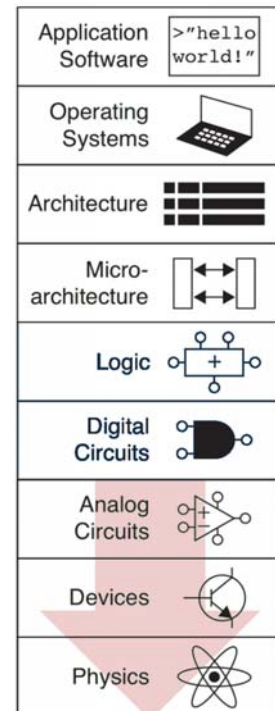
# Outline

- Beneath the digital abstraction
  - » Digital abstraction
  - » Noise margins
- **Analog electronics**
  - » Definition
  - » Diode & MOSFET
  - » Operational amplifier
  - » A/D and D/A conversion
  - » **Example: audio systems**
- Power electronics
- MEMS



# Analog vs. digital audio systems

## Signals in analog amplifier




## Signals in digital amplifier





# Digital audio system

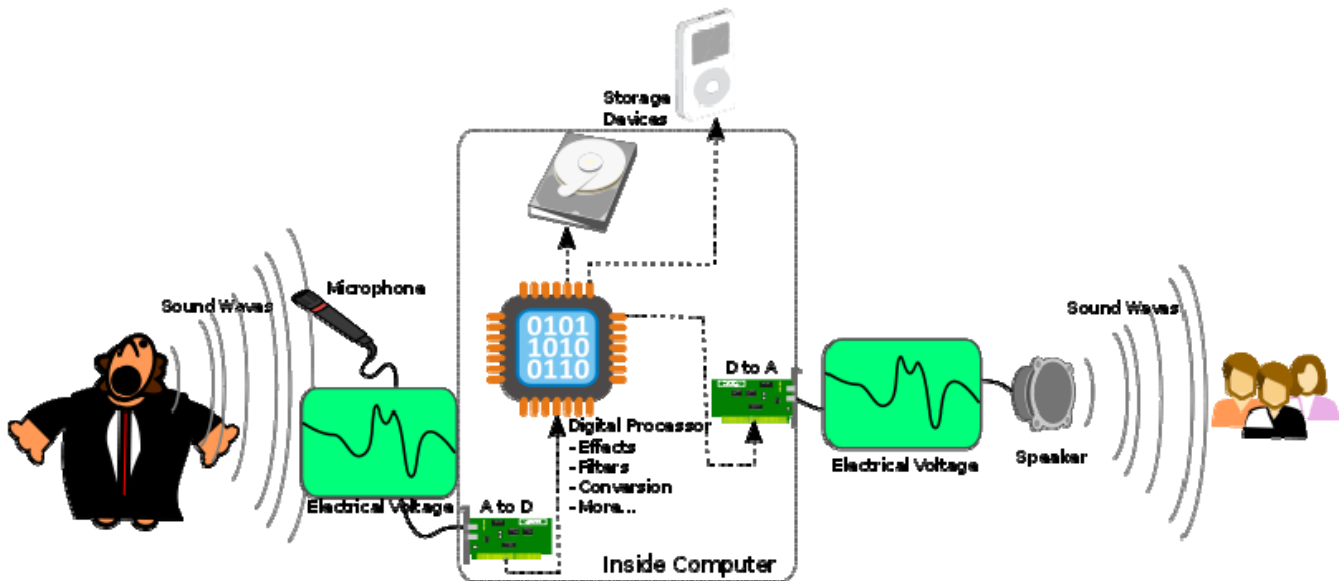

(Figures are from internet)


# Outline

- Beneath the digital abstraction
  - » Digital abstraction
  - » Noise margins
- Analog electronics
  - » Definition
  - » Diode & MOSFET
  - » Operational amplifier
  - » A/D and D/A conversion
  - » Example: audio systems
- **Power electronics**
- MEMS

Application Software	>"hello world!"
Operating Systems	
Architecture	
Micro-architecture	
Logic	
Digital Circuits	
Analog Circuits	
Devices	
Physics	



# Relations between signal and power

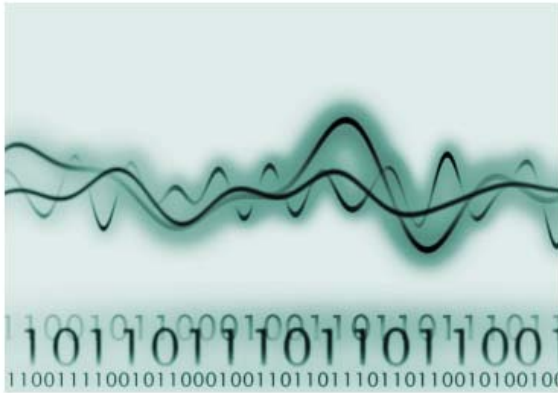


**Signal** – a function that conveys **information** about the behavior or attributes of some phenomenon

**Power** is a necessity for the acquisition, conditioning, transmission, storage, and visualization of signals (data)

(Figures are from internet)

# Different forms of electric power

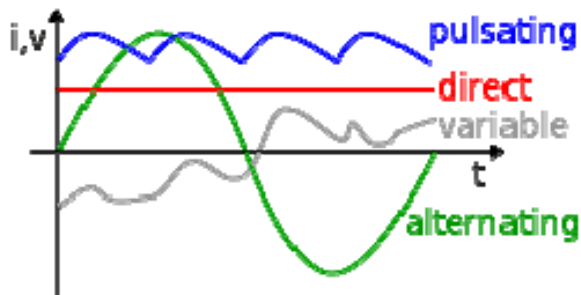

- Direct current (DC) power



- Alternating current (AC) power



(Figures are from internet)


# Power electronics

- The application of **solid-state electronics** to the control and conversion of electric power
- Conversions among different forms
  - » AC to DC (rectifier)
  - » DC to AC (inverter)
  - » DC to DC (DC-to-DC converter)
  - » AC to AC (AC-to-AC converter)


(Figures are from internet)

## Example: half-wave rectifier


### Without filter capacitor

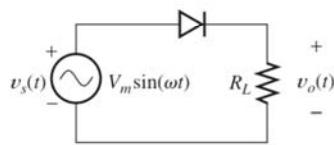

(a) Circuit diagram

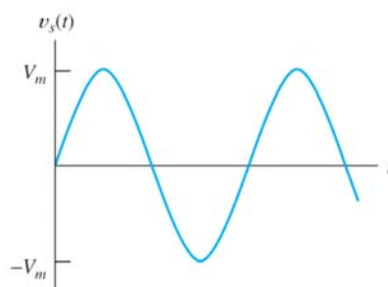


(b) Source voltage versus time

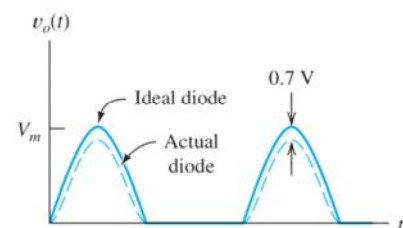


(c) Load voltage versus time


### With filter capacitor

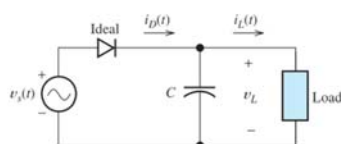

(a) Circuit diagram

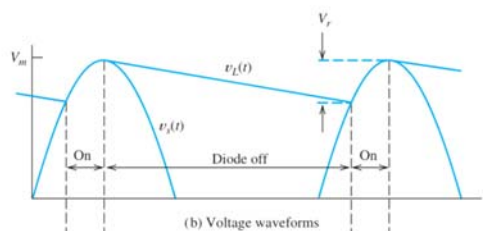


(b) Voltage waveforms

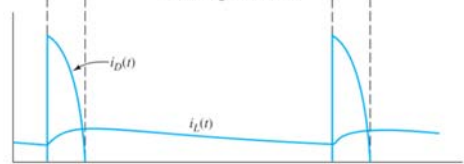

(c) Current waveforms


(Figures are from internet)

# Example: full-wave rectifier

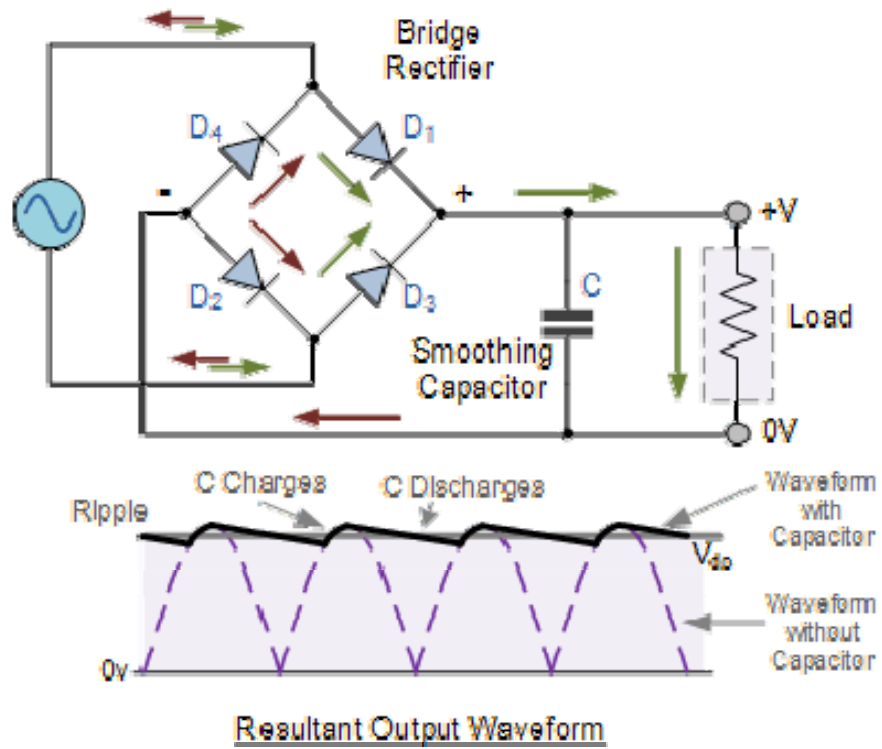


(Figures are from internet)

# PE applications

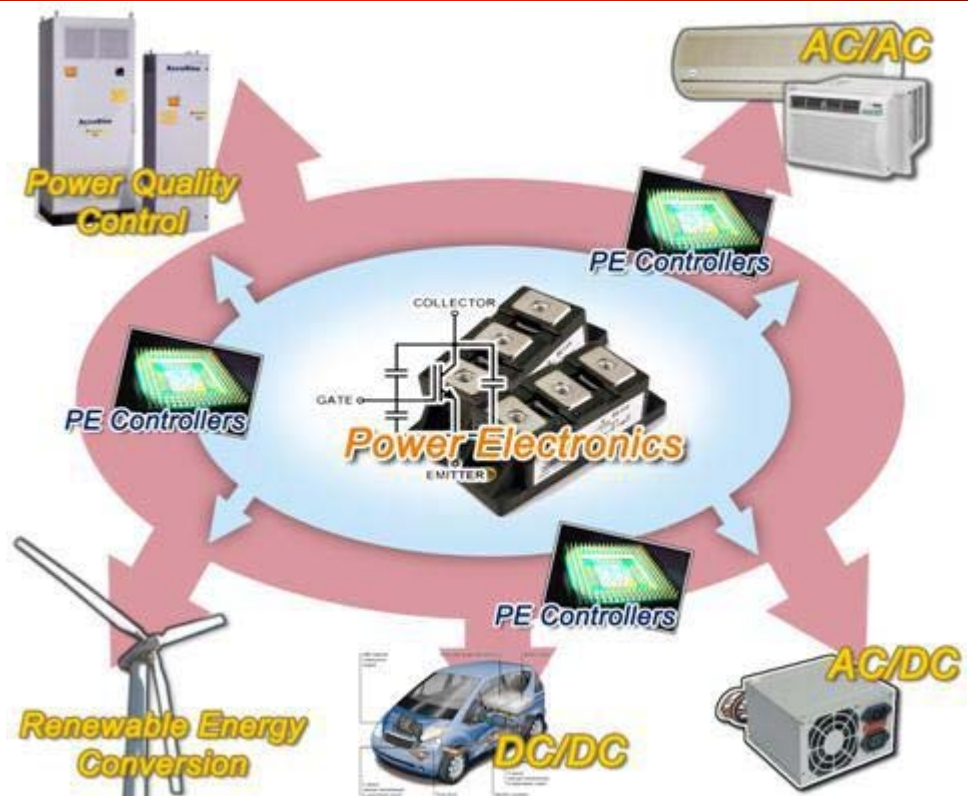


(Figures are from internet)

# PE devices

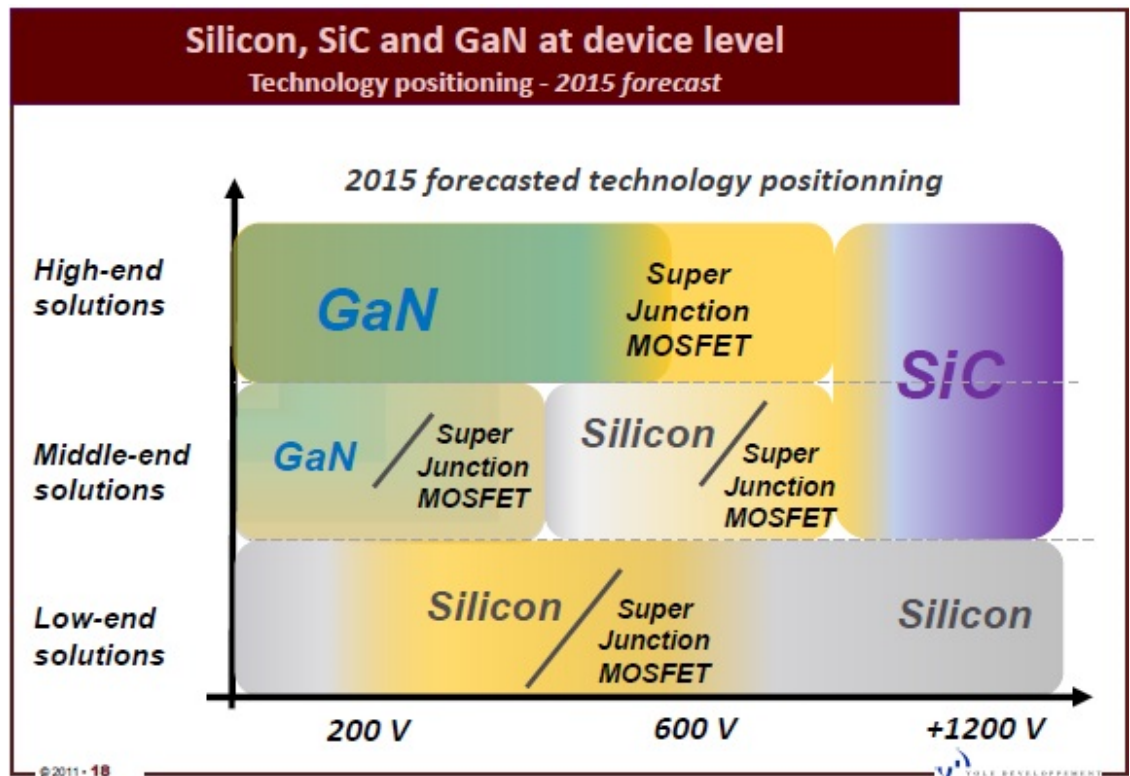
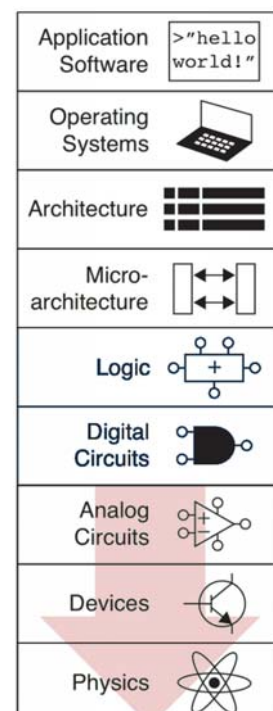
# Outline


- Beneath the digital abstraction
  - » Digital abstraction
  - » Noise margins
- Analog electronics
  - » Definition
  - » Diode & MOSFET
  - » Example: audio systems
  - » Operational amplifier
  - » A/D and D/A conversion
- Power electronics
- **MEMS**




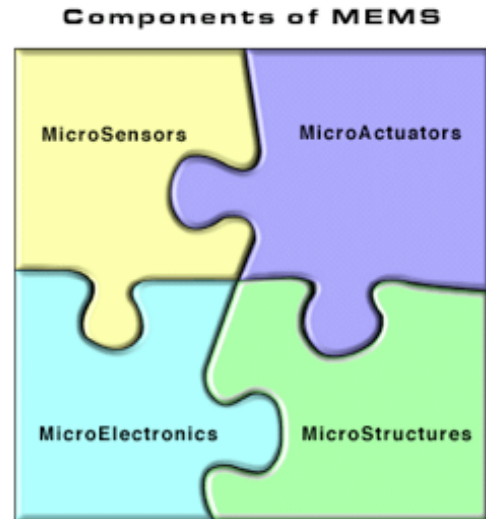
# MEMS


- Microelectromechanical systems
  - » miniaturized mechanical and electro-mechanical elements (i.e., devices and structures) that are made using the techniques of microfabrication
  - » it merges at the nano-scale into nanoelectromechanical systems (NEMS) and nanotechnology




(Figures are from internet)

# MEMS applications


- Sensors

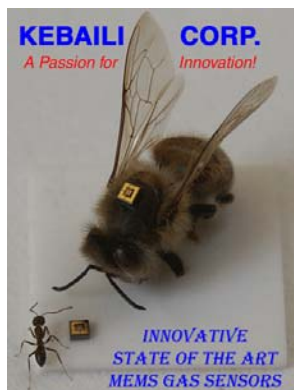

- Actuators

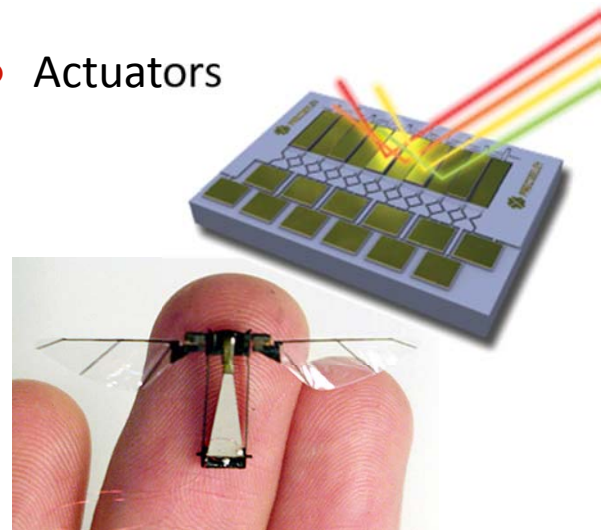

- Structures

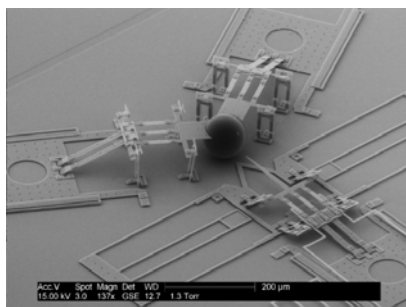

- Etc.

(Figures are from internet)

# MEMS in smart phone


Smart phone is driving new MEMS developments



(<http://smartphoneworld.me>)

# Example: MEMS accelerometer

● Principle

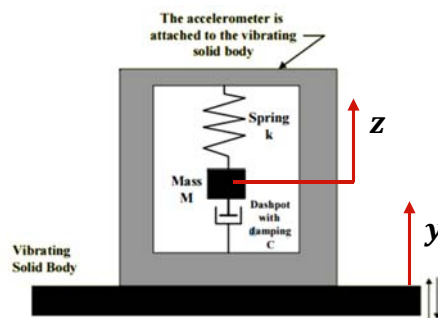


Relative displacement

$$x = z - y$$

$$\rightarrow \ddot{x} + \frac{C}{m} \dot{x} + \frac{k}{m} x = -\ddot{y} = -a(t)$$

In the frequency domain
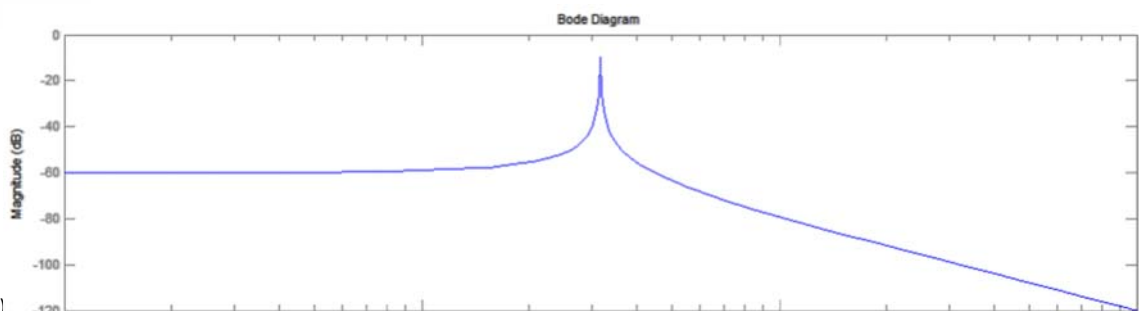
$$\frac{X(j\omega)}{A(j\omega)} = \frac{m}{k - m\omega^2 + j\omega c}$$





(Figures are from internet)




# Example: MEMS accelerometer

- Measurement

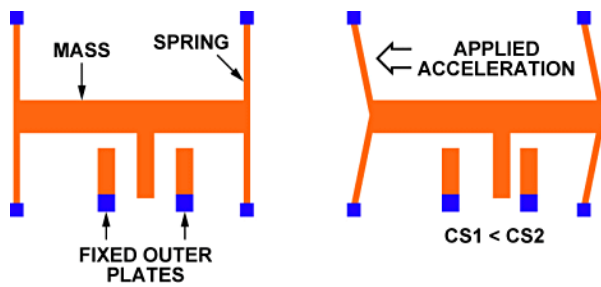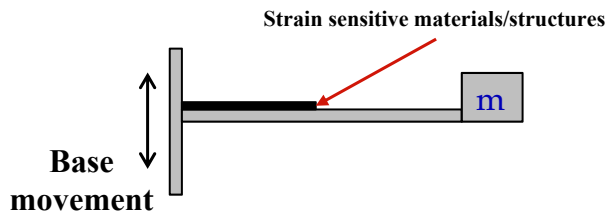

- Manufacturing process

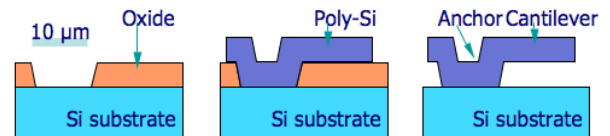

(Figures are from internet)