 


Computer Architecture Homework 4


Spring 2019, March

1 Synchronous Finite State Digital Machine Systems


- a. The circuit shown below can be simplified. Write a Boolean expression that represents the function of the simplified circuit using the minimum number of AND, OR, and NOT gate.



 b. Consider the finite state machine below which has 6 states and a single input that can take on the value of 0 and 1. The finite state machine should output 1 IF AND ONLY IF 6 + sum of all the input values is not divisible by 2 or 3. One transition has been provided; complete the remainder of the diagram. (Hint: If the sum of the inputs is a multiple of 6, then we have $6 + \text{sum of the inputs} = 6n$ for some n . As $6n$ is divisible by 2, $6n$ cannot be prime.)



 c. Consider the following circuit. Assume registers have a CLK to Q time of 60ps, a setup time of 40ps, and a hold time of 30ps. Assuming that all gates have the same propagation delay, what is the maximum propagation delay each individual gate could have to achieve a clock rate of 1 GHz.



2 Boolean Logic

1. Simplify each Boolean expression to one of the following ten expressions:
 $0, 1, A, B, AB, A + B, \bar{A} \bar{B}, \bar{A} + \bar{B}, A\bar{B}, \bar{A}B$
Each answer may be used as many times as necessary.

a. $A(A + \bar{A}) + B$

b. $(A + B)(\bar{A} + B)\bar{B}$

c. $\overline{\bar{A} + \bar{B}}$

2. Simplify the following expression step by step (as simple as possible):

a. Standard: $(A + B)(A + \bar{B})C$

b. Grouping & Extra Terms: $\bar{A} \bar{B} \bar{C} + \bar{A} B \bar{C} + A \bar{B} \bar{C} + A \bar{B} C + A B \bar{C} + A B C + A \bar{B} C$

c. DeMorgan's: $\overline{A(\bar{B} \bar{C} + BC)}$

